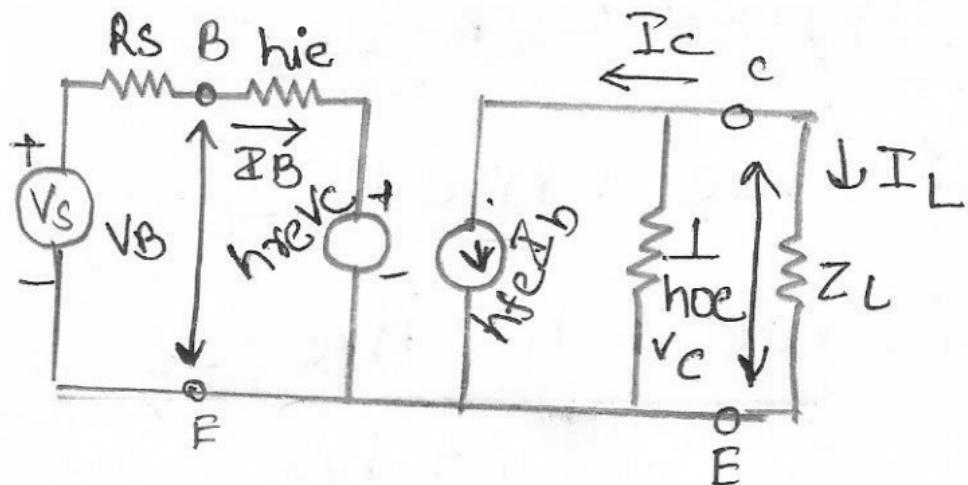


Analysis of CE amplifier;



$$V_B = h_{ie} Z_B + h_{re} V_C \quad \text{--- ①}$$

$$I_C = h_{fe} Z_B + h_{oe} V_C \quad \text{--- ②}$$

Current gain (A_i^o) :

$$A_i^o = -\frac{I_C}{Z_B}$$

$$V_C = I_L Z_L = -I_C Z_L$$

$$I_C (1 + h_{oe} Z_L) = h_{fe} Z_B$$

$$A_i^o = \frac{-h_{fe}}{1 + h_{oe} Z_L}$$

Input impedance (Z_i):

$$V_C = I_L Z_L = -I_C Z_L$$

$$A_i^o = \frac{-I_C}{Z_b}$$

~~$$V_C = A_i^o I_b Z_L$$~~

$$V_b = h_{ie} Z_b + h_{re} A_i^o Z_b Z_L$$

divide with Z_b

$$Z_i^o = h_{ie} + h_{re} A_i^o Z_L$$

$$Z_i^o = h_{ie} - \frac{h_{fe} h_{re} \cdot Z_L}{1 + h_{oe} Z_L}$$

$$Z_i^o = h_{ie} - \frac{h_{fe} h_{re}}{Y_0 + h_{oe}}$$

Voltage gain (A_v):

$$A_v = \frac{V_C}{V_b}$$

$$V_b = I_b Z_i^o$$

$$V_C = -I_C Z_L$$

$$= A_i^o I_b Z_L$$

$$A_v = \frac{A_i^o Z_L}{Z_i^o}$$

Output admittance (y_o):

Ratio of output voltage to output current when $V_s = 0$ and Z_L is 0Ω

$$I_c = h_{fe} I_b + h_{oe} V_C$$

divide with V_C

$$y_o = \frac{I_c}{V_C} = h_{fe} \frac{I_b}{V_C} + h_{oe} \quad \text{---(1)}$$

when $V_s = 0$


$$I_b R_S + h_{ie} I_b + h_{re} V_C = 0$$

$$\frac{I_b}{V_C} = -\frac{h_{re}}{R_S + h_{ie}} \quad \text{---(2)}$$

Sub (2) in (1)

$$y_o = h_{oe} - \frac{h_{re} h_{fe}}{R_S + h_{ie}}$$

Analysis of CB Amplifier

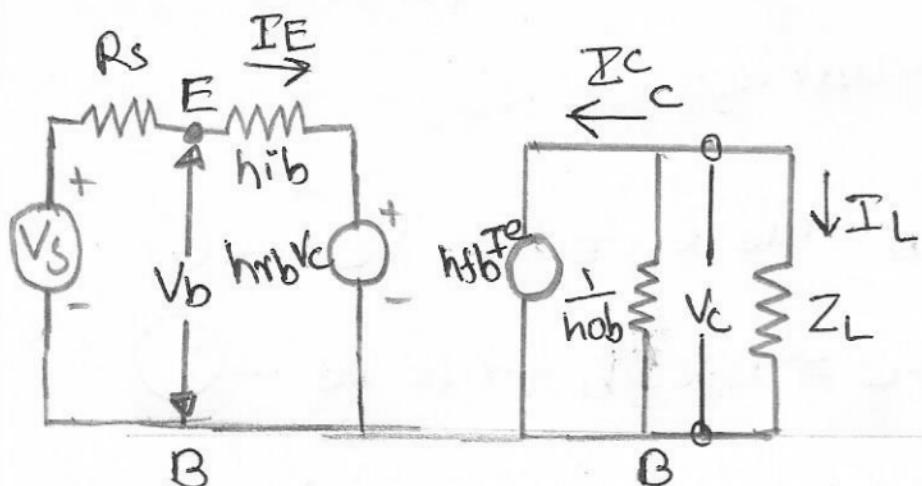

In CB configuration

V_e , I_c are dependent variables

I_e , V_c are independent variables

$$V_e = h_{fb} I_e + h_{rb} V_c \quad \text{--- (1)}$$

$$I_c = h_{fb} I_e + h_{ob} V_c \quad \text{--- (2)}$$

Current gain (A_i^o) :

$$A_i^o = \frac{I_L}{I_e} = \frac{-I_c}{I_e}$$

$$V_c = I_L Z_L = -I_c Z_L \quad \text{--- (3)}$$

Sub eq(3) in eq(2)

$$I_c (1 + h_{ob} Z_L) = h_{fb} I_e$$

$$A_i^o = \frac{-h_{fb}}{1 + h_{ob} Z_L}$$

Input impedance :

$$Z_i^o = \frac{V_e}{I_e}$$

$$V_e = h_{fb} I_e + h_{rb} V_c$$

$$V_c = Z_L Z_L = -Z_C Z_L$$

$$A_i = \frac{Z_L}{Z_e} = -\frac{Z_C}{Z_e}$$

$$V_C = A_i Z_e Z_L$$

$$V_e = h_{ib} Z_e + h_{rb} A_i Z_e Z_L$$

divide with Z_e

$$Z_i^o = h_{ib} + h_{rb} A_i Z_L$$

$$Z_i^o = h_{ib} - \frac{h_{fb} h_{rb} Z_L}{1 + h_{ob} Z_L}$$

$$Z_i^o = h_{ib} - \frac{h_{fb} h_{rb}}{Z_L \left[\frac{1}{Z_L} + h_{ob} \right]}$$

$$Z_i^o = h_{ib} - \frac{h_{fb} h_{rb}}{Y_L + h_{ob}}$$

Voltage gain: (A_v)

$$A_v = V_C / V_e$$

$V_e \rightarrow$ Input Voltage

$V_C \rightarrow$ Output Voltage

$$V_e = I_e Z_i^o$$

$$V_C = Z_L Z_L = -Z_C Z_L$$

$$A_i = \frac{Z_L}{I_e} = -\frac{Z_C}{I_e}$$

$$V_C = A_i I_e Z_L$$

$$A_v = \frac{V_C}{V_e} = \frac{A_i Z_L}{Z_i^o}$$

Output admittance

Ratio of output voltage to output current when

$$V_S = 0 \text{ & } Z_L \text{ is } \infty$$

$$V_E = h_{ib} I_E + h_{rb} V_C \quad \text{--- (1)}$$

$$Z_C = h_{fb} Z_E + h_{ob} V_C \quad \text{--- (2)}$$

divide Eq(2) with "V_C"

$$Y_0 = \frac{Z_C}{V_C} = h_{fb} \frac{Z_E}{V_C} + h_{ob} \quad \text{--- (3)}$$

if $V_S = 0$ then

$$I_E R_S + h_{ib} Z_E + h_{rb} V_C = 0$$


divide with V_C

$$\frac{Z_E}{V_C} = \frac{-h_{rb}}{R_S + h_{ib}} \quad \text{--- (4)}$$

sub (4) in (3)

$$Y_0 = h_{ob} - \frac{h_{fb} h_{rb}}{R_S + h_{ib}}$$

Analysis of CC Amplifier

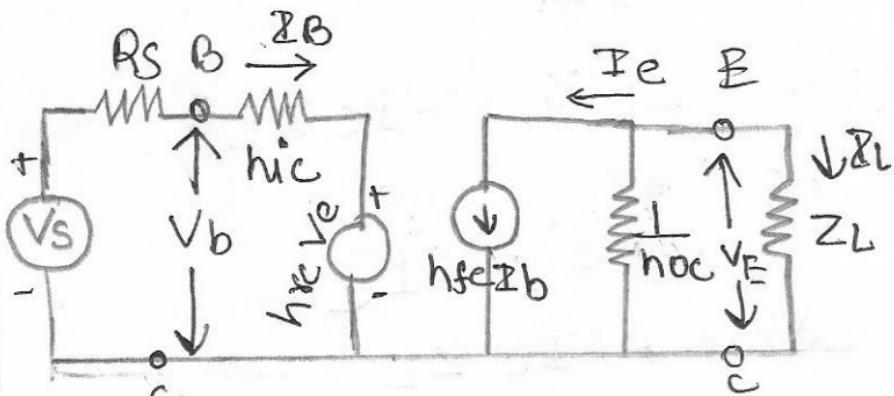

V_b , I_e are dependent variables
 R_b , V_e are independent variables

$$V_b = h_{ic} I_b + h_{oc} V_e \quad \textcircled{1}$$

$$\mathcal{E}_e = h_{fc} I_b + h_{oc} V_e \quad \textcircled{2}$$

Current gain (A_i)

$$V_e = \mathcal{E}_L Z_L = -\mathcal{E}_e Z_L \quad \textcircled{3}$$

Sub \textcircled{3} in \textcircled{1}

$$I_e(1+h_{oc} Z_L) = h_{fc} Z_b$$

$$A_i = \frac{-h_{fc}}{1+h_{oc} Z_L}$$

Input Impedance (Z_i) :

$$V_e = \mathcal{E}_L Z_L = -\mathcal{E}_e Z_L$$

$$A_i = \frac{I_L}{I_b} = \frac{-I_e}{I_b}$$

$$V_e = A_i I_b Z_L$$

$$V_b = h_{ic} I_b + h_{oc} A_i \mathcal{E}_b Z_L$$

divide with I_b

$$Z_i = h_{ic} + h_{oc} A_i Z_L$$

$$Z_i = h_{ic} - \frac{h_{fc} h_{oc} Z_L}{1+h_{oc} Z_L}$$

$$Z_i = h_{ic} - \frac{h_{fc} h_{rc}}{(Y_L + h_{oc})}$$

Voltage gain (Av) :

$$Av = \frac{V_e}{V_b}$$

$$V_b = Z_b Z_i$$

$$V_e = I_L Z_L = -\frac{I_e}{Z_b} Z_L$$

$$A_i = \frac{I_L}{I_b} = -\frac{I_e}{Z_b}$$

$$V_e = A_i Z_b Z_L$$

$$Av = \frac{A_i Z_L}{Z_i}$$

Output Admittance :

Ratio of output voltage to output current when $V_s = 0$ and $Z_L = \infty$

$$I_e = h_{fc} I_b + h_{oc} V_e \quad \text{--- (1)}$$

divide with V_e

$$Y_o = \frac{I_e}{V_e} = h_{fc} \frac{I_b}{V_e} + h_{oc}$$

if $V_s = 0$

$$R_b R_s + h_{ic} Z_b + h_{rc} V_e = 0$$


divide with V_e

$$\frac{E_b}{V_c} = \frac{-h_{rc}}{R_s + h_{ic}}$$

$$V_o = h_{oc} - \frac{h_{fc} h_{rc}}{R_s + h_{ic}}$$

①

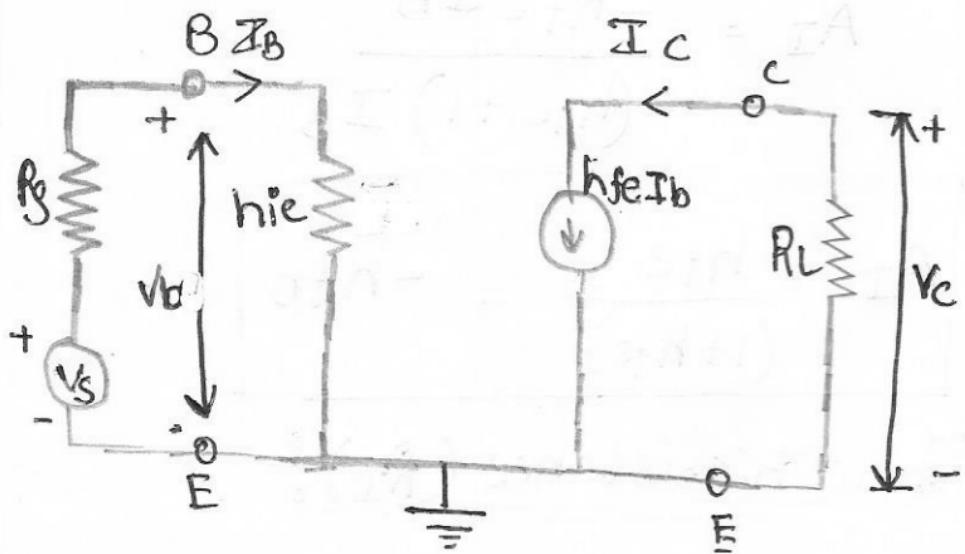Analysis of cE amplifier using approximate model :



Current gain (A_I) :

$$A_I = \frac{Z_C}{Z_B} = \frac{-I_C}{I_B} \quad \text{--- (1)}$$

$$\boxed{I_C = h_{FE} I_B} \quad \text{in eq (1)}$$

$$A_I = \frac{-h_{FE} I_B}{I_B}$$

$$\boxed{A_I = -h_{FE}}$$

Input Impedance (R_I)

$$R_I = \frac{V_B}{I_B}$$

$$V_B = h_{IE} Z_B$$

$$R_I = \frac{h_{IE} Z_B}{Z_B}$$

$$\boxed{R_I = h_{IE}}$$

Voltage gain (A_v) : ②

$$A_v = \frac{V_c}{V_b} = \frac{I_c R_L}{I_b h_{ie}}$$

$$\Rightarrow -\frac{I_L R_L}{Z_b h_{ie}}$$

$$\Rightarrow -\frac{h_{fe} I_b R_L}{Z_b h_{ie}}$$

$$A_v = \boxed{-\frac{h_{fe} R_L}{h_{ie}}}$$

Output admittance (R_o) :

$$R_o = 1/y_o \quad y_o = \frac{-I_L}{V_c}$$

$$= \frac{V_c}{-I_c} \quad I_L = -I_C$$

$$Z_b = 0, I_C = 0$$

$$R_o = \infty$$

{ Output port is open circuited }
 $Z_C = 0$

Characteristics :


- i) It has medium input impedance
- ii) High current gain (1K-2)
- iii) High Voltage gain
- iv) Moderate output impedance.
- v) Used for voltage amplification at audio frequency range
- vi) The phase shift is around 180° between input and output voltages

③

Applications :

Of the 3 configurations CE amplifier alone is capable of providing both voltage gain and power gain. Further the input resistance R_I and output resistance are moderately high. Hence CE amplifier is widely used for amplification.

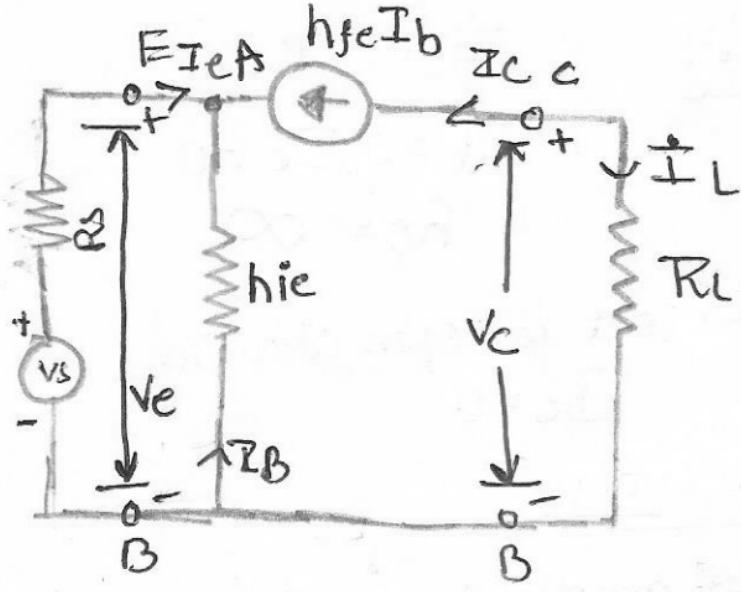Analysis of CB amplifier using approximate model :



The above figure shows the equivalent circuit of CB amplifier using approximate model, with the base grounded.

Current gain (A_2) :

$$A_2 = \frac{I_C}{I_E} = -\frac{I_C}{I_E}$$

KVL at node "A"

$$I_E + h_{FE} Z_B + I_B = 0$$

$$I_C = -h_{FE} I_B - I_B$$

(4)

$$\frac{I_C}{I_B} = -(h_{FE} + 1) \quad \{ \text{current gain} < 1 \}$$

$$A_I = \frac{-h_{FE} I_B}{-(h_{FE} + 1) I_B}$$

$$A_I = \frac{h_{FE}}{(1+h_{FE})} = -h_{FB}$$

Input Resistance (R_I) :

$$R_I = \frac{V_e}{I_e}$$

$$V_e = -h_{IE} I_B \quad \left. \begin{array}{l} \{ \text{-indefn} \\ i_c = -(1+h_{FE}) I_B \end{array} \right\}$$

$$R_I = \frac{h_{IE}}{(1+h_{FE})}$$

$$R_I = h_{IB}$$

Voltage gain :

$$A_V = \frac{V_C}{V_e}$$

(*) voltage gain is
high
*) no phase shift

$$V_C = I_L R_L = -I_C R_L$$

$$V_e = -I_B h_{IE}, \quad I_C = h_{FE} I_B$$

$$A_V = \frac{-h_{FE} I_B R_L}{-I_B h_{IE}}$$

$$A_V = \frac{h_{FE} R_L}{h_{IE}}$$

(A₂, A_V, R_I don't differ from exact values by more than 10%) (5)

Output Impedance :

$$R_o = \frac{V_c}{I_c} \text{ with } R_{L}=0, V_s=0$$

with $V_s = 0, I_e = 0 \& I_b = 0$
hence $I_b = 0$

*) Therefore $R_o = \infty$ using approximate model

CB characteristic :

- *) It's used as amplifier at high frequency.
- *) Current gain less than 1
- *) Input impedance low
- *) Voltage gain high
- *) O/P impedance high.
- *) There is no phase shift

Applications :


The CB amplifier is used for amplification

Used for:

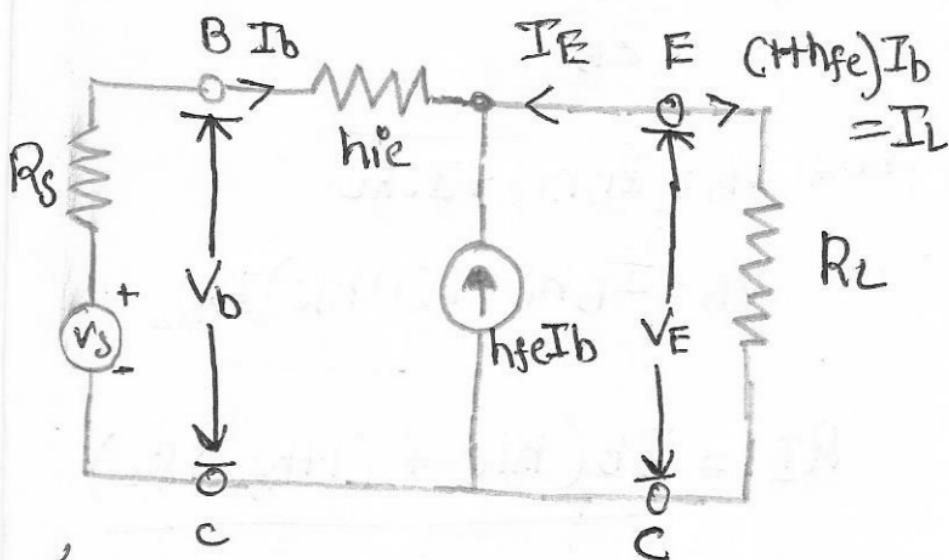- i) Matching a low impedance source
- ii) as a non-inverting amplifier with voltage-gain exceeding unity
- iii) for driving a high impedance load

6

Approximate hybrid model of CC & common amplifier)



The above figure shows the simplified h-parameter equivalent of a common collector amplifier. In this circuit the collector is grounded and load resistance R_L is connected between emitter & the ground.

It's consists h_{ie} - Input impedance
 h_{fe} - forward current gain
current gain (A_I):

$$A_I = \frac{I_L}{I_B} = \frac{-I_E}{I_B}$$

$$= \frac{(1+h_{fe}) I_B}{I_B}$$

{apply KCL at node "A".}

$$Z_L = -Z_C = h_{fe} I_B + I_B$$

$$I_L = (h_{fe} + 1) I_B$$

$$A_2 = 1+h_{fe}$$

7

Input Resistance (R_I) :

$$R_I = \frac{V_B}{I_B}$$

where $V_B = I_B h_{ie} + I_L R_L$

$$V_B = I_B h_{ie} + (1+h_{fe}) I_B R_L$$

$$R_I = \frac{I_B (h_{ie} + (1+h_{fe}) R_L)}{I_B}$$

$$R_I = h_{ie} + (1+h_{fe}) R_L$$

Voltage gain (A_v) :

$$A_v = \frac{V_E}{V_B} = \frac{(1+h_{fe}) I_B R_L}{[h_{ie} I_B + (1+h_{fe}) I_B R_L]}$$

$$\Rightarrow \frac{1+h_{fe}}{h_{ie} + (1+h_{fe}) R_L}$$

$$= 1 - \frac{h_{ie}}{h_{ie} + (1+h_{fe}) R_L}$$

$$A_v = 1 - \frac{h_{ie}}{R_I}$$

Output admittance (R_O) :

$$R_O = 1/y_0$$

$$V_o = i(t) \cdot R_L$$

$$y_0 = \frac{\text{Short ckt current at O/p}}{\text{Open ckt Voltage at O/p}}$$

$$y_0 = \frac{(1+hfe) I_b}{V_S}$$

$$I_b = \frac{V_S}{R_S + h_{ie}}$$

$$y_0 = \frac{(1+hfe) (V_S / R_S + h_{ie})}{V_S}$$

$$x_0 = \frac{1+hfe}{R_S + h_{ie}}$$


$$R_O = 1/y_0 = \frac{R_S + h_{ie}}{1+hfe}$$

Characteristics of CC:


- * It offers high input impedance
- * It offers low output impedance
- * Current gain A_I is high
- * $A_V \leq 1$
- * Not suitable for voltage amplification
- * It is suitable for impedance matching purpose such it can be used as a buffer between a high impedance source and low impedance load. It doesn't introduce phase shift between i/p, o/p signals.

Analysis of CE Amplifier

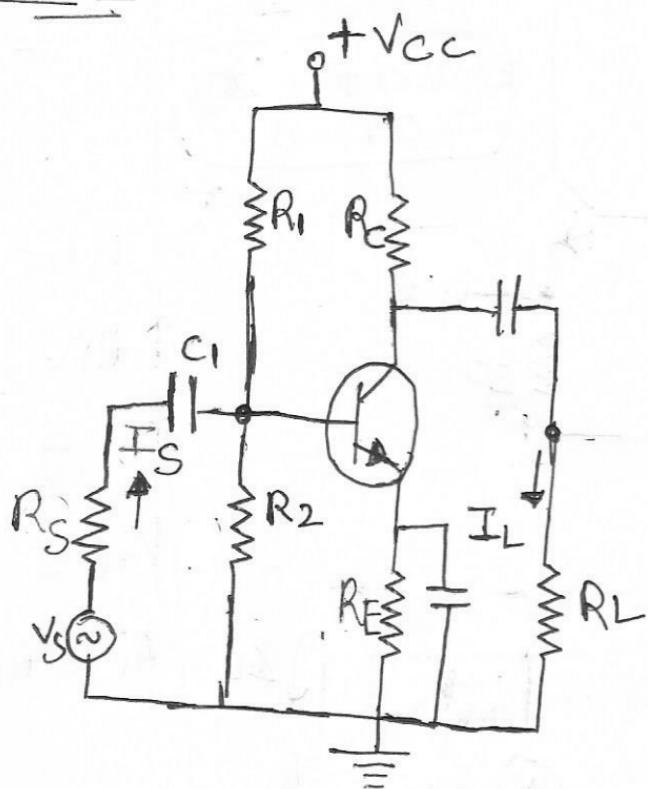
Analysis of CE amplifier using h-parameter model :-



Common Emitter Amplifier

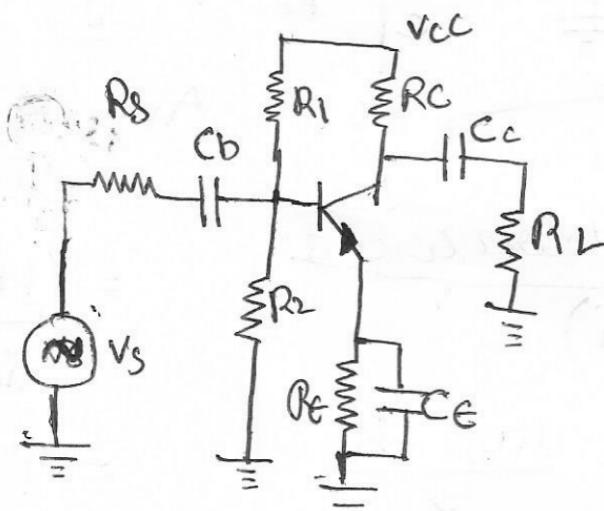


AC Equivalent circuit :

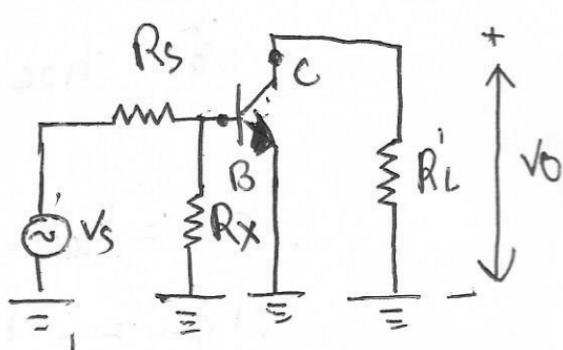

$$R_x = R_1 \parallel R_2$$

$$R_{L'} = R_C \parallel R_L$$

Replace BJT by its h-model :

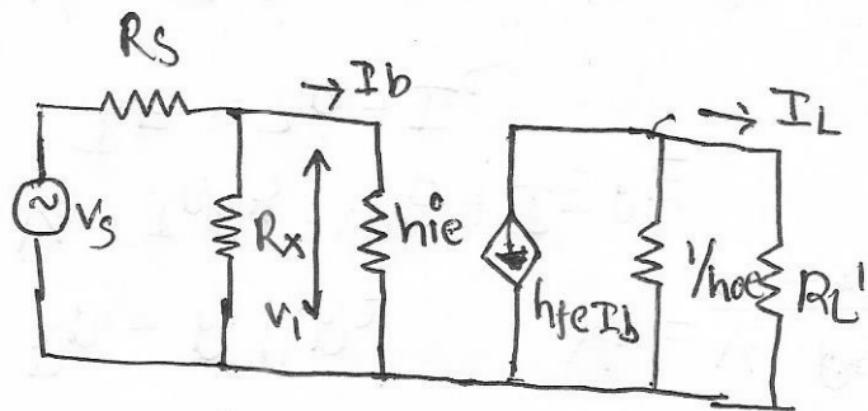

Current gain

$$A_i = \frac{I_L}{I_b} = \frac{-h_{fe}}{1 + h_{oe} R_L'}$$

If h_{oe} is negligible

then $A_i \approx -h_{fe}$ current gain is high

Input resistance

$$R_i = \frac{V_i}{I_b} = \frac{Z_b \times h_{ie}}{Z_b}$$

$R_i = h_{ie}$ R_i is high

Voltage gain : $\gamma_{hoe} \| R_i' = R_L''$

$$A_v = \frac{V_o}{V_i} = \frac{-h_{fe} Z_b R_L''}{I_b \cdot h_{ie}}$$

$A_v = \frac{-h_{fe} R_L''}{h_{ie}}$ Voltage gain is high


Output Resistance :

$$\frac{1}{R_o} = h_{oe} - \frac{h_{fe} h_{re}}{R_s' + h_{ie}}$$



If h_{re} is negligible

$$R_o = \frac{1}{h_{oe}}$$

R_o is very high

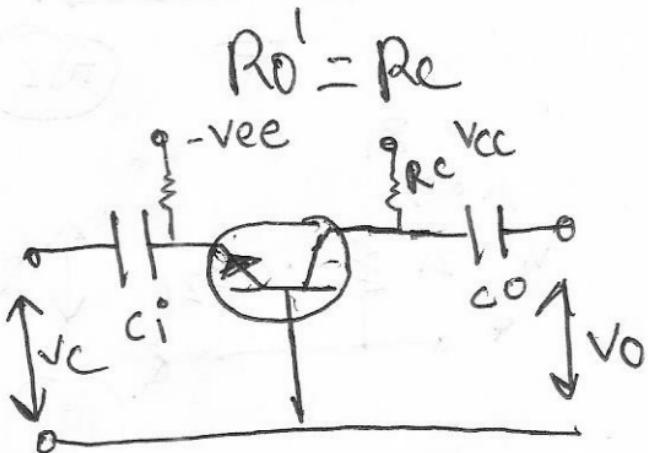


CB amplifier

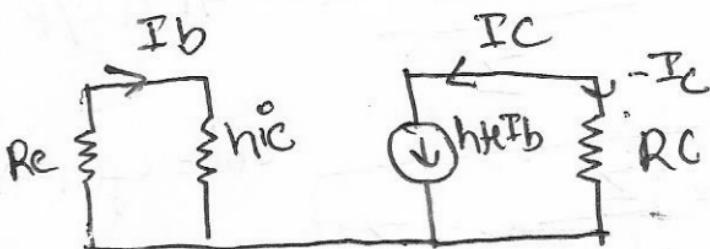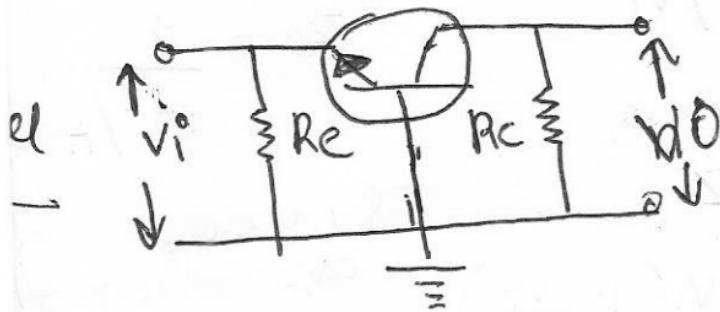

approximate model ~~using~~ of
CE amplifier

CB amplifier using approximate model

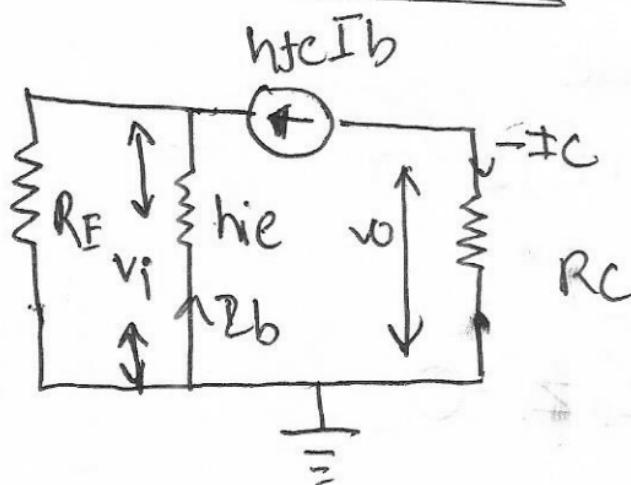



$$R_T = \frac{V_B}{Z_b} = \frac{-hie Z_b}{-(1+hfe) I_b}$$

$$A_Z = -\frac{Z_C}{Z_b} = \frac{-hfe I_b}{-(1+hfe) I_b}$$

$$A_Z = -hfe / (1+hfe)$$

$$A_V = \frac{V_o}{V_i} = \frac{-hfe Z_b R_C}{-hie I_b}$$

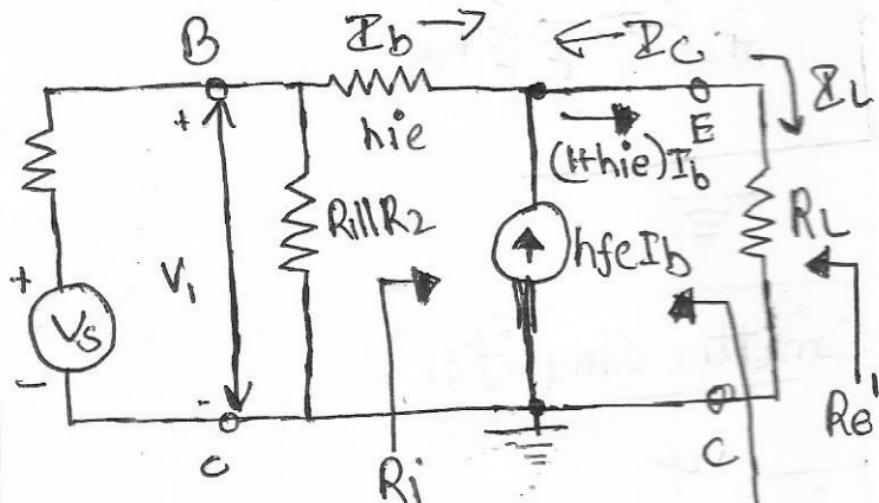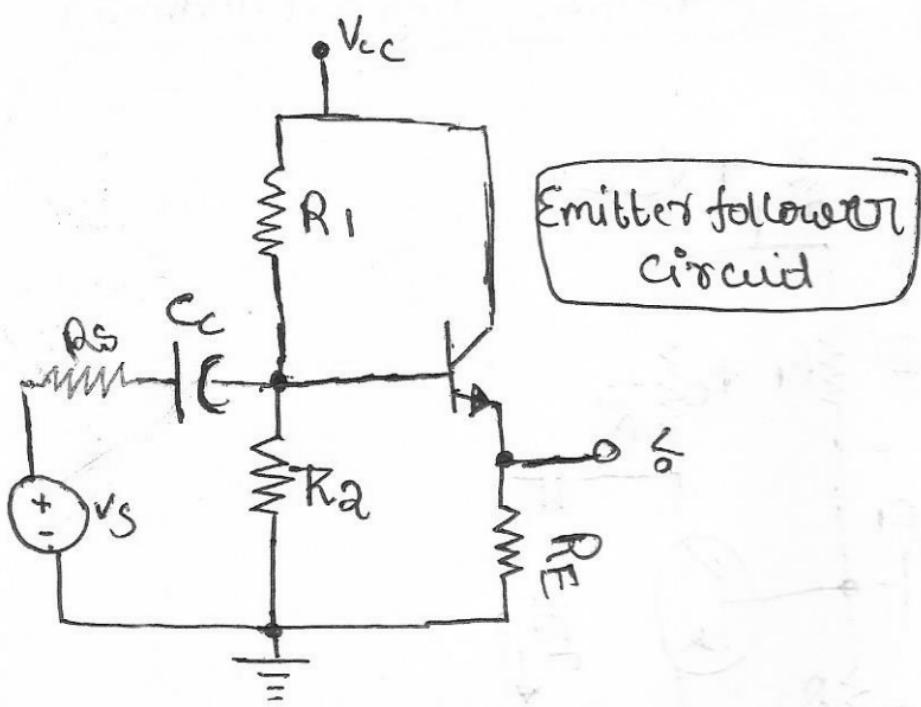Emitter follower analysis is using approximate model :



Simplified hybrid model
for emitter follower circuit

Current Gain : (A_i)

$$A_i = \frac{Z_L}{I_b} = \frac{Z_E}{Z_b} = \frac{(1+h_f)e}{Z_b}$$

$Z_E = (1+h_f)e I_b$

$$A_i = 1 + h_f e$$

Input Resistance (R_i) :

$$R_i = \frac{V_b}{I_b} =$$

$$= \frac{I_b h_{ie} + I_b (1+h_{fe}) R_L}{I_b}$$

[canceling " I_b " as they are common]

$$R_i = h_{ie} + (1+h_{fe}) R_L$$

$$R_i = 1100 \Omega + 101 * (2000 \Omega)$$

$$= 203.1 K\Omega$$

$$A_i = 1+100 = 101$$

$$R_i' = R_i \| R_b = 203.1 K\Omega \| 25 K\Omega$$

$$= 22.25 K\Omega$$

$$R_b = R_1 \| R_2 = 25 K\Omega$$

Voltage gain (A_v) :

$$A_v = \frac{V_o}{V_i} = \frac{A_i R_L}{R_i}$$

$$= \frac{(1+h_{fe}) R_L}{h_{ie} + (1+h_{fe}) R_L} = \frac{R_i - h_{ie}}{R_i}$$

$$= 1 - \frac{h_{ie}}{R_i} \quad \left\{ A_v = 1 - \frac{h_{ie}}{R_i} \right\}$$

$$\text{Output Resistance (R_o) : } 1 - \left(\frac{1100}{203100} \right) = 0.99$$

$$Y_o = h_{oc} - \frac{h_{fc} h_{rc}}{R_s + h_{ie}}$$

$$h_{oc} = h_{oc} = 25 \times 10^{-6} A/V$$

$$h_{fc} = 1+h_{fe}$$

$$h_{rc} = 1$$

$$h_{ic} = h_{ie}$$

$$R_s' = R_g \parallel R_1 \parallel R_2$$

$$= 500\Omega \parallel 2k\Omega$$

$$= 0.9k\Omega$$

$$y_0 = -h_{fc}$$

$$R_s' + h_{ic}$$

$$R_o = 1/y_0 = \frac{R_s' + h_{ie}}{1+h_{fe}}$$

$$= \frac{900 + 1100}{101}$$

$$= 19.80\Omega$$

$$R_o' = R_o \parallel R_L$$

* * *

Q) In Emitter follower

$$R_s = 500\Omega,$$

$$R_1 = R_2 = 2k\Omega$$

$$h_{fe} = 100, h_{ic} = 1.01k\Omega$$

determine R_i , R_o , A_i , A_v

Single stage CE Amplifier

In CE configuration the operating point is the mid-point of DC load line. Biasing stabilizes the operating point in the active region due to change in temperature, change in β and change in V_{BE} .

Biasing ensure emitter base junction forward biased and collector base junction reverse biased.

Transistor Biasing Techniques

- i) Fixed bias
- ii) Collector to Base bias
- iii) Self bias

Fixed Bias :



In CE configuration

$$I_c = \beta I_B + (1+\beta) I_{CO}$$

Stability factor

$$S = \frac{dI_c}{dI_{CO}}$$

$$S = \frac{1+\beta}{1-\beta} \frac{\frac{dI_B}{dI_c}}{\frac{dI_B}{dI_c}}$$


In fixed bias

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$\frac{dI_B}{dI_c} = 0$$

fixed bias has
poor stabilization
technique but
it's simple

Collector to Base Bias :

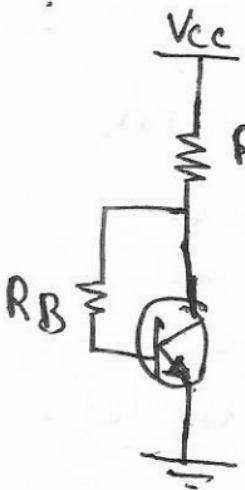


The feedback Resistor
is between collector
and base cause
negative feedback

$$S = \frac{1+\beta}{1 + \frac{\beta R_C}{R_C + R_B}}$$

$$R_C \gg R_B$$

Stability factor is 1

Common Emitter Amplifier

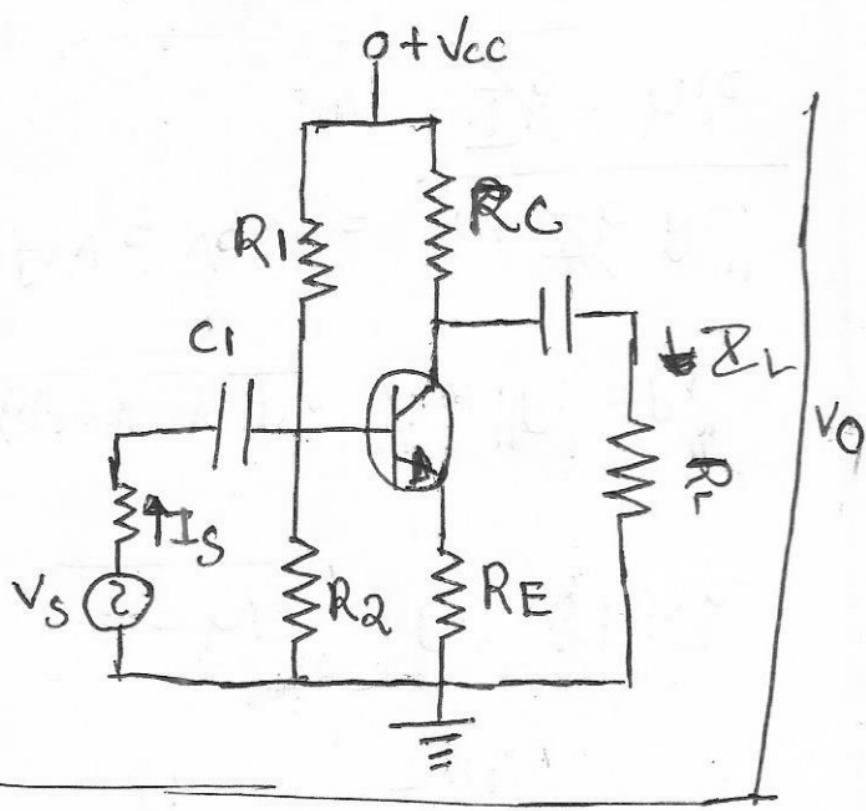

In self bias CE amplifier the voltage drop across R_2 provides emitter base junction forward bias.

The Voltage drop across R_C provides collector base junction Reverse bias.

" R_E " provides stabilization.

The capacitor C_1, C_2 couples input & output signal.

V_o is output observed across load Resistor R_L .

Stabilization factor(s) = 1

$$R_B = R_1 \parallel R_2 \quad V_a = \frac{V_{cc} R_2}{R_1 + R_2}$$

$$Z_B = Z_B + I_C$$

$$V_a = Z_B R_B + V_{BE} + (Z_B + Z_C) R_E$$

differentiate the above equation
with respect to \mathfrak{Z}_C

$$\frac{dI_B}{d\mathfrak{Z}_C} = \frac{-R_E}{R_E + R_B}$$

$$S = \frac{1+\beta}{1 + \frac{\beta R_E}{R_E + R_B}}$$

R_E is stabilizing resistor

$$\mathfrak{Z}_C = \beta \mathfrak{Z}_B + (1+\beta) I_{C0}$$

$$V_2 = \mathfrak{Z}_B R_B + V_{BE} + I_E R_F$$

$$I_B = (V_2 - V_{BE} - \mathfrak{Z}_E R_E) / R_B$$

As temperature increases

\mathfrak{Z}_C increases, \mathfrak{Z}_E also increases
 \mathfrak{Z}_B decreases now \mathfrak{Z}_C becomes
constant. So operating point
is stable.

here as I_C increases lead to
decrease in \mathfrak{Z}_B due to
voltage drop across R_F

$$V_{CC} = I_C R_C + V_{CE} + I_E R_E$$

$$I_C \approx I_E$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

Stability factor

$$S = \frac{(1+\beta)(R_B + R_E)}{R_B + R_E(1+\beta)}$$


$$R_E = R_1 // R_2$$

$$S = \frac{(1+\beta)(1 + \frac{R_B}{R_E})}{\frac{R_B + (1+\beta)}{R_E}}$$

$$S = \frac{1+\beta}{1+\beta} = 1$$

Frequency Response

$$A_v = A_v(f) \angle \phi(f)$$

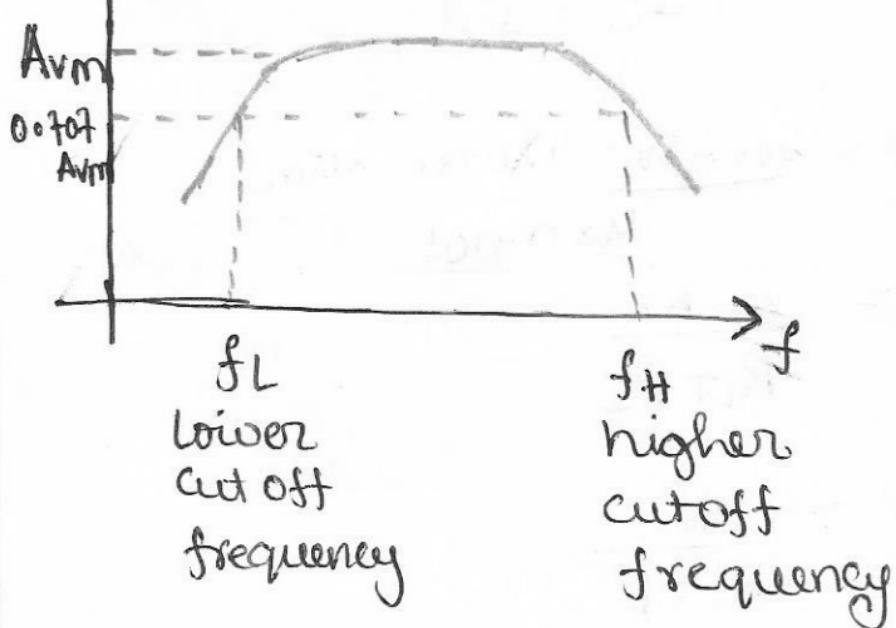

The drop of Voltage gain is due to:

- 1) Increasing reactance of capacitors at low frequency

Design of Single Stage CE amplifier:

R_C , β , V_{CC} , V_{CE} ,

$$Z_C = \beta I_B \quad S, \beta_{\text{core}}$$

$$Z_B = Z_C / \beta \quad \text{Known}^{\circ}$$

$$V_{CC} - V_{CE} - I_C R_E$$

$$\underline{\underline{\text{Given } I_C^{\circ}}}$$

$$R_C = \frac{V_{CC} - V_{CE} - V_E}{I_C}$$

$$V_E = I_E R_E$$

$$Z_E = I_B + I_C$$

$$R_E = \frac{V_{CC} - V_{CE} - I_C R_C}{I_C + I_B}$$

$$V_2 = \frac{V_{CC} R_2}{R_1 + R_2}$$

$$R_B = \frac{R_1 R_2}{R_1 + R_2}$$

$$S = \frac{1 + \beta}{1 + \frac{\beta R_E}{R_E + R_B}}$$

$$\underline{\underline{S, \beta \text{ Given}}}$$

R_B from S can be found

$$V_2 = Z_B R_B + V_{BE} + I_E R_E$$

$$\frac{V_2}{V_{CC}} = \frac{R_2}{R_1 + R_2}$$

$$R_B = \frac{R_1 R_2}{R_1 + R_2}; \text{ so } R_B = \frac{R_2 V_2}{V_{CC}}$$

$$R_1 = \frac{R_B V_{CC}}{V_2}$$

$$V_{CC} - V_2 = 2R_1$$

$$V_2 = IR_2; \quad \frac{V_2}{V_{CC} - V_2} = \frac{R_2}{R_1};$$

$$R_2 = \frac{V_2 R_1}{V_{CC} - V_2}$$

To find C_E

$$X_{CE} \text{ is } \frac{R_E}{10}$$

$$X_{CE} = \frac{1}{2\pi f_i C_E}$$

$$C_E = \frac{1}{2\pi f_i X_{CE}}$$

To find C_1 :

$$X_{C1} \text{ is } R_i/10$$

$$R_i = R_1 || R_2 || h_{ie}$$

$$C_1 = \frac{1}{2\pi f_i X_{C1}}$$

To find C_2

$$X_{C2} \text{ is } R_C || R_L/10$$

$$C_2 = \frac{1}{2\pi f_i X_{C2}}$$

The frequency response of

CE Amplifier:

The voltage gain (V_o/V_i) decreases due to

- 1) X_{CE} , X_{ci} , X_{co} increases at low frequency
- 2) Parasitic capacitance effect increases at high frequency
- 3) C_E , C_C diffusion capacitance, transition capacitance exists between Emitter & base of transistor,
Collector base of transistor

Millers theorem

from fig 1

$$Z_1 = \frac{V_1 - V_2}{Z}$$

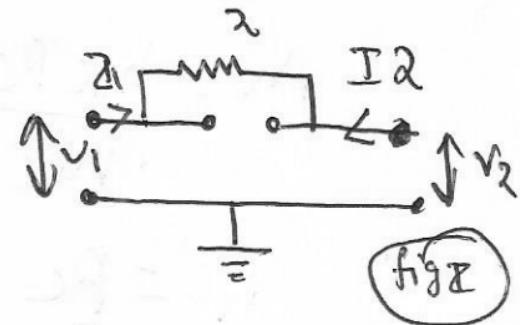


fig 1

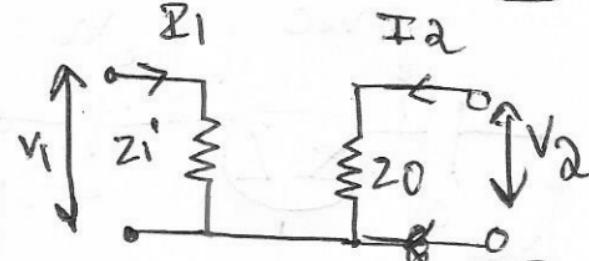


fig 2

$$I_d = \frac{V_d - V_1}{Z}$$

$$Z_1' = \frac{Z}{1-A}$$

$$A = V_d / V_1$$

$$Z_0 = \frac{Z}{1 - 1/A}$$

$$Z_1 = \frac{V_1 - V_2}{Z}$$

$$Z_1 = \frac{V_1 \left(1 - \frac{V_2}{V_1}\right)}{Z}$$

note CF
 capacitor connected
 b/w I/P & O/P

$$\boxed{\frac{V_1}{I_1} = \frac{Z}{1-A} = Z_1'}$$

$$C_{MI} = C_f(1-A)$$

$$I_d = \frac{V_2 - V_1}{Z}$$

$$C_{MO} = C_f(1 - 1/A)$$


$$I_d = \frac{V_2 \left(1 - \frac{V_1}{V_2}\right)}{Z}$$

$$\frac{V_d}{I_d} = \frac{Z}{1 - 1/A} = \frac{A \cdot Z}{A - 1}$$

$$\boxed{Z_0 = \frac{Z}{1-A}}$$

Millers theorem states that the impedance b/w input & output can be split towards i/p side impedance Z_1^* & o/p side impedance Z_0

Dual of millers theorem:

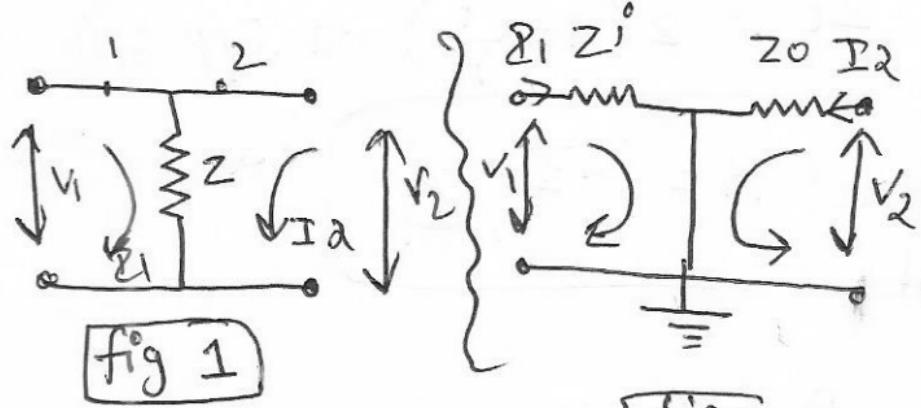

at i/p side in fig 1

$$V_1 = (I_1 + I_2) Z \quad \text{--- (1)}$$

at o/p side

$$V_2 = (I_2 + I_1) Z \quad \text{--- (2)}$$

from fig 2

$$V_1 = Z_1^* Z_i \quad \text{--- (3)}$$

$$V_2 = I_2 Z_0 \quad \text{--- (4)}$$

$$(1) = (3)$$

$$(Z_1^* + I_2) Z = Z_1^* Z_i$$

$$Z_1^* = \left(\frac{I_1 + I_2}{Z_1} \right) Z$$

$$A = -I_2/Z_1$$

$$Z_1^* = (1-A)Z$$

$$I_2 Z_0 = (I_2 + Z_1^*) Z$$

$$Z_0 = \left(\frac{I_2 + Z_1^*}{I_2} \right) Z \Rightarrow Z_0 = \left(1 - \frac{1}{A} \right) Z$$

Dual of miller's theorem states
that if an impedance Z connected
as shunt element between i/p &
o/p can be replaced by

$$Z_i = Z(1 - A) \text{ at i/p side}$$

$$Z_o = Z\left(1 - \frac{1}{A}\right) \text{ at o/p side}$$

note: $A = -I_2/Z_1$

$A \Rightarrow$ Current gain