


Unit-IIISteady state switching characteristics of devices* Diode switching times:

If device is OFF/OPEN, then it is non-conducting. If device is ON/closed, then it is conducting.

→ Diode forward recovery time:

When diode is driven from reverse biased condⁿ to forward bias condⁿ or opposite of this, then an interval of time elapses before diode recovers to its steady-state. The forward recovery transient depends on magnitude of current that drive the diode.

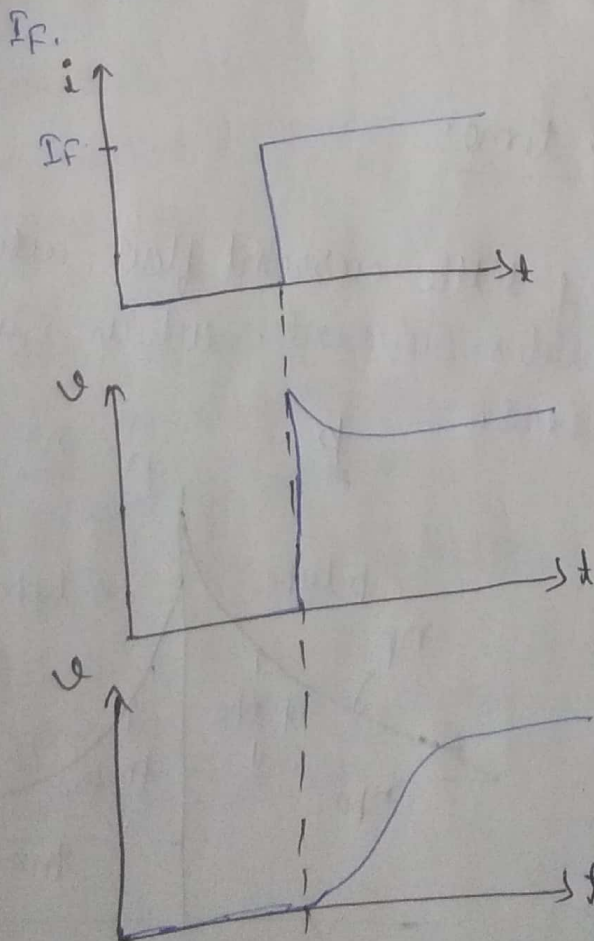The diode current is compared with step current



→ Step current as I_F

→ when current is large, overshoot occurs since in starting diode behaves as resistor.
when $i \gg$

→ when current is small.

when $i \ll$

The magnitude of overshoot increases as the magnitude of i/p current increases. At large current amplitude, the diode behaves as combination of a resistor and an inductor.


At low current the diode is represented by parallel resistor-capacitor combination.

At intermediate currents, the diode behaves as a resistor, inductor and capacitor circuit and oscillations may be produced.


For a specified rise time, the forward recovery time t_{fr} is difference b/w the time when diode voltage reaches and remains within 10% of its final value.

→ Diode reverse recovery time:

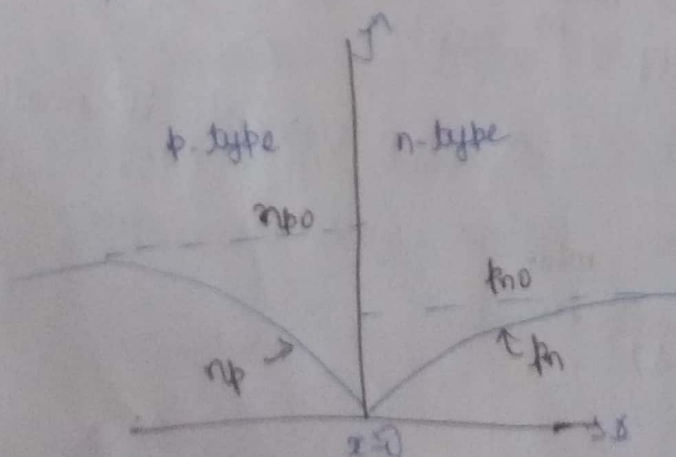In reverse bias very little current flows, which is known as reverse saturation current, which is due to minority charge carriers.



Reverse bias

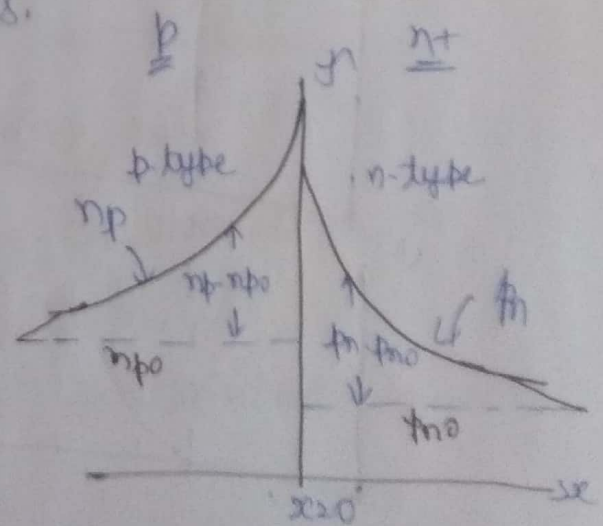


Forward bias

p_{n0} & n_{p0} is thermal equilibrium value. The carrier from j^n , the density of minority charge carriers remain unaltered.

If diode is carrying current in forward dirⁿ and external voltage is suddenly reversed then diode current will not fall immediately to steady state reverse value.

Storage & transition time:

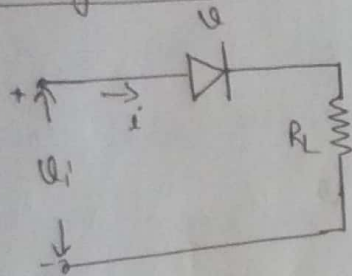

→ up to $t = t_1$, $V_i = V_F$

The current 'i' is given as,





$$i \approx \frac{V_F}{R_L} = I_F$$

→ At $t = t_1$, If voltage reverse abruptly to value $V_i = -V_R$.

So, current is given as,

$$i \approx -\frac{V_R}{R_L} = -I_R, \text{ until } t = t_2$$

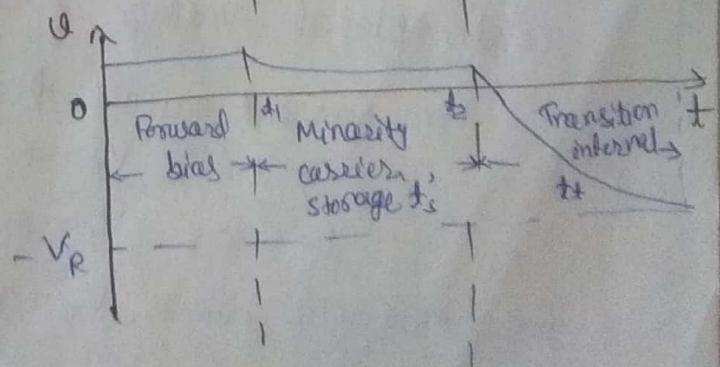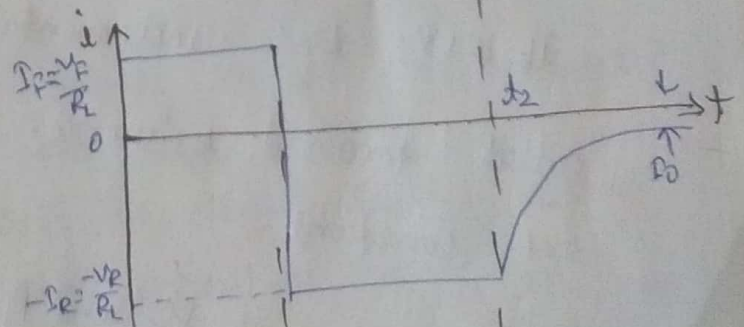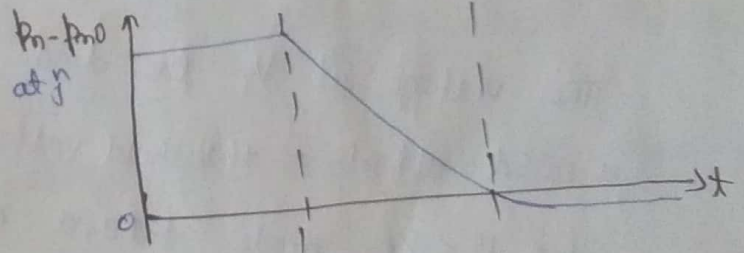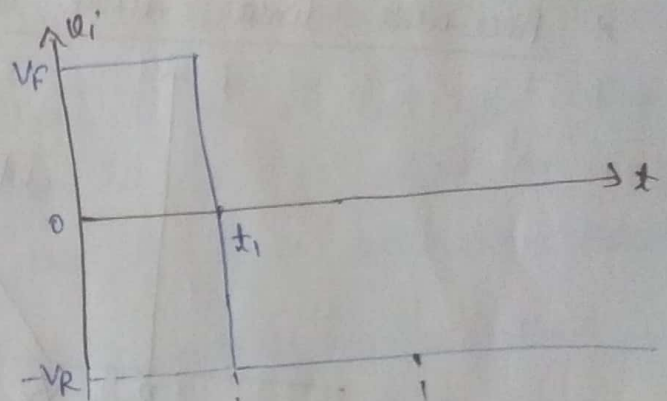→ The injected minority charge carriers drop to zero.




When excess minority carriers have been swept back across the J , the diode voltage begins to reverse and magnitude of diode current decreases.

The time interval from t_1 to t_2 , when minority charge become zero is called storage time t_s .

The time which elapses b/w t_2 and time when diode has nominally recovered is called transition time t_t .

Piece-wise linear diode characteristics:

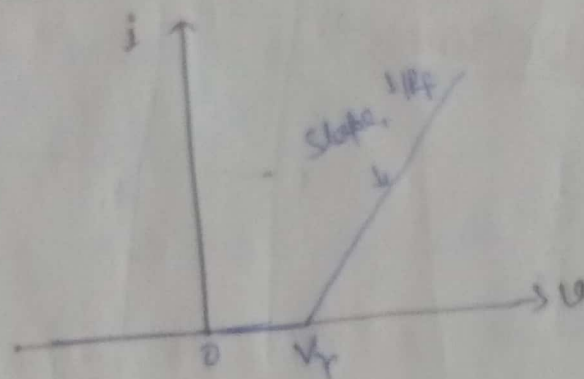

The voltage at V_f the diode behaves as close-circuit, which is called offset or threshold voltage.

For $V < V_f$, diode behaves as open ckt.

If $V > V_f$, diode incremental resistance is $r = \frac{dV}{di}$. It is called forward resistance. The static resistance $R = V/i$ is not constant.

The value of V_f and R_f depend upon type of diode and contemplated voltage & current swings.



For current swings from cut-off to 10 mA.

For Ge, $V_f = 0.2V$ & $R_f = 20\Omega$

For Si, $V_f = 0.6V$ & $R_f = 15\Omega$.

For avalanche diodes, $V_f = V_Z$ and R_f is dynamic resistance

* Transistor as Switch:

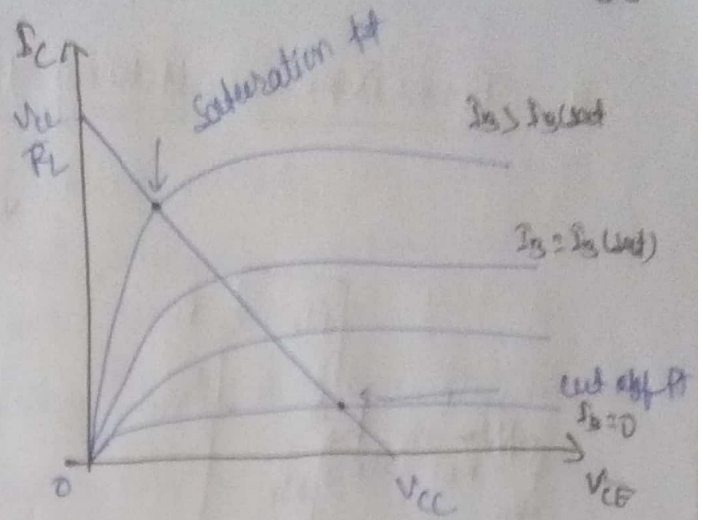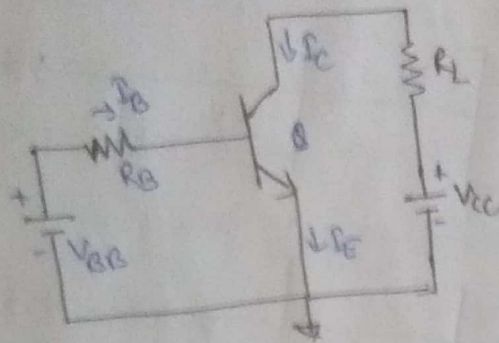


- The transistor has three regions of operation. when both $J's$ are reverse bias then it is in cut-off. when $I_P J^n$ is FB & $O_P J^n$ is FB then it is in active mode. when both $J's$ are in FB then it is in saturation mode.
- when transistor switch from cut-off to saturation and from saturation to cut-off with negligible active region, then it is operated as switch.
- during saturation J voltages are very small but operating currents are large.
- during cut-off, except leakage current all currents are zero but J voltages are large.
- when Q is saturated, it acts as closed switch from collector to emitter & when Q is cut-off, it is like an open switch from collector to emitter.

$$I_C = \frac{V_{CC} - V_{CE}}{R_L} \quad \& \quad I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$V_{CE(\text{cut-off})} = V_{CC} \quad \& \quad I_{C(\text{sat})} = V_{CC}/R_L$$

$0 < I_B < I_{B(\text{sat})} \rightarrow$ transistor operates in active region & behave as amplifiers.

* Transistor switching times:

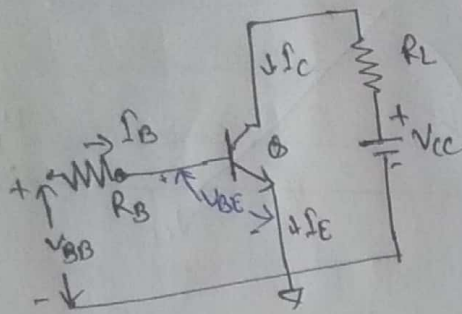

→ Transistor acts as switch, when it is either in saturation or cut off.

→ The collector current doesn't respond immediately to IP signal. So, the time required to rise to 10% of its max^m value is called as delay time 't_d'


→ Rise time 't_r' is time duration to rise from 10% to 90% of its final value.

→ Total turn on time is given as, $t_{on} = t_d + t_r$.

when IP signal returns to its initial stage, again collector current doesn't change immediately, so, the interval when I_c drops to 90% of final value is called storage time t_s.

→ when I_c falls 90% to 10% of final value is called as fall time.

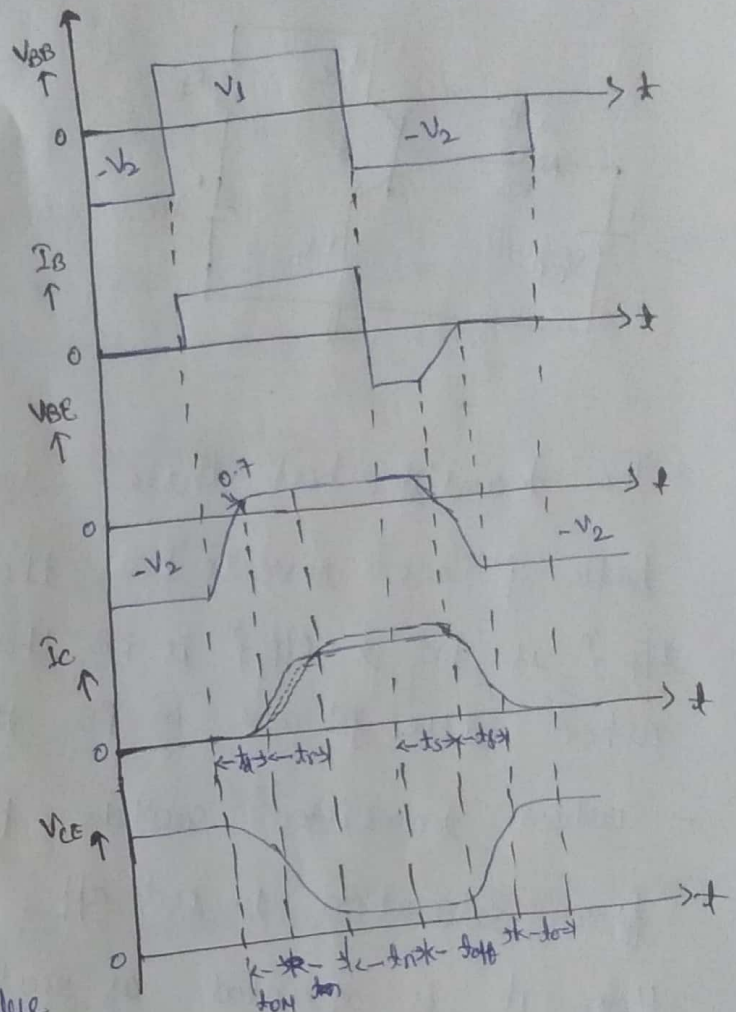So, turn off time is equal to $t_s + t_f$.



* Breakdown Voltage of a transistor:


During switching, the voltage change across collector terminal is approx V_{CC} . The max^m allowable voltage depends upon transistor characteristics and base circuitry.

The max^m reverse bias voltage before breakdown is represented by BV_{CEO} . The breakdown occurs due to avalanche multiplication of the current I_{CO} , which crosses collector J^n . So, current becomes $M I_{CO}$.

At high voltage, higher than BV_{CEO} , the multiplication factor M becomes infinite and breakdown attained. The current rises abruptly with small changes in applied voltage.

The multiplication factor is given as,
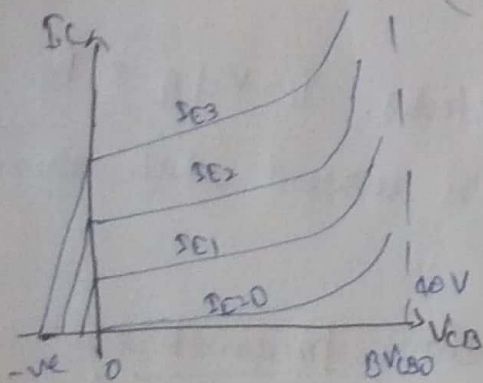
$$M = \frac{1}{1 - \left(\frac{V_{CB}}{BV_{CEO}} \right)^n}, \text{ where } n \text{ lies b/w } 2 \text{ to } 40.$$



The current I_E is given as,

$$\alpha = \frac{I_C}{I_E} \Rightarrow I_C = \alpha I_E$$


after avalanche multiplication,

$$I_C = M \alpha I_E, \text{ so } \alpha^* = M \alpha.$$

gn CE

$$h_{fe} = \alpha / (1 - \alpha) \Rightarrow h_{fe}^* = \frac{\alpha^*}{1 - \alpha^*} = \frac{M \alpha}{1 - M \alpha}.$$

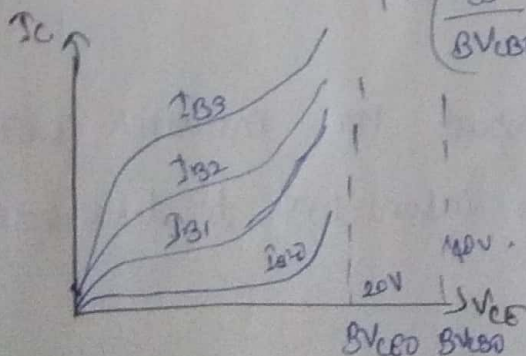For any base current, it will give large collector current for $M \alpha \approx 1$. So, $M = \frac{1}{1 - \left(\frac{V_{CB}}{BV_{CEO}} \right)^n} \approx \frac{1}{\alpha}$.



* Transistor (Switch) in saturation:

When transistor switch from saturation to cut-off, the speed of response is important. It depends upon capacitor charging, which appears shunt across the off terminals of the transistor. Capacitor is going to charge through R_L . so, R_L is kept small. In saturation current is V_{CC}/R_L . Since R_L is already small, so, V_{CC} kept small to maintain limitations.

The voltage swing is $V_{CC} - V_{CE(sat)}$. The ratio of $V_{CE(sat)}/I_C$ is called as common emitter saturation resistance, $R_{CE(sat)}$. The $V_{CE(sat)}$ depends upon operating voltage as well as type of semiconductor material.

Alloy P has lowest value, Ge transistor has $V_{CE(sat)}$ lesser than Si transistor.

h_{FE} is specified by manufacturers. $I_C > V_{CC}/R_L \times h_{FE}$ is known then $I_B > I_C/h_{FE}$, it is current which saturate the transistor.

* Temperature variation of transistor parameters:

At constant base & collector currents, V_{BE} has sensitivity in the range of -1.5 to $-2 \text{ mV}/^\circ\text{C}$. In saturation the voltage change at one p due to change in temp. is cancelled by the change in other p .

At small & moderate current h_{FE} increases with temp. At high currents, h_{FE} is insensitive to temperature.