

UNIT - IV

FILTERS.

- Filters : classification of filters
- Constant K - low pass , High pass , Band pass and Band stop filter.
- Illustrative problems.

Ideal Filter:

An ideal filter would transmit signals under the pass band frequencies without attenuation and complementary suppress the signal with attenuation band of frequencies with a sharp cut-off profile.

A filter is an electrical network that can transmit signals within a specified frequency range. This frequency range is called 'pass band' and other frequency band where the signals are suppressed is called 'attenuation band' or 'stop band'.

Properties of filter:

a, Characteristic impedance: The characteristic impedance (Z_0) of a filter matches with the circuit to which

it is connected throughout the pass band. This prevents reflection loss in the combination.

b, Pass band characteristics: The filter should have minimum attenuation in its pass band range and high attenuation in the stop band range.

c, Cut-off frequency characteristics: The frequency that separates the pass band and attenuation bands is known as cut-off frequency.

→ Applications of filters










- 1, T.V Broadcasting,
- 2, A.M detection,
- 3, Telephony,
- 4, Radio broadcasting,
- 5, Voice rejection.
- 6, audio amplifiers.

→ Classification of filters

a, Depending upon the relation between the arm impedances (i.e series arm impedance z_1 and shunt arm impedance z_2) the filters are classified as

- (i) Constant K-filter or prototype filter.
- (ii) m-derived filter.

b, identifying their frequency characteristics the filters are classified as

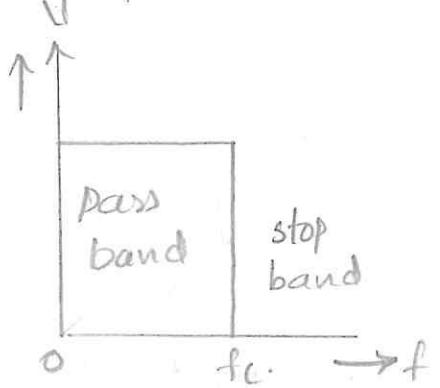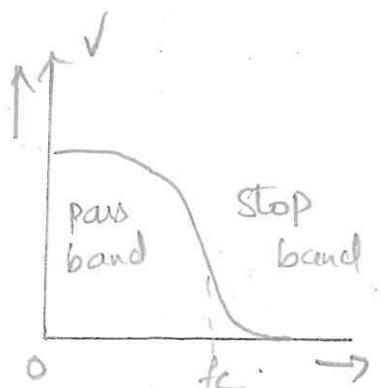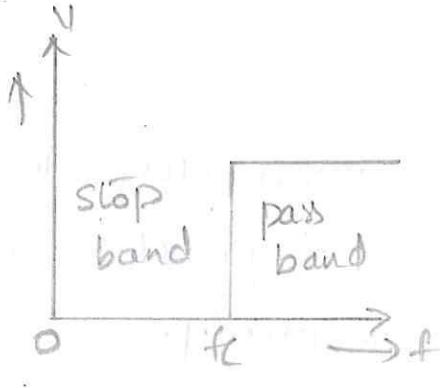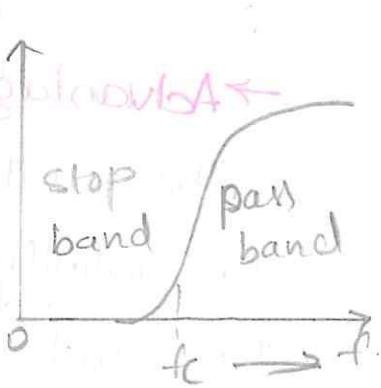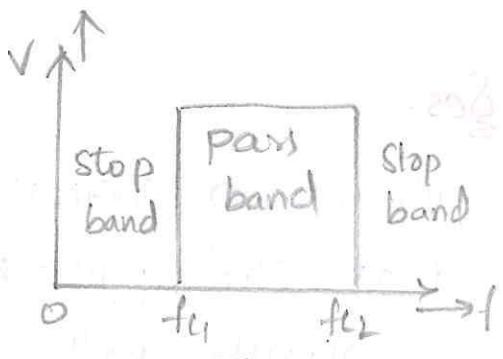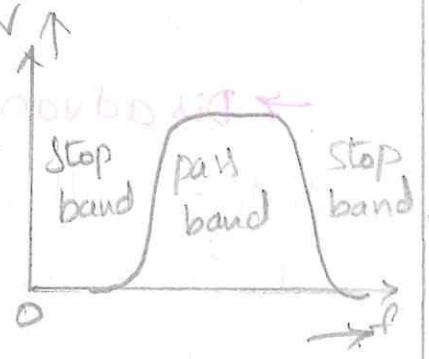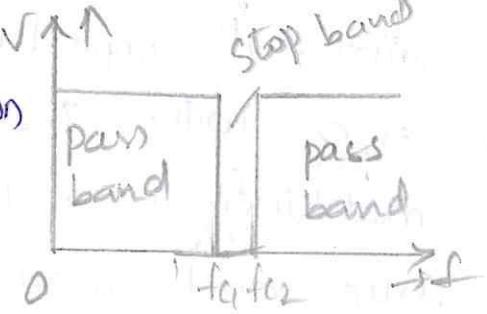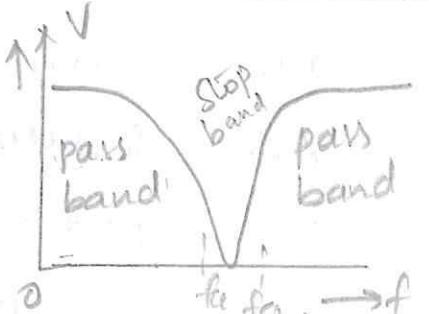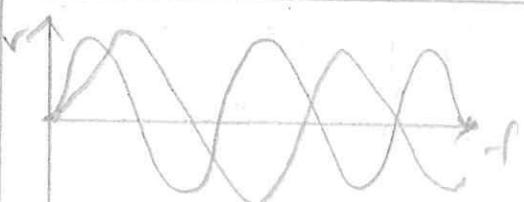Type	Ideal characteristics	Practical characteristics
1 Low pass filter		
2 High pass filter		
3 Band pass filter		
4 Band stop or Band Elimination or Notch filter		
5 All pass filter		

→ Constant K filter (prototype filter)

- In this filter, the series and shunt arm impedances (z_1 and z_2) are such that $z_1 z_2 = R_0^2 \equiv K$ (constant)

where R_0 = real number and independent of frequency.

- Any filter, where this relationship is maintained is known as constant K or prototype filter.

→ Advantages:



- The filter attenuation in stop band tends to infinity at frequencies that are distant from the cut-off frequency.
- Easy to design

→ Disadvantages:

- The filter attenuation increases very slowly and this means that the pass-band and stop-band are not always well defined.
- There are significant impedance variations with frequency even with the pass-band. If the impedance matching is required, then this can be an issue and may need to be overcome - possibly with the use of attenuators, although this reduces the signal level.

→ Constant K low pass filter (LPF)

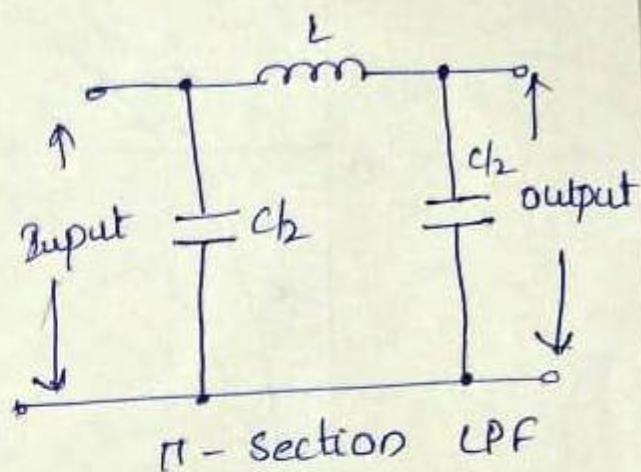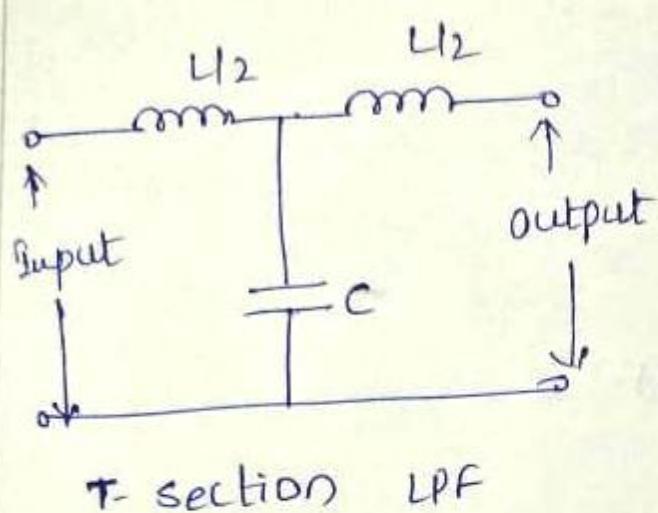→ It is the simplest type of filter which allows all frequencies, upto the specified cut-off frequency, to pass through it and attenuates all other frequencies above the cut off frequency.



T-section LPF

In T or π section total series impedance

$$Z_1 = j\omega L \quad [\because x_1 = \omega L] \quad -①$$

and total shunt impedance

$$Z_2 = \frac{1}{j\omega C} = \frac{-j}{\omega C} \quad [\because x_2 = -\frac{1}{\omega C}] \quad -②$$

Multiplying eq ① & eq ②


$$Z_1 Z_2 = j\omega L \left[-\frac{j}{\omega C} \right] = \frac{L}{C} = R_0^2 \quad -③$$

$$\text{Again } \frac{Z_1}{4Z_2} = -\frac{\omega^2 LC}{4} \quad -④$$

But from two port network

$$Z_{0T} = \sqrt{Z_1 Z_2 \left[1 + \frac{Z_1}{4Z_2} \right]} \quad -⑤$$

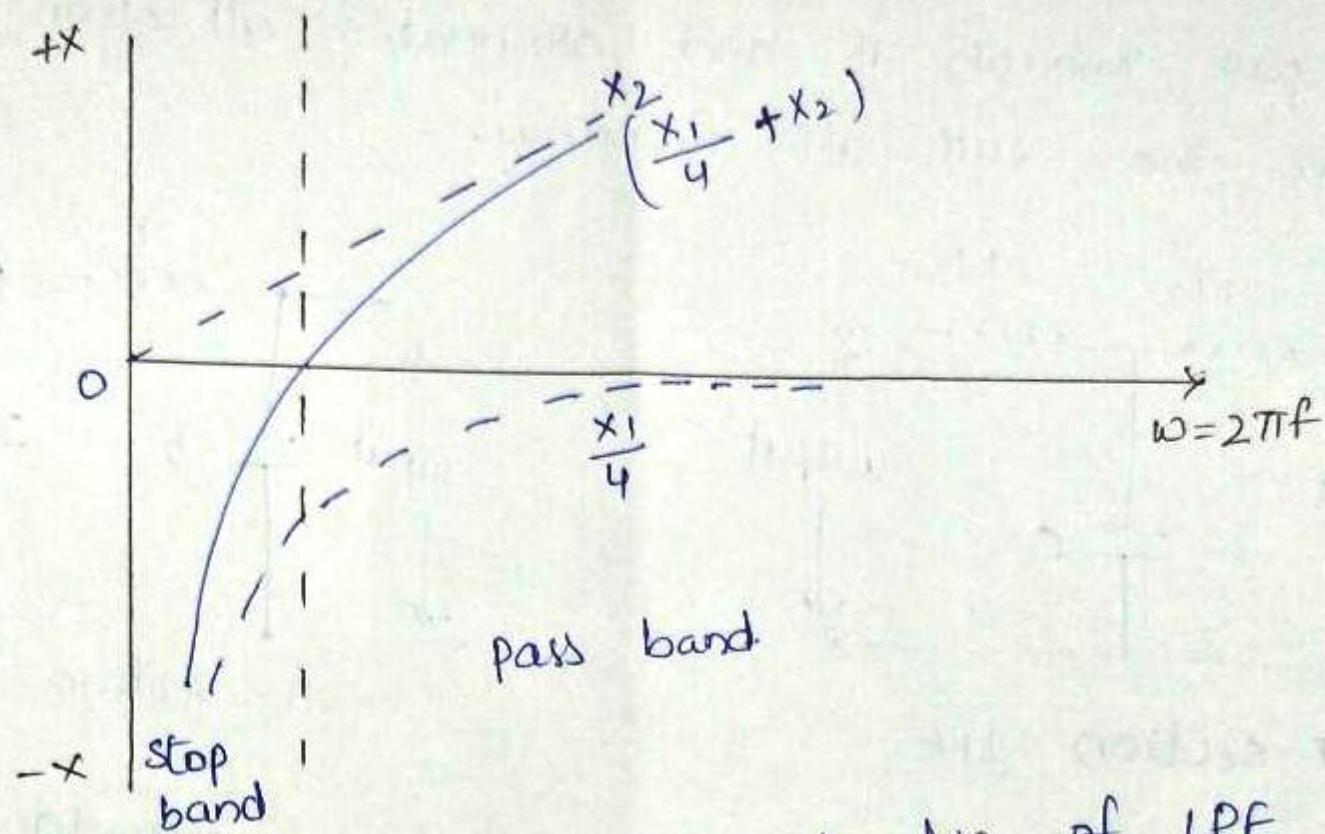where Z_{OT} = characteristic impedance of the π section of the reactance characteristic



Reactance frequency characteristic of LPF

Substituting the value of $z_1 z_2$ and $\frac{z_1}{4z_2}$
from in eq ⑤

$$Z_{OT} = \sqrt{\frac{L}{C} \left[1 + \left(-\frac{\omega^2 LC}{4} \right) \right]}$$

$$= \sqrt{\frac{L}{C}} \cdot \sqrt{1 - \frac{\omega^2 LC}{4}}$$

$$= R_0 \cdot \sqrt{1 - \frac{\omega^2 LC}{4}} = R_0 \cdot \sqrt{1 - \frac{\omega^2}{4LC}}$$

$$Z_{OT0} = R_0 \cdot \sqrt{1 - \frac{\omega^2}{\omega_c^2}} \quad \therefore \text{where } \omega_c^2 = \frac{4}{LC}$$

$$= R_0 \cdot \sqrt{1 - \left[\frac{f}{f_0} \right]^2}$$

$$Z_{OT} = \left[R_0 \sqrt{1 - \frac{\omega^2 LC}{4}} \right] \text{ is real if}$$

$$\frac{\omega^2 LC}{4} \leq 1 \quad \omega$$

imaginary if $\frac{\omega^2 LC}{4} > 1$.

Hence the low pass filter possessed a cut-off frequency given by


$$\omega_C = \frac{2}{\sqrt{LC}} \quad \text{or} \quad f_C = \frac{1}{\pi \sqrt{LC}} \quad \text{--- (1)}$$

For the Π -section, the characteristic impedance is given by

$$Z_{OT\Pi} = \frac{Z_1 Z_2}{Z_{OT}} = \frac{R_0^2}{R_0 \sqrt{1 - \left(\frac{f}{f_C}\right)^2}}$$

$$= \frac{R_0}{\sqrt{1 - \left(\frac{f}{f_C}\right)^2}}$$

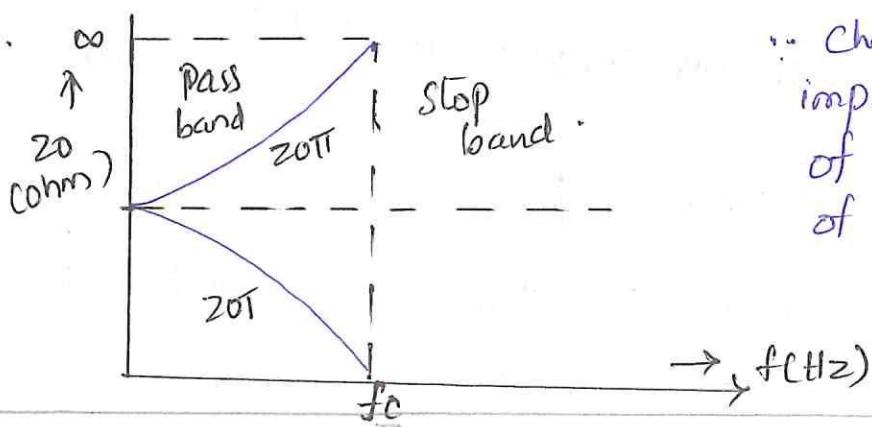In pass band $f < f_C$: $Z_{OT\Pi}$ is real & positive
 $f > f_C$: $Z_{OT\Pi}$ is imaginary



∴ characteristic impedance profile of Π & T sections of an LPF

- Attenuation (α) and phase shift (β) characteristics of LPF section

In two port network

$$\text{coh} \gamma = 1 + \frac{z_1}{2z_2} \quad \text{--- (7)}$$

where $\gamma = \alpha + j\beta$

In a filter section $z_1 = jx_1$ and $z_2 = jx_2$, where x_1 and x_2 are the reactances of the series & shunt branch.

For an LPF section $x_1 = j\omega L$ $x_2 = -\frac{j}{\omega C}$

Also, for the same LPF T section

$$\left[1 + \frac{z_1}{2z_2} \right] = 1 - \frac{\omega^2 LC}{2} \quad \left[\because \frac{z_1}{2z_2} = -\frac{\omega^2 LC}{4} \right]$$

$$\text{cosh} \gamma = 1 - \frac{\omega^2 LC}{2}$$

$$\text{or } \text{coh}(\alpha + j\beta) = 1 - \frac{\omega^2 LC}{2} \quad \text{--- (8)}$$

$$\text{cosh} \alpha \cos \beta + j \sinh \alpha \sin \beta = 1 - \frac{\omega^2 LC}{2} \quad \text{--- (9)}$$

Equating the real & imaginary parts of above equation (9)

$$\text{cosh} \alpha \cos \beta = 1 - \frac{\omega^2 LC}{2} \quad \text{--- (10)}$$

$$\sinh \alpha \sin \beta = 0 \quad \text{--- (11)}$$

For pass band. In the pass band, there is no attenuation Hence $\alpha = 0$

$$\cos \beta = 1 - \frac{\omega^2 LC}{2} \quad \text{--- (12)}$$

The value of $\cos \beta$ swings from +1 and -1. Hence $\cos \beta = 1$ gives, from eq (12) $\frac{\omega^2 LC}{2} = 0$ ie $\omega = 0$. This gives $f = 0$ i.e. the lower cut off frequency of the filter operation.

If $\cos \beta = -1$ gives the higher cut off frequency.

from eq (12) $\frac{\omega^2 LC}{2} = 2$.

i.e. $\omega_c = \frac{2}{\sqrt{LC}}$ giving $f_c = \frac{1}{\pi \sqrt{LC}}$
(i.e. the higher cut-off frequency).

from eq (12)

$$\cos \beta = 1 - \frac{\omega^2 LC}{2} = 1 - \frac{\omega^2}{2LC} = 1 - 2 \frac{\omega^2}{\omega_c^2}$$

$$\beta = \cos^{-1} \left[1 - 2 \frac{\omega^2}{\omega_c^2} \right] \text{ radians} \quad \text{--- (13)}$$

Also, $\cos \beta = 1 - 2 \sin^2 \frac{\beta}{2} = 1$

$$= 1 - \frac{\omega^2 LC}{2}$$

$$2 \sin^2 \frac{\beta}{2} = 2 \frac{\omega^2}{\omega_c^2}$$

$$\beta = 2 \sin^{-1} \frac{\omega}{\omega_c} \text{ rad.}$$

For attenuation band:

In attenuation band it is obvious that $a \neq 0$. Hence it is justified to answer, from eq (11)

$$\beta = n \pi$$

Then from eq (10) for $n=1$

$$-\cosh a = 1 - 2 \frac{\omega^2}{\omega_c^2}$$

$$\alpha = \cosh^{-1} \left[2 \frac{\omega^2}{\omega_c^2} - 1 \right] \text{Nepers} \quad (14)$$

Also $\cosh \alpha = 1 + 2 \cosh^2 \frac{\alpha}{2}$

$$1 + 2 \cosh^2 \frac{\alpha}{2} = 1 + 2 \frac{\omega^2}{\omega_c^2}$$

which gives

$$\alpha = 2 \cosh^{-1} \left[\frac{\omega}{\omega_c} \right] \text{Nep} = 2 \cosh^{-1} \left[\frac{f}{f_c} \right] \text{Nepers}$$

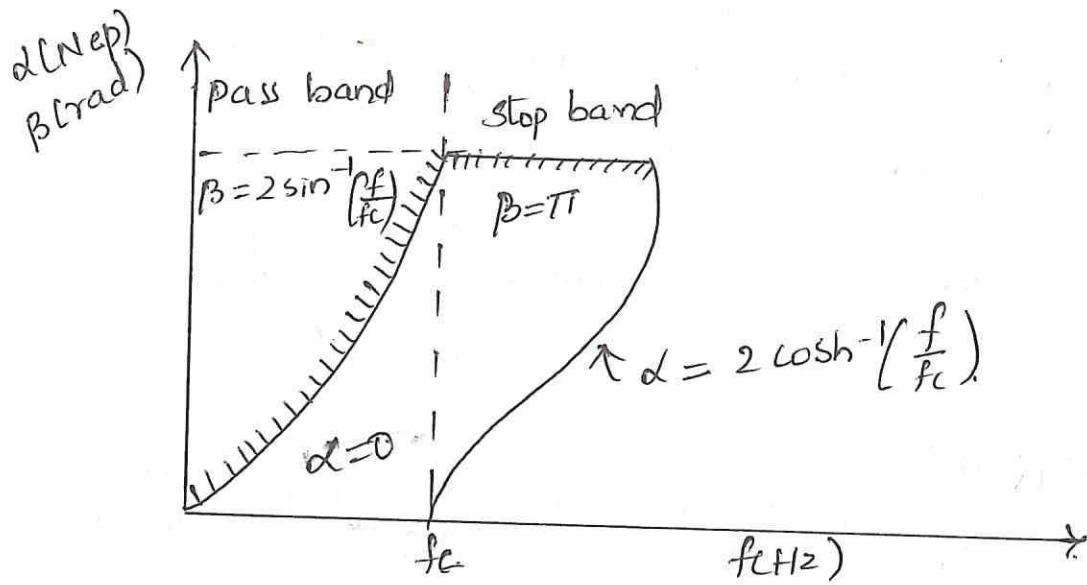


Fig: α and β characteristics of LPF section.

→ Design of a prototype LPF section.

$$K = R_0 = \sqrt{\frac{L}{C}}$$

$$f_c = \frac{1}{\pi \sqrt{LC}}$$

$$L = \frac{R_0}{\pi f_c}$$

$$C = \frac{1}{\pi R_0 f_c}$$

Problems

1. In a simple T section, a low pass filter has a design impedance R_0 . Find Z_{0T} at $0.9f_c$.

Sol

$$\frac{f}{f_c} = 0.9$$

for LPF $Z_{0T} = \frac{R_0}{\sqrt{1 - \left(\frac{f}{f_c}\right)^2}} = \frac{R_0}{\sqrt{1 - (0.9)^2}} = 2.3R_0$

2. Design a constant K -lowpass filter having cut-off frequency 2.5 kHz and design resistance $R_0 = 700\Omega$. Also find the frequency at which this filter produces attenuation of 19.1 dB . Find its characteristic impedance and phase constant at pass band and stop or attenuation band.

Sol Given data

$$f_c = 2.5\text{ kHz} = 2500\text{ Hz}$$

$$R_0 = 700\Omega$$

$$\text{Attenuation } d = 19.1\text{ dB} = \frac{19.1}{8.686} = 2.199 \text{ nepers.}$$

The design elements of LPF are L and C given by the relations

$$L = \frac{R_0}{\pi f_c} = \frac{700}{\pi \times 2500} = 89.127\text{ mH}$$

$$C = \frac{1}{\pi R_0 f_c} = \frac{1}{\pi \times 700 \times 2500} = 0.1824\text{ F}$$

Attenuation in attenuation band of a LPF is given by the relation

$$\alpha = 2 \cosh^{-1} \left[\frac{f}{f_c} \right]$$

where f be the frequency at which this filter produces attenuation 19.1 dB or 2.199 nepers.

$$\frac{f}{f_c} = \cosh \left(\frac{\alpha}{2} \right)$$

$$\frac{f}{2500} = \cosh \left(\frac{2.199}{2} \right) = 1.66785$$


$$f = 2500 \times 1.66785 = 4.170 \text{ kHz.}$$

The phase constant (β) in pass band is given by


$$\beta = 2 \sin^{-1} \left[\frac{f}{f_c} \right] = 2 \sin^{-1} \left[\frac{4.170}{2.500} \right] \text{ radians.}$$

But as $f > f_c$, β in pass band is imaginary or impracticable, but in attenuation band the phase constant (β) is given by

$$\beta = \pi \text{ radians.}$$

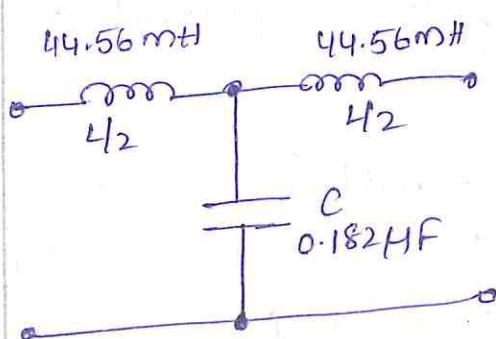

T-type section LPF

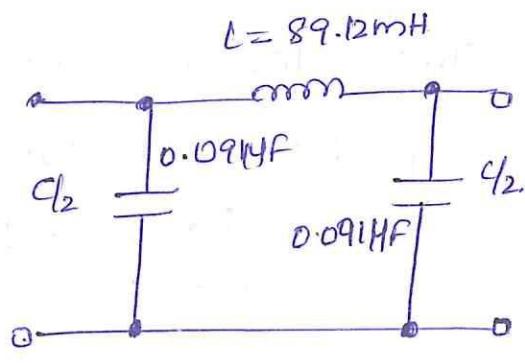

Tl-type LPF

3, A T-section low pass filter has series inductance 80mH and shunt capacitance 0.022μF. Determine the cut-off frequency and nominal design impedance (R_0). Also design an equivalent π-section.

Sol) From the Given data

$$L = 80 \text{ mH} \quad \text{and} \quad C = 0.022 \mu\text{F}$$

Therefore, the cut-off frequency f_c is given by



$$f_c = \frac{1}{\pi \sqrt{LC}} = \frac{1}{\pi \sqrt{(80 \times 10^{-3})(0.022 \times 10^{-6})}} \text{ Hz.}$$

$$f_c = 7.587 \text{ kHz.}$$

The nominal design impedance (R_0) is given by

$$R_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{80 \times 10^{-3}}{0.022 \times 10^{-6}}} \Omega = 1.907 \text{ k}\Omega.$$

The required T and π-section filters are

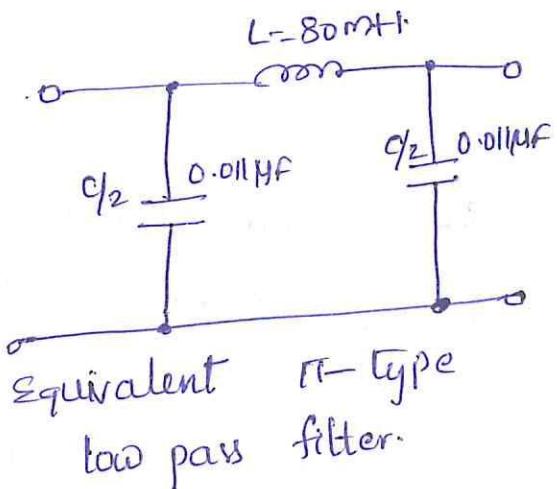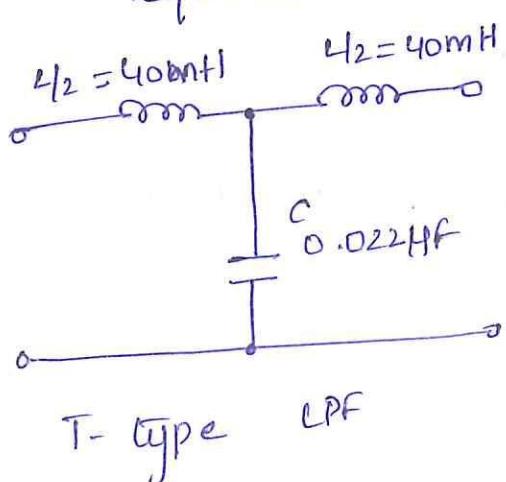


→ Constant K High pass filter.

In both T and Π sections, the total series impedance is given by


$$Z_1 = \frac{1}{j\omega C} \quad \text{--- (1)}$$

and shunt impedance
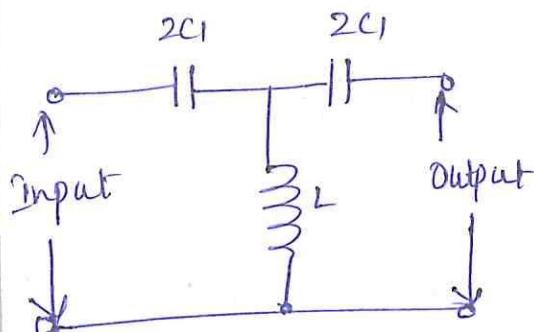
$$Z_2 = 1 + j\omega L \quad \text{--- (2)}$$



T-type prototype HPF

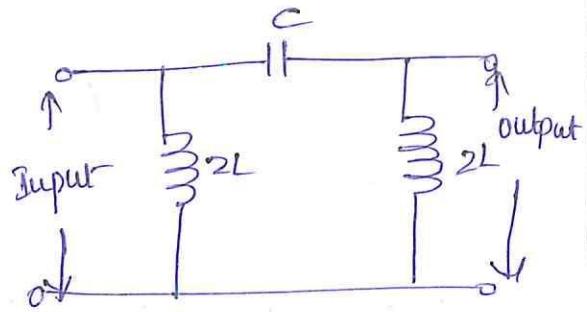

Π -section prototype HPF.

Hence eq (1) \times eq (2)

$$Z_1 Z_2 = \frac{1}{j\omega C} \times j\omega L = \boxed{\frac{L}{C} = R_0^2} \quad \text{--- (3)}$$

$$\Rightarrow R_0 = \sqrt{\frac{L}{C}}$$

The characteristic impedance of a T section being given by

$$Z_{OT} = \sqrt{\frac{Z_1^2 + Z_2^2}{4}}$$

In case of constant - K HPF section

$$Z_{OT} = \sqrt{\frac{1}{4\omega^2 C^2} + \frac{L}{C}} \\ = \sqrt{\frac{L}{C}} \sqrt{1 - \frac{1}{4\omega^2 CL}} \quad \text{--- (4)}$$

$$= R_0 \sqrt{1 - \frac{1}{4\omega^2 LC}} \quad \text{--- (4)}$$

If $4\omega^2 LC > 1$: Z_{OT} is real and filter works in the pass band.

$4\omega^2 LC < 1$: Z_{OT} is imaginary, the filter lies in the attenuation band.

The cut off frequency is given by

$$4\omega_c^2 LC = 1 \quad \text{i.e. } \omega_c = \frac{1}{2\sqrt{LC}}$$

$$\boxed{f_c = \frac{1}{4\pi\sqrt{LC}}} \quad \text{--- (5)}$$

Also $Z_{OT} = R_0 \sqrt{1 - \frac{1}{4\omega^2 LC}}$

$$= R_0 \sqrt{1 - \frac{\omega_c^2}{\omega^2}} = R_0 \sqrt{1 - \frac{f_c^2}{f^2}} \quad \text{--- (6)}$$

where $\omega_c^2 = 1/4LC$

Hence $Z_{OTI} = \frac{R_0^2}{Z_{OT}} = \frac{R_0^2}{R_0 \sqrt{1 - \frac{\omega_c^2}{\omega^2}}} = \frac{R_0}{\sqrt{1 - \left(\frac{\omega_c}{\omega}\right)^2}}$

$$\boxed{Z_{OTI} = \frac{R_0}{\sqrt{1 - \left(\frac{f_c}{f}\right)^2}}} \quad \text{--- (7)}$$

The relative frequency characteristic has been shown


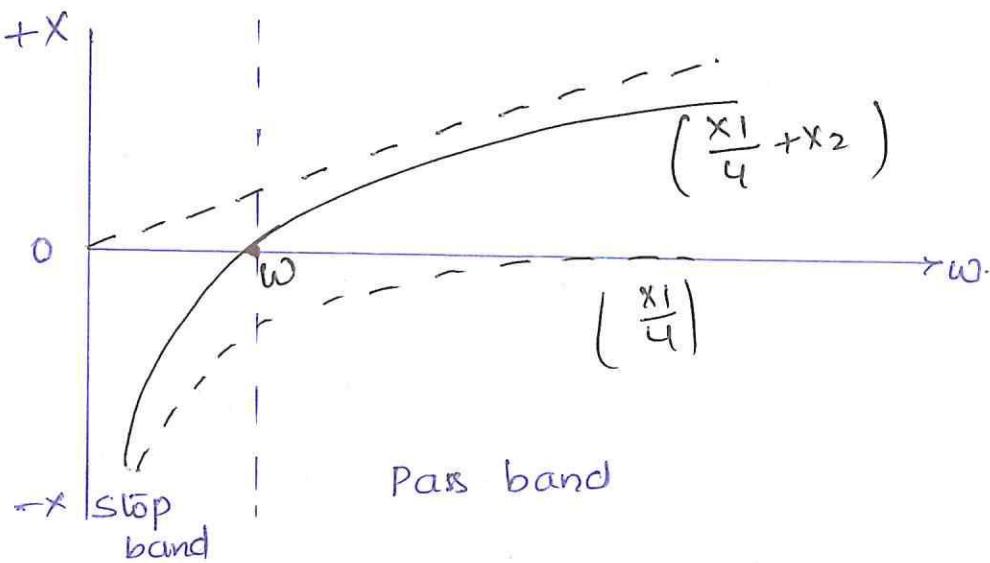


Fig: Reactance frequency characteristic of HPF

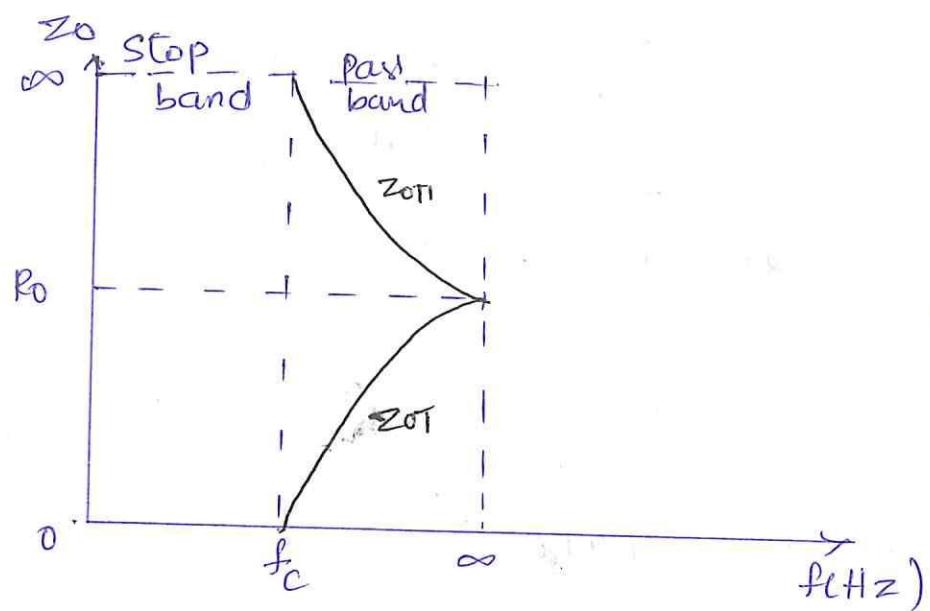

z_0 profile of HPF

→ Attenuation (α) and the phase shift (β) characteristic of HPF

for a T network, the propagation constant (r) is given by the relation

$$\cosh r = 1 + \frac{Z_1}{2Z_2} \quad \text{--- (8)}$$

$$\text{But } 1 + \frac{Z_1}{2Z_2} = 1 + \frac{1/j\omega C}{2j\omega L} = 1 + \frac{1}{j\omega C} \times \frac{1}{2j\omega L}$$

$$\cosh r = 1 - \frac{1}{2\omega^2 LC} \quad - ⑨$$

But $r = \alpha + j\beta$

$$\cosh(\alpha + j\beta) = 1 - \frac{1}{2\omega^2 LC}$$

$$\cosh \alpha \cos \beta + j \sinh \alpha \sin \beta = 1 - \frac{1}{2\omega^2 LC} \quad - ⑩$$

Equating Real and Imaginary eq.

$$\cosh \alpha \cos \beta = 1 - \frac{1}{2\omega^2 LC} \quad - ⑩.a$$

$$j \sinh \alpha \sin \beta = 0 \quad - ⑩.b$$

from eq ⑩.b either $\alpha = 0$ or $\beta = n\pi$.

• for pass band

In pass band $\alpha = 0$ (as there is no attenuation). Phase shift exists giving the value of

$$\cos \beta = 1 - \frac{1}{2\omega^2 LC} \text{ when } \alpha = 0.$$

It is evident from $\cos \beta = 1$ gives cut-off frequency (as with $\cos \beta = 1$, from equation $\cos \beta = 1 - \frac{1}{2\omega^2 LC}$, $\omega = \infty$ i.e $f = \infty$)

This can be referred as cut-off frequency.

When $\cos \beta = -1$ in eq ⑩-a

$$-1 = 1 - \frac{1}{2\omega^2 LC}$$

$\omega_c^2 = \frac{1}{4LC}$ [∴ ω_c represents a particular value of ω when $\cos\beta = -1$].

Hence, the lower cut-off frequency

$$\omega_c = \frac{1}{2\sqrt{LC}}$$

$$f_c = \frac{1}{4\pi\sqrt{LC}}$$

Also from $\cos\beta = 1 - \frac{1}{2\omega^2 LC}$

$$\cos\beta = 1 - \frac{2\omega_c^2}{\omega^2}$$

$$\beta = \cos^{-1} \left[1 - \frac{2\omega_c^2}{\omega_c^2} \right] = \cos^{-1} \left[1 - 2 \left(\frac{f_c}{f_c} \right)^2 \right]$$

Again $\cos\beta = 1 - 2 \sin^2 \frac{\beta}{2} = 1 - 2 \frac{\omega_c^2}{\omega^2}$

$$\beta = 2 \sin^{-1} \frac{\omega_c}{\omega}$$


radians — ⑪

• For Attenuation Band:

utilizing $\beta = \pi$ in eq 10.b, α being not equal to zero ($\alpha \neq 0$)

$$\cosh \alpha = -1 + \frac{1}{2\omega^2 LC} = -1 + 2 \frac{\omega_c^2}{\omega^2}$$
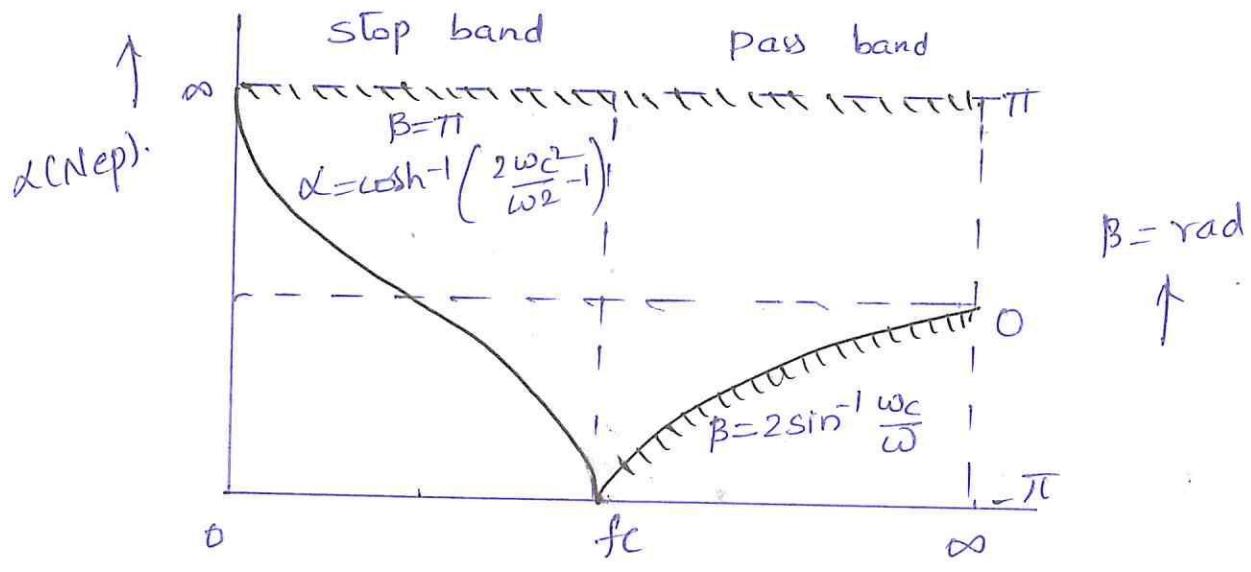
$$\alpha = \cosh^{-1} \left[2 \frac{\omega_c^2}{\omega^2} - 1 \right] \quad \text{—— ⑫}$$



α and β profile of HPF.

- (i) Design a T and Π section constant $-K$ high pass filter having cut-off frequency of 12 kHz and nominal impedance $R_0 = 500 \Omega$. Also find (ii) its characteristic impedance and phase constant at 24 kHz and (iii) attenuation at 4 kHz.



Sol) The shunt arm inductance L is given by

$$L = \frac{R_0}{4\pi f_c} = \frac{500}{4\pi \times 12 \times 10^3} = 3.316 \text{ mH}$$

The series arm capacitance C is given by

$$C = \frac{1}{4\pi R_0 f_c} = \frac{1}{4\pi \times 1 \times 500 \times 12 \times 10^3} = 0.0013 \mu F$$

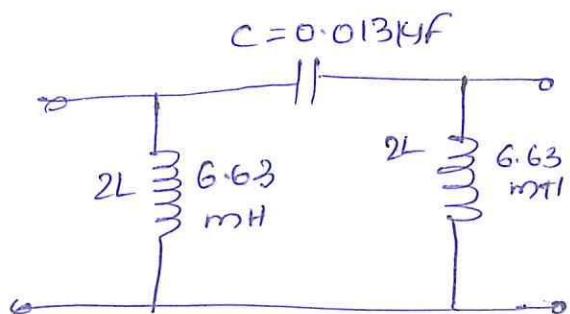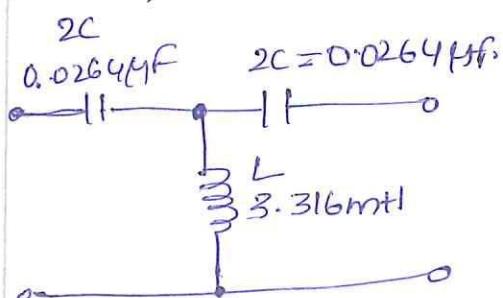Hence, the required T and Π -section high pass filter.



(i) If $f = 24\text{kHz}$, the characteristic impedances of T and π-section are given by.

$$Z_{OT} = R_0 \sqrt{1 - \left[\frac{f_c}{f} \right]^2}$$

$$= 500 \sqrt{1 - \left[\frac{12 \times 10^3}{24 \times 10^3} \right]^2} = 433.013 \Omega$$

$$Z_{O\pi} = \frac{R_0}{\sqrt{1 - \left[\frac{f_c}{f} \right]^2}}$$

$$= \frac{500}{\sqrt{1 - \left[\frac{12 \times 10^3}{24 \times 10^3} \right]^2}} = 577.350 \Omega$$

The phase constant (β) in pass band is given by

$$\beta = 2 \sin^{-1} \left[\frac{f_c}{f} \right]$$

$$= 2 \sin^{-1} \left[\frac{12 \times 10^3}{24 \times 10^3} \right]$$

$$= 60^\circ$$

In attenuation band, α is given by at


frequency 4kHz .

$$\alpha = 2 \cosh^{-1} \left[\frac{f_c}{f} \right] \text{neper}$$


$$= 2 \cosh^{-1} \left[\frac{12 \times 10^3}{4 \times 10^3} \right] \text{neper} = 3.525 \text{ nepers.}$$

→ Band Pass Filter (CBPF)

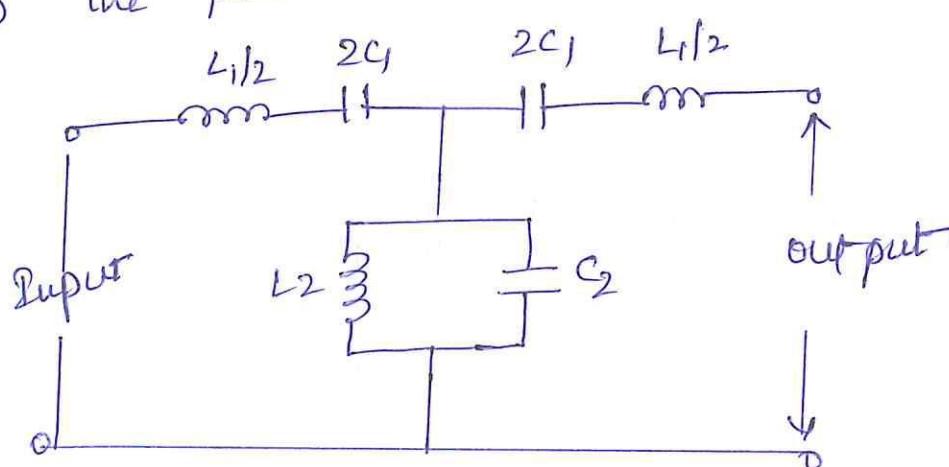- This filter is a combination of two parallel tuned circuits. At resonance, the shunt arm behaves as a rejector circuit offering a very high impedance in the shunt arm while the series arm at resonance offers least impedance (acceptor circuit); thus, any electric signal, incident at the input of the filter allows its transmission through it within the pass band.



T- configuration

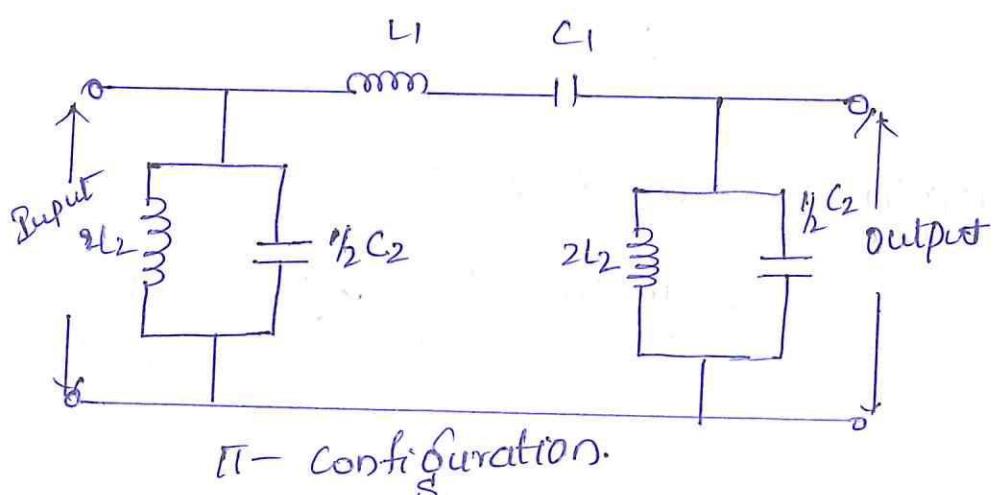

Π - configuration.

Hence, at resonance, for each of the series and shunt arm,

$$\omega_0^2 L_1 C_1 = 1 \quad \text{--- (1)}$$

$$\omega_0^2 L_2 C_2 = 1 \quad \text{--- (2)}$$

\therefore at resonance $f_0 = \frac{1}{2\pi\sqrt{LC}}$ and $\omega_0 = \frac{1}{\sqrt{LC}}$

f_0 & ω_0 being the resonance frequency in Hz
or rad/sec]

Comparing eq ① & ②

$$\omega_0^2 L_1 C_1 = \omega_0^2 L_2 C_2$$

$$\frac{L_1}{C_1} = \frac{L_2}{C_2} \quad \text{--- (3)}$$

$$\text{Now } z_1 = j\omega L_1 + \frac{1}{j\omega C_1}$$

$$= j \left[\frac{\omega^2 L_1 C_1 - 1}{\omega C_1} \right] \quad \text{--- (4)}$$

$$z_2 = \frac{j\omega L_2 \left[\frac{1}{j\omega C_2} \right]}{j\omega L_2 + \frac{1}{j\omega C_2}} = j \frac{\omega L_2}{1 - \omega^2 L_2 C_2} \quad \text{--- (5)}$$

Multiplying eq ④ & ⑤

$$\begin{aligned} z_1 z_2 &= j \left[\frac{\omega^2 L_1 C_1 - 1}{\omega C_1} \right] \times j \frac{\omega L_2}{1 - \omega^2 L_2 C_2} \\ &= \frac{L_2 (\omega^2 L_1 C_1 - 1)}{C_1 (\omega^2 L_2 C_2 - 1)} \quad \text{--- (6)} \end{aligned}$$

finally $z_1 z_2 = \frac{L_2}{C_1} \left[\text{i.e. } \frac{L_1}{C_2} \text{ by using eq (3)} \right]$

$$= R_0^2 \text{ (say)}$$

$Z_1 Z_2 = R_0^2$, R_0 being a real quantity. — (7)

The characteristic impedance Z_0 of any T section being given by

$$Z_{0T}^2 = \frac{Z_1^2}{4} + Z_1 Z_2$$

normalisation for Z_1 yields

$$\frac{Z_{0T}^2}{Z_1} = \frac{Z_1^2}{4} + Z_2$$

$$\frac{Z_{0T}^2}{Z_1 Z_2} = \frac{Z_1}{4Z_2} + 1 \quad \longrightarrow (8)$$

[\because Dividing both sides by Z_2]

From eq (8), it can be observed that the limiting condition ($Z_{0T}=0$) is achieved if

$$\frac{Z_1}{4Z_2} = -1$$

Thus for, $\frac{Z_1}{4Z_2} = -1$

$$Z_1 = -4Z_2$$

$$Z_1 Z_1 = -4Z_2 \cdot Z_1$$

$$Z_1^2 = -4Z_1 Z_2$$

$$= -4Z_0^2 \Rightarrow -4R_0^2$$

$$Z_1 = \pm j2R_0 \quad \longrightarrow (9)$$

Equation ⑨ indicates that Z_1 is either positive or negative at the limiting condition.

It shows that Z_1 is positive for a particular frequency f_1 and Z_1 is negative for another particular frequency, f_2 .

* Substituting the value of Z_1 from eq ⑩ in eq ⑨

$$j \left[\frac{\omega_1^2 L_1 C_1 - 1}{\omega_1 C_1} \right] = j Z_0$$

[taking +ve value of Z_1 and corresponding frequency at f_1]

$$\omega_1^2 L_1 C_1 - 1 = Z_0 \omega_1 C_1$$

$$\omega_1^2 L_1 C_1 - Z_0 \omega_1 C_1 - 1 = 0$$

$$\omega_1 = \frac{Z_0 C_1 \pm \sqrt{4 Z_0^2 C_1^2 + 4 L_1 C_1}}{2 L_1 C_1}$$

$$f_1 = \frac{Z_0 C_1 \pm \sqrt{4 Z_0^2 C_1^2 + 4 L_1 C_1}}{2 \pi \times 2 L_1 C_1}$$

$$= 2 \pi Z_0 + \frac{\sqrt{\left[Z_0^2 + \frac{L_1}{C_1} \right] 4 C_1^2}}{2 \pi \times 2 L_1 C_1}$$

$$= \frac{2 C_1 \left[Z_0 + \sqrt{Z_0^2 + \frac{L_1}{C_1}} \right]}{2 \pi \times 2 L_1 C_1}$$

$$f_1 = \frac{R_o + \sqrt{R_o^2 + \frac{L_1}{C_1}}}{2\pi L_1} \quad \text{--- (10-a)}$$

The equation (10.a) provides the particular one of the cut-off frequencies of the BPF when Z_1 behaves as a positive impedance.

Assuming f_2 to be other particular frequency when Z_1 behaves as negative impedance, in a similar way

$$j \left[\frac{\omega_2^2 L_1 C_1 - 1}{\omega_2 C_1} \right] = -j Z_o R_o$$

$$j \omega_2^2 L_1 C_1 - 1 = -j Z_o \omega_2 C_1$$

$$\omega_2^2 L_1 C_1 - 1 = -Z_o \omega_2 C_1$$

$$\omega_2^2 L_1 C_1 - Z_o \omega_2 C_1 - 1 = 0$$

$$-b \pm \sqrt{b^2 - 4ac}$$

This gives

$$\omega_2 = \frac{-Z_o C_1 \pm \sqrt{4Z_o^2 C_1^2 + 4L_1 C_1}}{2\pi \times 2L_1 C_1} \quad \text{--- (11)}$$

$$f_2 = \frac{-Z_o C_1 \pm \sqrt{4Z_o^2 C_1^2 + 4L_1 C_1}}{2\pi \times 2L_1 C_1}$$

$$= -Z_o \pm \sqrt{\frac{Z_o^2 + L_1}{C_1}}$$

$$f_2 = - \left[\frac{R_o + \sqrt{R_o^2 + \frac{L_1}{C_1}}}{2\pi L_1} \right] \quad \text{--- } \textcircled{II-b} \quad \text{II-a}$$

Eq (II-a) gives the second cut-off frequency of the B.P.F.

- As negative frequency does not carry any physical meaning hence the sign of the root of f_1 and f_2 both are taken to be positive.

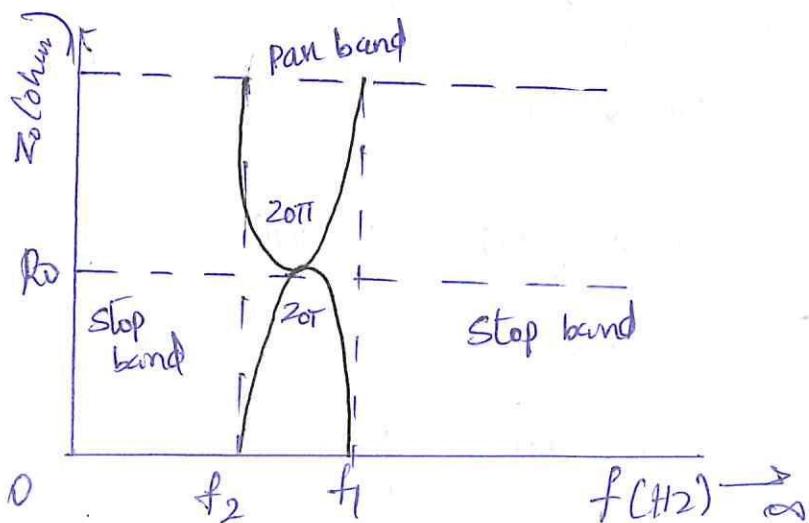
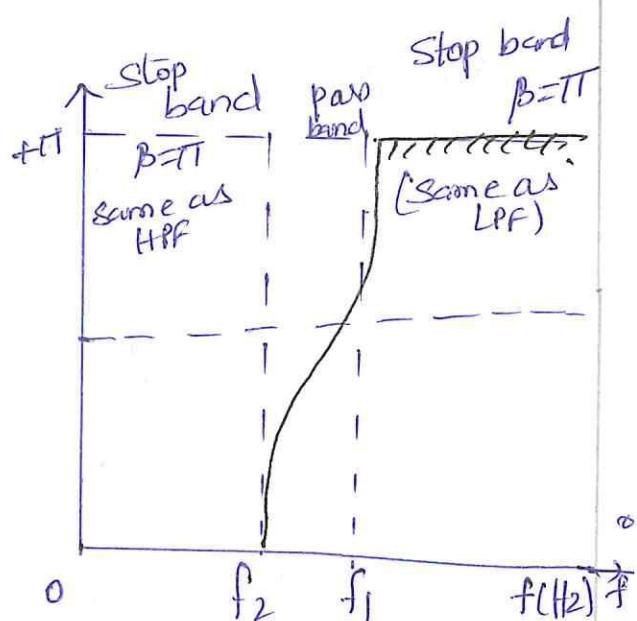
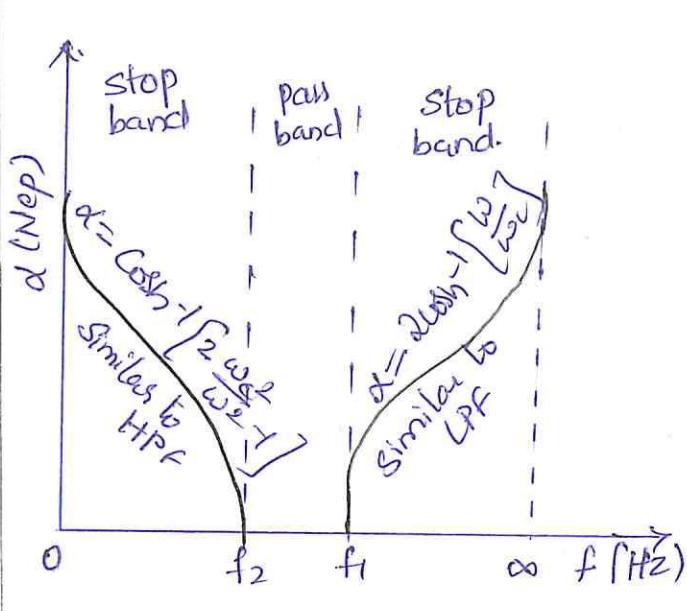


Figure: characteristic of BPF section.

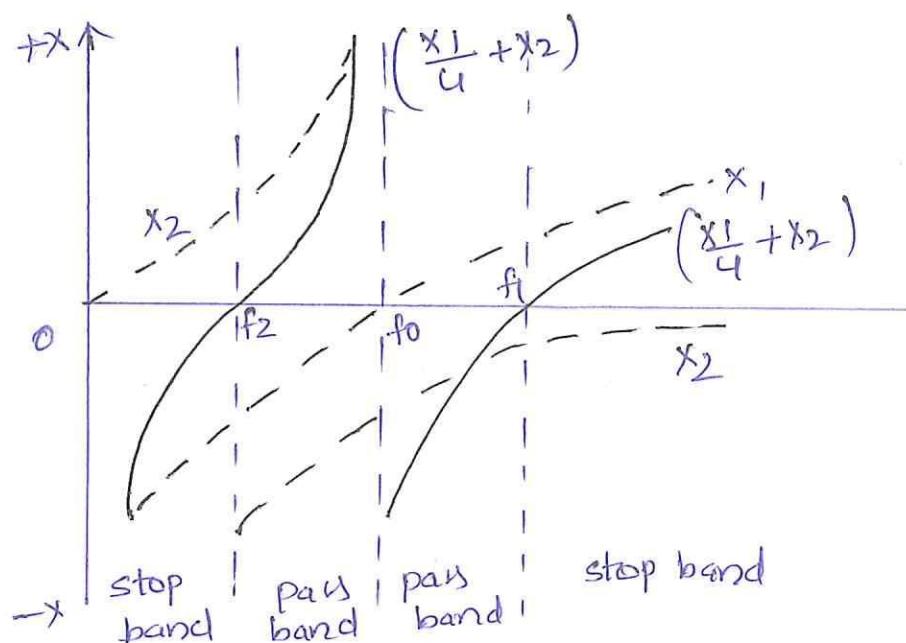


Figure: Reactance frequency characteristics of BPF

→ Design of Prototype Band Pass filter.

Taking $Z_1 = -j2R_0$ & substituting the values of

Z_1

$$\frac{\omega_2^2 L_1 C_1 - 1}{\omega_2 C_1} = -2R_0$$

[$\because \omega_2$ being the frequency in rad/sec when $Z_1 = -j2R_0$]

$$\frac{1 - \omega_2^2 L_1 C_1}{\omega_2 C_1} = 2R_0$$

$$1 - \omega_2^2 L_1 C_1 = 2R_0 \omega_2 C_1$$

$$1 - \frac{\omega_2^2}{\omega_0^2} = 2R_0 \omega_2 C_1$$

$$\left[\because L_1 C_1 = L_2 C_2 = \frac{1}{\omega_0^2} \right]$$

$$1 - \frac{f_2^2}{f_0^2} = 2R_0 \times 2\pi f_2 \times C_1$$

[$\because f_2$ in Hz corresponds to ω_2 in rad/sec]

$$1 - \frac{f_2^2}{f_1 f_2} = 4\pi f_2 R_0 C_1$$

$$[\because f_0^2 = f_1 f_2]$$

As the magnitude of Z_1 remains same at f_1 & f_2
the only difference being the change of sign
between f_1 and f_2 hence it is justified to

write

$$Z_1 \text{ at } f_1 = Z_1 \text{ at } f_2$$

$$\left[j\omega_1 L_1 + \frac{1}{j\omega_1 C_1} \right] = - \left[j\omega_2 L_1 + \frac{1}{j\omega_2 C_1} \right]$$

$$\left[\omega_1 L_1 - \frac{1}{\omega_1 C_1} \right] = - \left[\omega_2 L_1 - \frac{1}{\omega_2 C_1} \right]$$

$$\frac{\omega_1^2 L_1 C_1 - 1}{\omega_1 C_1} = - \frac{\omega_2^2 L_1 C_1 - 1}{\omega_2 C_1}$$

$$\left[\frac{\omega_1^2 - 1}{\omega_0^2} \right] / \omega_1 = - \left[\frac{\omega_2^2 - 1}{\omega_0^2} \right] / \omega_2$$

~~$$\frac{\omega}{f_0} \left[\frac{f_1^2}{f_0^2} - 1 \right] / f_1 = - \left[\frac{f_2^2}{f_0^2} - 1 \right] / f_2$$~~

$$1 - \frac{f_1^2}{f_0^2} = \frac{f_1}{f_2} \left[\frac{f_2^2}{f_0^2} - 1 \right]$$

$$1 - \frac{f_1^2}{f_0^2} = \frac{f_1 f_2}{f_0} - \frac{f_1}{f_2}$$

$$1 + \frac{f_1}{f_2} = \frac{f_1 f_2}{f_0} + \frac{f_1^2}{f_0^2}$$

$$= \frac{f_1 f_2 + f_1^2}{f_0^2}$$

$$\frac{f_1 + f_2}{f_2} = \frac{f_1 f_2 + f_1^2}{f_2}$$

$$f_0^2 = \frac{(f_1 f_2 + f_1^2)}{f_1 + f_2} = f_1 f_2,$$

$$\boxed{f_0 = \sqrt{f_1 f_2}} \quad \text{--- (12)}$$

$$1 - \frac{f_2}{f_1} = 4\pi f_2 R_0 C_1$$

$$f_1 - f_2 = 4\pi f_1 f_2 R_0 C_1$$

$$\boxed{C_1 = (f_1 - f_2) \times \frac{1}{4\pi f_1 f_2 R_0}} \quad \text{forad --- (13)}$$

Again from $L_1 C_1 = \frac{1}{\omega_0^2}$

$$\begin{aligned} L_1 &= \frac{1}{\omega_0^2 C_1} = \frac{1}{(2\pi f_0)^2 \times C_1} \\ &= \frac{1}{4\pi^2 f_1 f_2 (f_1 - f_2) \times \frac{1}{4\pi f_1 f_2 R_0}} \quad \text{--- (14)} \end{aligned}$$

$$L_1 = \frac{R_0}{\pi (f_1 - f_2)} \text{ Henry}$$

Also from

$$R_0 = \sqrt{\frac{L}{C}}, \quad L = R_0^2 C_1 \quad \text{i.e.} \quad L_2 = R_0^2 C_1$$

$$\left[\because \frac{L_2}{C_1} = \frac{L_1}{C_2} = R_0^2 \right]$$

$$L_2 = R_0^2 C_1 = (f_1 - f_2) \frac{1}{4\pi f_1 f_2 R_0} \cdot R_0^2$$

$$\boxed{L_2 = \frac{R_0 (f_1 - f_2)}{4\pi f_1 f_2} \text{ Henry}} \quad \text{--- (15)}$$

Similarly $C_2 = \frac{L_1}{R_o^2}$ gives

$$C_2 = \frac{R_o / \pi (f_1 - f_2)}{R_o^2}$$

$$C_2 = \frac{1}{\pi R_o (f_1 - f_2)} \text{ paracl}$$

1. Design a prototype bandpass filter section (T & T') having cut-off frequencies of 3000Hz and 6000 Hz and nominal characteristics impedance of 600Ω. Also find the resonant frequency of shunt arm or series arm.

From the given data

$$f_2 = 3000 \text{ Hz} \quad f_1 = 6000 \text{ Hz} \quad \text{and} \quad R_o = 600 \Omega$$

$$L_1 = \frac{R_o}{\pi (f_2 - f_1)} = \frac{600}{\pi (6000 - 3000)} \text{ H.}$$

$$= 63.662 \text{ mH}$$

$$\text{Hence } \frac{L_1}{2} = \frac{63.662}{2} = 31.831 \text{ mH.}$$

The series arm capacitance (C_1) is given by

$$C_1 = \frac{(f_1 - f_2)}{4\pi R_o f_1 f_2}$$

$$= \frac{6000 - 3000}{4\pi \times 600 \times 3000 \times 6000}$$

$$= 0.022 \text{ HF}$$

Hence, $2C_1 = 0.044 \text{ HF}$

Again, the shunt arm impedance inductance (L_2) and capacitance (C_2) are given by

$$\begin{aligned} L_2 &= \frac{R_0(f_1 - f_2)}{4\pi f_1 f_2} \\ &= \frac{600(6000 - 3000)}{4\pi \times 6000 \times 3000} \text{ F} \end{aligned}$$

$$L_2 = 7.96 \text{ mH}$$

Hence $2L_1 = 15.92 \text{ mH}$

$$\begin{aligned} C_2 &= \frac{1}{\pi R_0 (f_1 - f_2)} \\ &= \frac{1}{\pi \times 600 (6000 - 3000)} \text{ F} \\ &= 0.177 \text{ HF} \end{aligned}$$



Hence $\frac{C_2}{2} = 0.0885 \text{ HF}$

Now, the resonant frequency (f_0) of the band pass filter is given by

$$\begin{aligned} f_0 &= \sqrt{f_1 f_2} = \sqrt{3000 \times 6000} \\ &= 4242.64 \text{ Hz} \end{aligned}$$

The band pass filter (T and π -section) are.


shown as

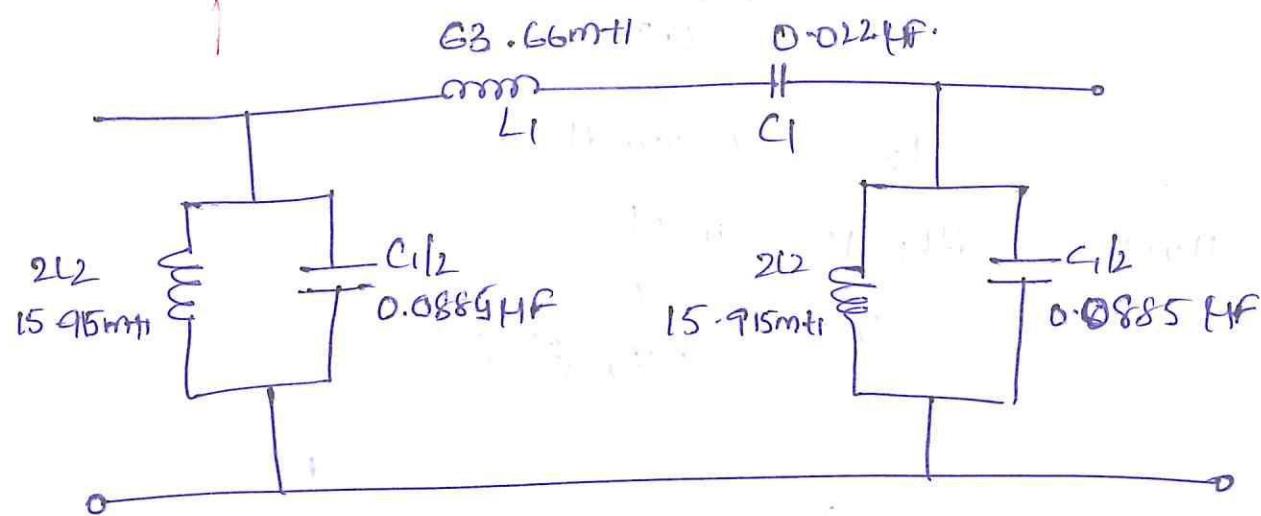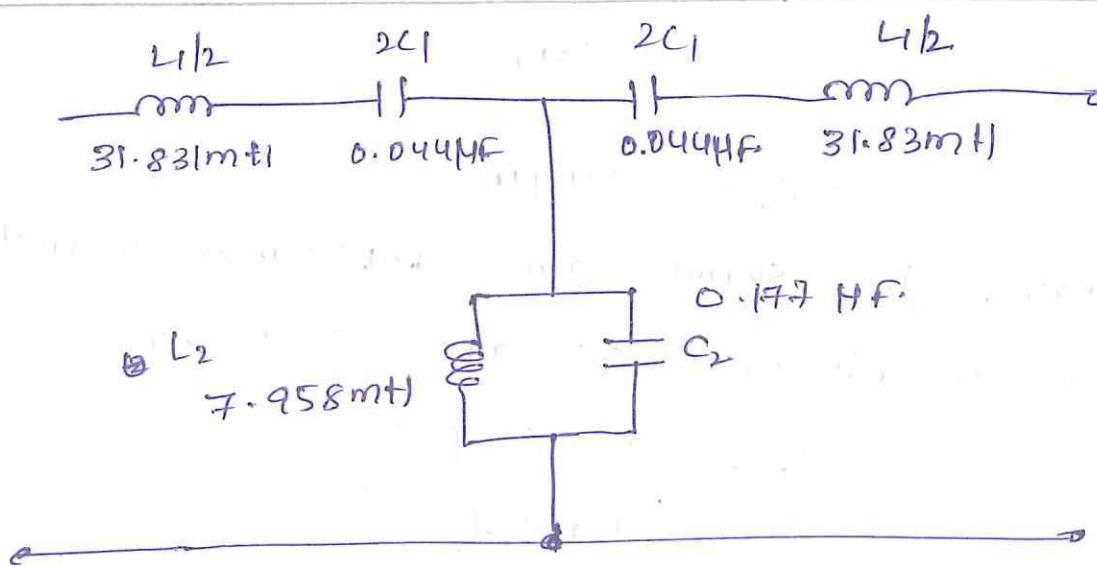


→ Analysis of a Prototype Band stop filter (BSF)

- A band stop filter, in its simplest form is a tandem of a low pass filter with a high pass filter.
- Here, the cut off frequency of the two high pass filter is higher than the cut-off frequency of the low pass filter.
- The overlapping attenuation band of the two filters then constitutes the stop band of the band stop filter.

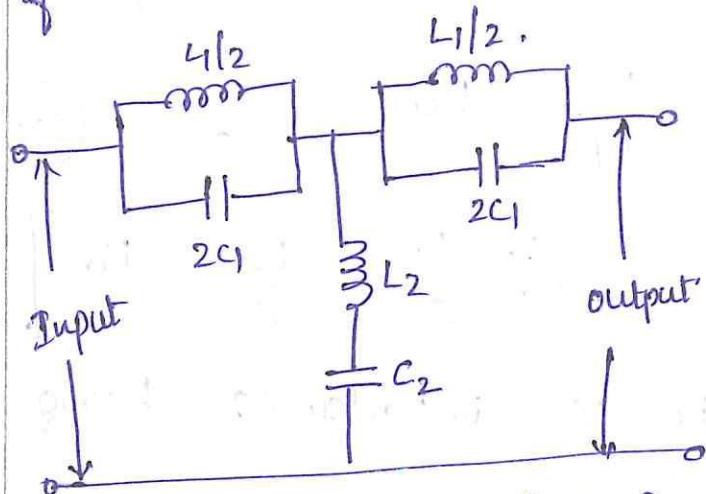Z_1 becomes series impedance of a parallel tuned circuit and Z_2 is the shunt impedance of series tuned circuit.



T-configuration of BSF

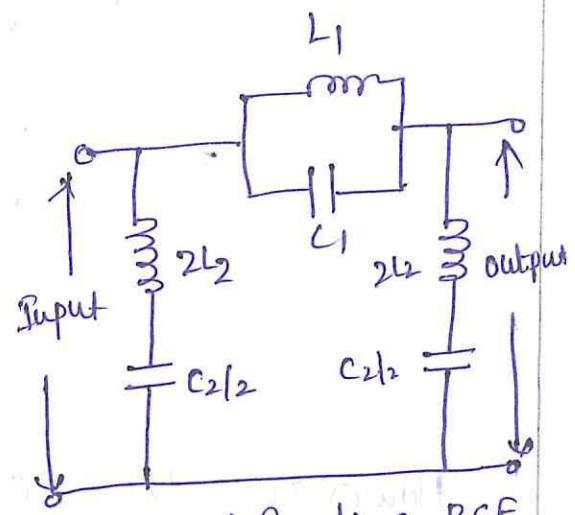

π -configuration BSF

Operation is initiated when resonance occurs so that shunt impedance ($C_{2/2}$) becomes minimum and series impedance (C_1) becomes maximum. Thus incident signal is blocked at this particular condition.

Thus at resonance:

$$\omega_0^2 L_1 C_1 = 1$$

—①

$$\omega_0^2 L_2 C_2 = 1$$

- ②

$$L_1 C_1 = L_2 C_2 = \frac{1}{\omega_0^2} \quad - ③$$

L

C

$$2j\omega^2 L_1 C_1 + 2$$

however

$$Z_1 = 2 \left[\frac{j\omega L_1}{2} \left[\frac{1}{2j\omega C_1} \right] \right] = j \frac{\omega L_1}{1 - \omega^2 L_1 C_1} \quad - ④$$

$$Z_2 = j\omega L_2 + \frac{1}{j\omega C_2} = j \left[\frac{\omega^2 L_2 C_2 - 1}{\omega C_2} \right] \quad - ⑤$$

Therefore

$$Z_1 Z_2 = j \frac{\omega L_1}{1 - \omega^2 L_1 C_1} \times j \left[\frac{\omega^2 L_2 C_2 - 1}{\omega C_2} \right]$$

$$= \frac{L_1}{C_2} = \frac{L_2}{C_1} = R_0^2 \quad - (6.9)$$

$$\therefore \frac{L_1}{C_2} = \frac{L_2}{C_1} = R_0^2$$

However the characteristic impedance being given

$$Z_{0T}^2 = \frac{Z_1^2}{4} + Z_1 Z_2$$

normalisation by Z_1 and division by Z_2 gives.

$$\frac{Z_{0T}^2}{Z_1 Z_2} = \frac{Z_1}{4 Z_2} + j$$

$$\frac{Z_1}{4 Z_2} = -1$$

Gives the critical condition as with

$$\frac{z_1}{4z_2} = -1$$

$$Z_{DT} = 0$$

$$\frac{z_1}{4z_2} = -1$$

$$z_1 = -4z_2$$

$$z_1^2 = -4z_1 z_2$$

$$= -4R_0^2$$

$$\therefore z_1 = \pm j2R_0$$

Citing similar reasoning as done for the BPF, it can be commented that z_1 will be positive with f_1 and z_2 will be negative with system frequency f_2 .

Considering z_1 to be positive,

$$z_1 = +j2R_0$$

$$j \frac{\omega_1 L_1}{1 - \omega_1^2 L_1 C_1} = j2R_0$$

$$\omega_1 L_1 = 2R_0 (1 - \omega_1^2 L_1 C_1)$$

$$\omega_1^2 L_1 C_1 \cdot 2R_0 + \omega_1 L_1 - 2R_0 = 0$$

$$\omega_1 = \frac{-L_1 \pm \sqrt{L_1^2 + 4L_1 C_1 \cdot 4R_0^2}}{2L_1 C_1 \cdot 2R_0}$$

$$= -L_1 \pm \frac{\sqrt{L_1^2 + 16L_1 C_1 R_0^2}}{2L_1 C_1 \cdot 2R_0}$$

$$f_1 = \frac{-L_1 \pm \sqrt{L_1^2 + 16L_1 C_1 R_0^2}}{8\pi L_1 C_1 R_0}$$

$$= \frac{-L_1 \pm \sqrt{1 + 16 \frac{C_1}{L_1} R_o^2}}{8\pi C_1 R_o} \text{ Hz.} \quad - (7)$$

Equation (7) provides the lower root of frequency of the Band stop filter.

considering the negative impedance Z_1 for f_2

$$Z_1 = -j2R_o$$

$$j \frac{\omega_2 L_1}{1 - \omega_2^2 L_1 C_1} = -j2R_o$$

[ω_2 being the frequency at which $Z_1 = -j2R_o$]

$$\frac{\omega_2 L_1}{\omega_2^2 L_1 C_1 - 1} = 2R_o$$

$$\omega_2 L_1 = 2R_o (\omega_2^2 L_1 C_1 - 1)$$

$$2R_o \cdot \omega_2^2 L_1 C_1 - \omega_2 L_1 - 2R_o = 0$$

$$\omega_2 = \frac{L_1 \pm \sqrt{L_1^2 + 16R_o^2 L_1 C_1}}{4R_o L_1 C_1}$$

$$= \frac{1 \pm \sqrt{1 + 16R_o^2 \frac{C_1}{L_1}}}{4R_o L_1 C_1}$$

$$f_2 = \frac{1 \pm \sqrt{1 + 16R_o^2 \frac{C_1}{L_1}}}{8\pi R_o C_1} \text{ Hz.} \quad - (8)$$

f_2 gives the higher cut-off frequency.

→ Design of a Band stop filter.

From $Z_1 = j^2 R_0$

$$j \left[\frac{\omega_1 L_1}{1 - \omega_1^2 L_1 C_1} \right] = j^2 R_0$$

$$1 - \omega_1^2 L_1 C_1 = \frac{\omega_1 L_1}{Z R_0}$$

$$1 - \frac{\omega_1^2}{\omega_0^2} = \frac{\omega_1 L_1}{Z R_0}$$

$$1 - \frac{f_2^2}{f_0^2} = \frac{\pi f_1 L_1}{R_0}$$

$$1 - \frac{f_1^2}{f_1 f_2} = \frac{\pi f_1 L_1}{R_0^2}$$

$$\therefore f_0^2 = f_1 + f_2$$

$$1 - \frac{f_1}{f_2} = \frac{\pi f_1 L_1}{R_0}$$

$$L_1 = \frac{R_0 (f_2 - f_1)}{\pi f_1 f_2} \text{ Henry} \quad \text{--- (9)}$$

But $\omega_0^2 L_1 C_1 = 1$

$$C_1 = \frac{1}{\omega_0^2 L_1} = \frac{1}{4\pi^2 f_0^2 L_1}$$

Sub L value

$$C_1 = \frac{1}{4\pi^2 (f_1 f_2) \left(\frac{R_0 (f_2 - f_1)}{\pi f_1 f_2} \right)}$$

$$C_1 = \frac{1}{4\pi R_0 (f_2 - f_1)} \text{ farad.} \quad \text{--- (10)}$$





From $C_2 = \frac{L_1}{R_0^2}$

$$C_2 = \frac{R_o(f_2 - f_1)}{\pi f_1 f_2} \quad \text{Ro}^2$$

$$\boxed{C_2 = \frac{f_2 - f_1}{\pi f_1 f_2 R_o} \text{ found}} \quad \rightarrow (11)$$

$$L_2 = C_1 R_o^2$$
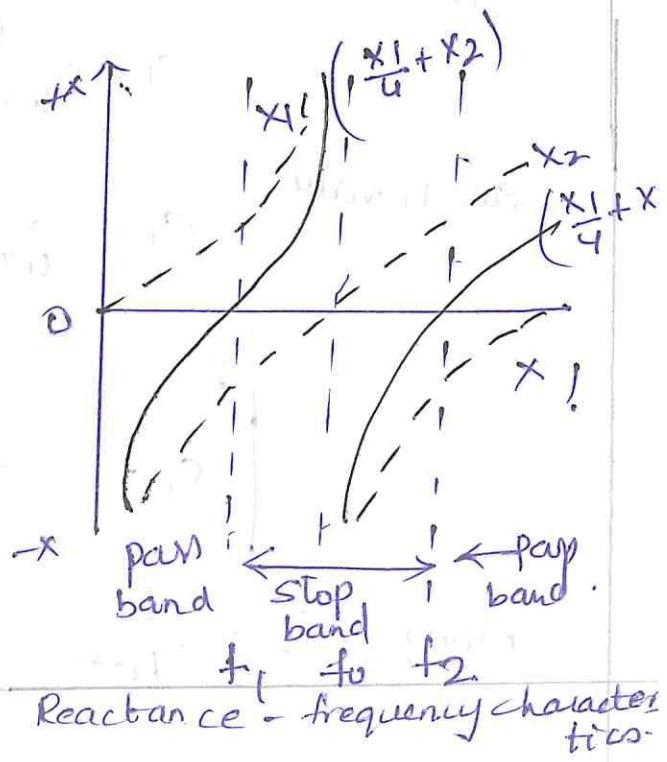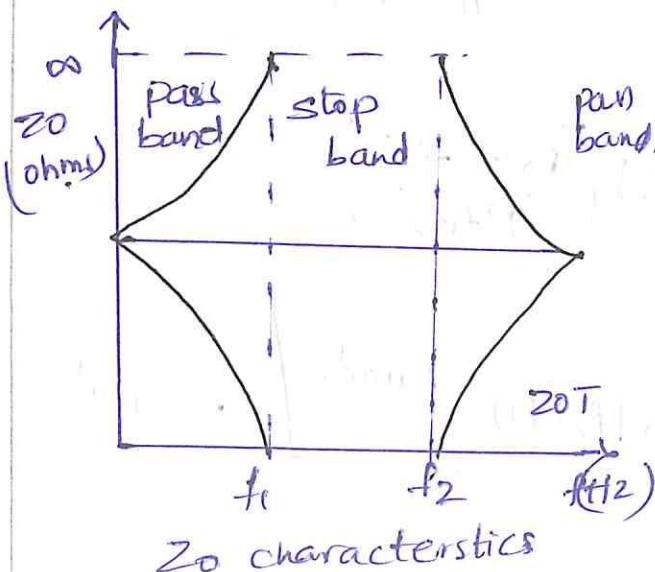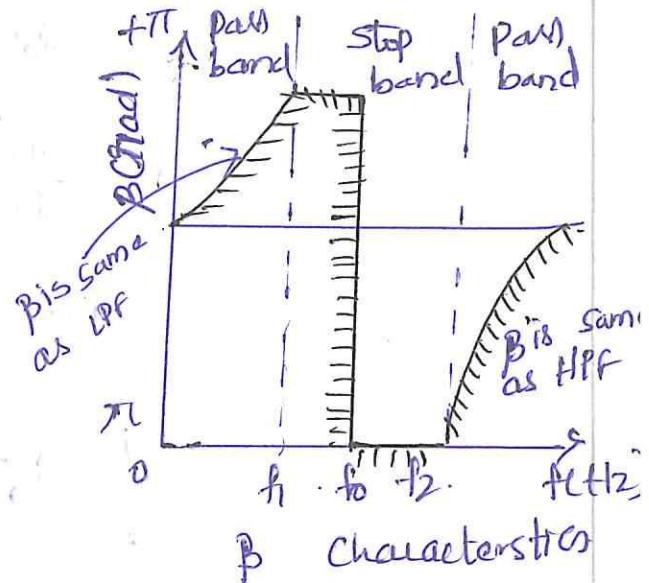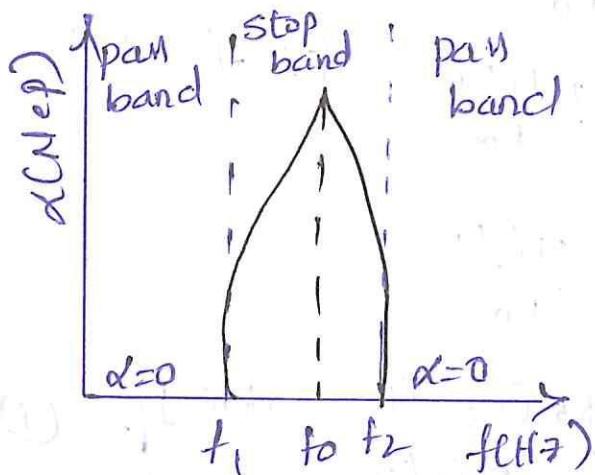
$$\boxed{L_2 = \frac{R_o}{4\pi T^2 (f_2 - f_1)}} \quad \text{Henry} \quad \rightarrow (12)$$



Design a prototype band stop filter section having cut-off frequencies of 2000 Hz and 5000 Hz and design resistance of 600 Ω.

∴ The series arm inductance (L_1) and capacitance (C_1) are given by

$$L_1 = \frac{R_0(f_2 - f_1)}{4\pi f_1 f_2}$$

$$= \frac{600(5000 - 2000)}{\pi \times 2000 \times 5000}$$

$$L_1 = 57.32 \text{ mH}$$

$$\frac{L_1}{2} = \frac{57.32}{2} = 28.66 \text{ mH}$$

The shunt inductance (L_2) and capacitance (C_2)

$$L_2 = \frac{R_0}{4\pi(f_2 - f_1)}$$


$$= \frac{600}{4\pi(5000 - 2000)}$$

$$L_2 = 15.92 \text{ mH}$$

$$C_2 = \frac{(f_2 - f_1)}{4\pi R_0 f_1 f_2}$$

$$= \frac{5000 - 2000}{4\pi \times 600 \times 5000 \times 1000}$$

$$C_2 = 0.159 \text{ HF}$$

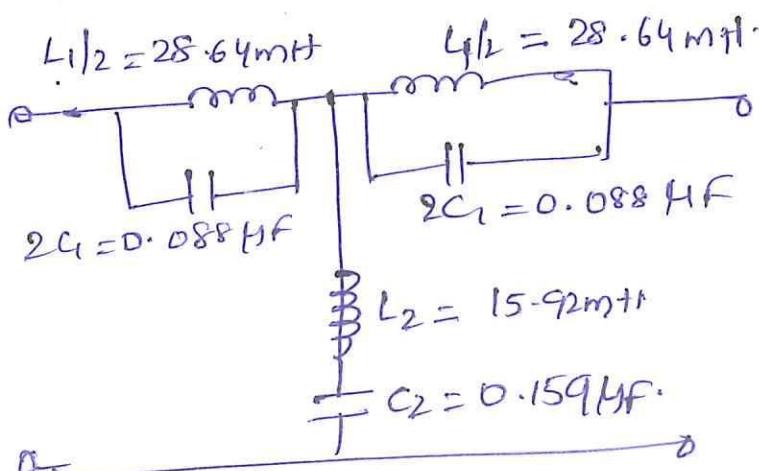

$$C_1 = \frac{1}{4\pi R_0(f_2 - f_1)}$$

$$= \frac{1}{4\pi \times 600 \times (5000 - 2000)}$$

$$= 0.044 \mu\text{F}$$

$$\text{Hence } 2C_1 = 2 \times 0.044 \mu\text{F}$$

$$= 0.088 \mu\text{F}$$

Band stop T.
section filter