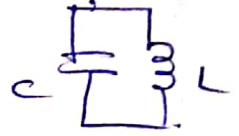


Tuned Amplifiers

①

Tuned amplifier amplifies a particular frequency and rejects all the other frequencies. The load to the tuned ~~amplifier~~ is parallel resonant circuit, as shown fig. This is also known as tank circuit, or tuned circuit. The tuned circuit offers high impedance at resonant frequency. At other frequencies it has low impedance.



In Tx Rx to select a particular channel among the all other channels tuned amplifier is used.

Tuned amplifiers classified into 3 types.

1. Single tuned amplifiers.
2. Double tuned amplifiers.
3. Stagger tuned amplifiers.

Single tuned amplifiers use one parallel resonant circuit as the load impedance in each stage and all the tuned circuits are tuned to the same frequency.


Double tuned amplifiers use two inductively coupled tuned circuits per stage, both the tuned circuits tuned to the same frequency.

Stagger-tuned amplifier is cascading of two single tuned amplifiers, the tuned circuits in each stage tuned to slightly different frequencies. $C_1 C_1 \neq C_2 C_2$

Q-factor of a capacitor

①
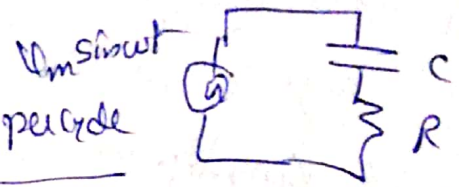
$$Q = \frac{2\pi \times \text{Maximum Energy stored per cycle}}{\text{Energy dissipated per cycle.}}$$



$$E = \frac{1}{2} C V_{\max}^2$$

$$R < \frac{1}{\omega C}$$

$$V_{\max} = I_m X_C = \frac{I_m}{\omega C}$$


$$E = \frac{1}{2} C \frac{I_m^2}{\omega^2 C^2} = \frac{1}{2} \frac{I_m^2}{\omega^2 C} \quad \text{--- (1)}$$

Energy dissipated per cycle = power \times time
 $t = \frac{1}{f}$ power = $\left(\frac{I_m}{\sqrt{2}} \right)^2 R$

$$\text{Energy dissipated per cycle} = \frac{I_m^2 R}{2f} \quad \text{--- (2)}$$

① & ② Substitute in Q factor equation
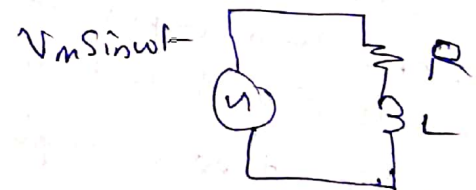
$$Q = 2\pi \left[\frac{\frac{I_m^2}{2\omega^2 C}}{\frac{I_m^2 R}{2f}} \right] = \frac{1}{\omega C R}$$



Q-factor of Inductor

$$E = \frac{1}{2} L I_m^2$$

$$\text{Energy dissipated per cycle} = \frac{I_m^2 R}{2f}$$

$$Q = \frac{2\pi \times \frac{1}{2} L I_m^2}{\frac{I_m^2 R}{2f}} = \frac{2\pi f L}{R} = \frac{\omega L}{R}$$


(1) parallel

$$\boxed{RL} \quad Q = \frac{R}{\omega L}, \quad \boxed{RC} \quad Q = \omega C R$$


(2) series RLC $Q = \omega L / R = 1 / \omega C R$, $\parallel RLC \quad \frac{R}{\omega L} = \omega C R$

Capacitance - Coupled Single tuned amplifiers

(1)

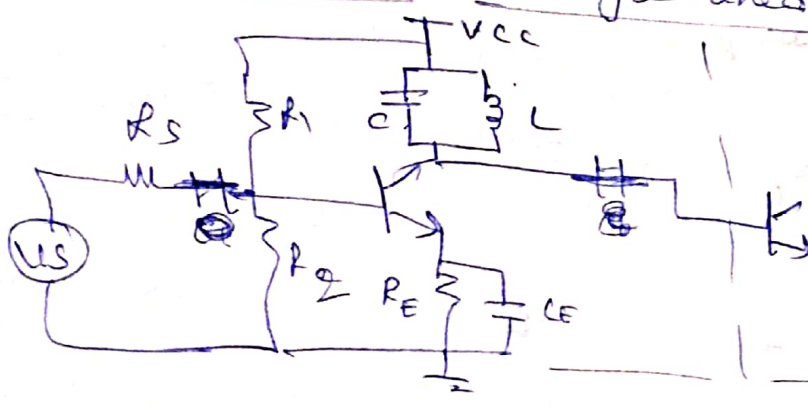


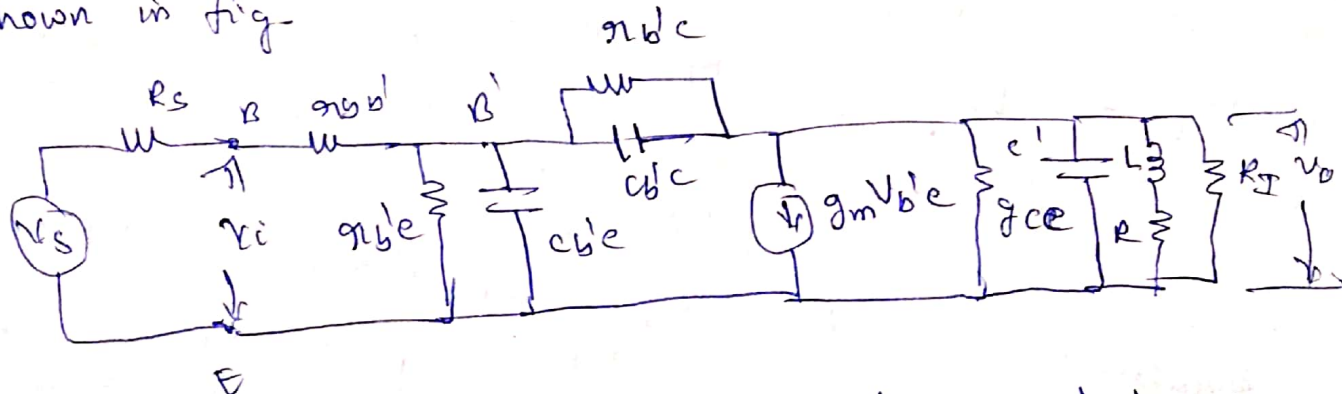Single tuned amplifier analyzed using hybrid \$\pi\$ model shown in fig-



To find Voltage gain and Bandwidth of a single tuned amplifier is shown in fig.

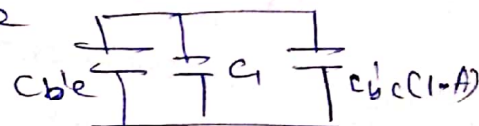Stray Capacitance at the i/p side and o/p side \$C_1\$ and \$C_2\$.



the i/p side capacitance

$$C_{in} = C_{be} + C_1 + C_{bc}(1-A_v)$$

the o/p side capacitance

$$C_{out} = C_2 + C' + C_{bc}\left(\frac{A_v-1}{A_v}\right)$$

(1)

$$g_{ce} = \frac{1}{r_{ce}} = h_{oe} - g_m h_{re} = h_{oe} = \frac{1}{R_o}$$

where \$R_o\$ is the o/p resistance of the current generator \$g_m V_{b'e}\$

Inductor in series with resistor \$\Rightarrow\$

$$Y_i = \frac{1}{R + j\omega L} = \frac{R - j\omega L}{R^2 + \omega^2 L^2} = \frac{R}{R^2 + \omega^2 L^2} - \frac{j\omega L}{R^2 + \omega^2 L^2}$$

$$\frac{1}{R_p + j\omega L_p} = \frac{R}{R^2 + \omega^2 L^2} - \frac{j\omega L}{R^2 + \omega^2 L^2} \Rightarrow R_p = \frac{R^2 + \omega^2 L^2}{R}$$


$$\omega L_p = \frac{R^2 + \omega^2 L^2}{\omega L} \Rightarrow \omega_p = \frac{R^2 + \omega^2 L^2}{\omega^2 L}$$

$$R_p = \frac{R^2 + \omega^2 L^2}{R}$$

$$\omega L_p = \frac{R^2 + \omega^2 L^2}{\omega L}$$

$$L_p = \frac{R^2 + \omega^2 L^2}{\omega^2 L}$$

$$\div \omega^2 L$$

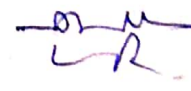$\omega L \gg R$ in 

$$L_p = \frac{R^2}{\omega^2 L} + \frac{\omega^2 L^2}{\omega^2 L}$$

$\frac{R^2}{\omega^2 L}$ can be neglected

$$L_p = L$$

$$R_p = R \left(R + \frac{\omega^2 L^2}{R} \right)$$


$\frac{\omega^2 L^2}{R} \gg R$
R neglected

$$R_p = \frac{\omega^2 L^2}{R}$$

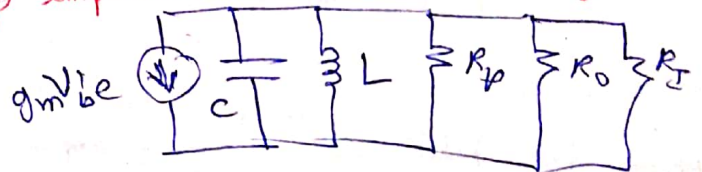(2)

Equivalent circuit of the tuned amplifier shown in fig
 R_T - i/p impedance of the second stage

$$\frac{1}{R_T} = \frac{1}{R_p} + \frac{1}{R_o} + \frac{1}{R_i}$$



$Q_e = \frac{\text{Susceptance of inductance or capacitance } C}{\text{Conductance of shunt resistance } R_T}$

$$Q_e = \omega_0 C R_T = \frac{R_T}{\omega_0 L}$$



$$V_o = -g_m V_{be} Z$$

$$Y = \frac{1}{Z} = \frac{1}{R_T} + \frac{1}{j\omega L} + j\omega C$$

$$= \frac{1}{R_T} \left[1 + \frac{R_T}{j\omega L} + j\omega C R_T \right] \quad \text{Multiply N \& D by } \omega_0$$

$$Y = \frac{1}{R_T} \left[1 + \frac{R_T \omega_0}{j\omega L \cdot \omega_0} + \frac{j\omega C R_T \cdot \omega_0}{\omega_0} \right]$$

$$Y = \frac{1}{R_T} \left[1 + \frac{Q_e \omega_0}{j\omega} + jQ_e \frac{\omega}{\omega_0} \right] = \frac{1}{R_T} \left[1 + 2jQ_e \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right]$$

$$Z = \frac{1}{Y} = \frac{R_t}{1 + j\omega C_e \left[\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right]}$$

(3)

$$s = \frac{\omega}{\omega_0} - 1 \quad 1 + s = \frac{\omega}{\omega_0} \quad \frac{1}{1+s} = \frac{\omega_0}{\omega}$$

$$Z = \frac{R_t}{1 + j\omega C_e \left[1 + s - \frac{1}{1+s} \right]} = \frac{R_t}{1 + j\omega C_e \left[\frac{1 + s^2 + 2s - 1}{1+s} \right]}$$

$$Z = \frac{R_t}{1 + j\omega C_e \left[\frac{s^2 + 2s}{1+s} \right]} = \frac{R_t}{1 + j2s\omega C_e \left[\frac{s+1}{1+s} \right]}$$

$$Z = \frac{R_t}{1 + j2s\omega C_e}$$

$$Z = R_o || R_p || R_i$$

$$V_{be} = \frac{V_i r_{be}}{r_{be} + r_{bb'}}$$

$$V_o = g_m V_{be} Z = \frac{g_m V_i r_{be}}{r_{be} + r_{bb'}}$$

$$A_{v_{mid}} = \frac{V_o}{V_i} = \frac{g_m r_{be}}{r_{be} + r_{bb'}} \cdot Z = \frac{g_m r_{be}}{r_{be} + r_{bb'}} \cdot \frac{R_t}{1 + j2s\omega C_e}$$

At resonance $s = 0$ $\frac{\omega}{\omega_0} = 1$ $\frac{\omega}{\omega_0} = 1$ $\omega = \omega_0$

$$A_{v_{mid}} = \frac{g_m r_{be}}{r_{be} + r_{bb'}} \cdot R_t$$

$$\frac{A_v}{A_{v_{mid}}} = \frac{1}{1 + j2s\omega C_e} = \frac{1}{\sqrt{1 + (2s\omega C_e)^2}}$$

$$\phi = -\tan^{-1}(2s\omega C_e)$$

At resonance

4

$$\frac{A_v}{A_{vres}} = \frac{1}{\sqrt{1 + (2sQ_e)^2}}$$

$$1 + (2sQ_e)^2 = 2$$

$$2sQ_e = 1$$

$$s = \frac{1}{2Q_e}$$

$$Q_e = \frac{R_L}{\omega_0 L} = \omega_0 C R_L \quad \text{in parallel tuned circuit}$$

$$2s = \frac{1}{Q_e} \Rightarrow \boxed{s = \frac{1}{2Q_e}}$$

The 3dB Bandwidth $\Delta\omega = \omega_2 - \omega_1$


$$s + s \quad \frac{\omega_2 - \omega_0}{\omega_0} + \frac{\omega_0 - \omega_1}{\omega_0} = 2s$$

$$\Delta\omega = 2s \quad \Delta\omega = 2s\omega_0$$

$$\boxed{\Delta\omega = \frac{\omega_0}{Q_e}}$$

$\omega_0 \rightarrow$ resonant frequency

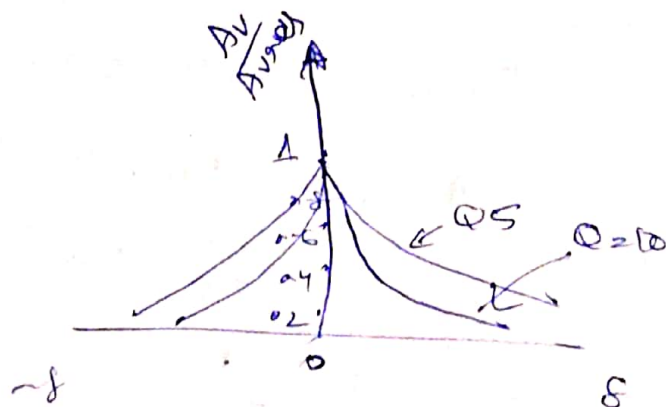$Q_e \rightarrow$ effective Quality factor



effect of cascading single-tuned amplifiers on Bandwidth

$$\frac{A}{A_{res}} = \frac{1}{\sqrt{1 + (2\delta Q_e)^2}}$$

$$\left[\frac{A}{A_{res}} \right]^n = \left[\frac{1}{\sqrt{1 + (2\delta Q_e)^2}} \right]^n = \frac{1}{\sqrt{2}}$$

$$\left[\sqrt{1 + (2\delta Q_e)^2} \right]^n = \sqrt{2}$$

Squaring on both sides.

$$\left[1 + (2\delta Q_e)^2 \right]^n = 2$$

$$(2\delta Q_e)^2 = 2^{\frac{1}{n}} - 1$$

$$2\delta Q_e = \sqrt{2^{\frac{1}{n}} - 1}$$

$$2 \left[\frac{f - f_0}{f_0} \right] Q_e = \sqrt{2^{\frac{1}{n}} - 1}$$

$$f - f_0 = \frac{f_0}{2Q_e} \sqrt{2^{\frac{1}{n}} - 1}$$

$$f_2 - f_0 = \frac{f_0}{2Q_e} \sqrt{2^{\frac{1}{n}} - 1} \quad \text{--- (1)}$$

$$f_0 - f_1 = \frac{f_0}{2Q_e} \sqrt{2^{\frac{1}{n}} - 1} \quad \text{--- (2)}$$

$$f_2 - f_0 + f_0 - f_1$$

Bandwidth

$$f_2 - f_1 = \frac{f_0}{2Q_e} \sqrt{2^{\frac{1}{n}} - 1} + \frac{f_0}{2Q_e} \sqrt{2^{\frac{1}{n}} - 1}$$

$$f_2 - f_1 = \frac{f_0}{Q_e} \sqrt{2^{\frac{1}{n}} - 1}$$

vs the single stage tuned amplifiers

$$n=2$$

$$= \sqrt{2^{\frac{1}{2}} - 1} = 0.643$$

$$n=3$$

$$= \sqrt{2^{\frac{1}{3}} - 1} = 0.51$$

Bandwidth of n stages

$$B_n = B_1 \sqrt{2^{\frac{1}{n}} - 1}$$

as n increases
Bandwidth reduces



Effect of cascading double tuned amplifiers

The 3dB bandwidth of the cascaded double-tuned amplifier is $B_{2n} = B_2 \left[2^{1/n} - 1 \right]^{1/n}$.

where B_2 is the 3dB bandwidth of the single stage - double - tuned amplifier and n is the number of identical stages connected in cascade.

Double tuned amplifier

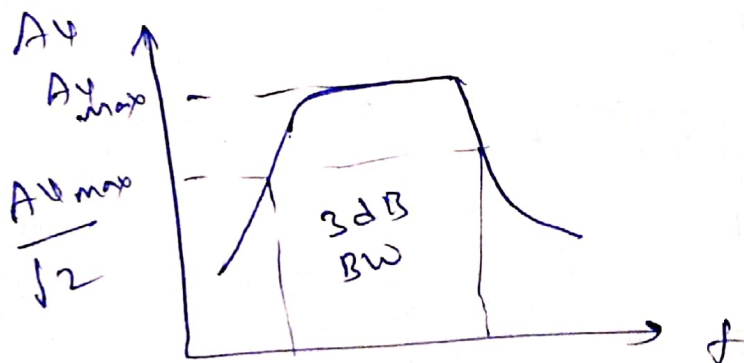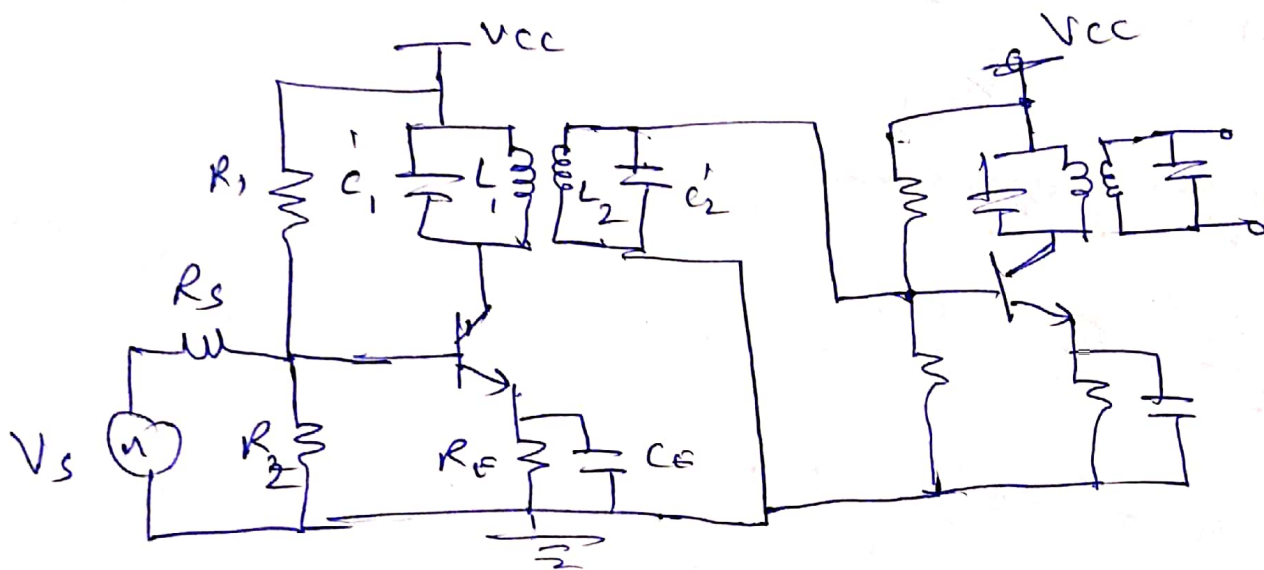It uses two inductively coupled tuned circuits per stage, both the tuned circuits being tuned to the same frequency.



Frequency response is flat and has steeper ends ~~and~~ and Gain Bandwidth product is large.

stagger tuned amplifiers

(7)


Double tuned amplifiers used to increase the Bandwidth.
The alignment of double tuned amplifiers is difficult.
So stagger tuned amplifiers is used.

In stagger tuned amplifier has two single tuned Cascade amplifiers. Each stage has certain Bandwidth.
The resonant frequency of the two tuned circuits are so adjusted that they are separated by an amount equal to the bandwidth of each stage.
Since the resonant frequencies are displaced or staggered, there are known as stagger-tuned circuits.

$\Delta_1 = \text{Bandwidth of 1st stage}$

$\Delta_2 = \text{Bandwidth of 2nd stage}$

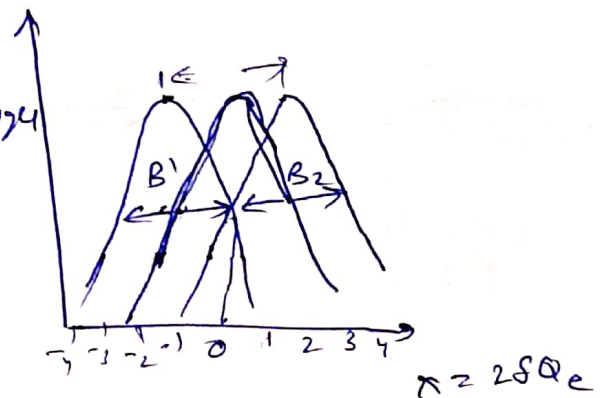$\Delta_1 = \Delta_2 = \Delta$ Bandwidth of stagger tuned amplifiers.



the stagger tuned amplifier
bandwidth $\sqrt{2} \Delta$

$$\frac{A_v}{A_{vres}} = \frac{1}{1 + j2\delta Q_e} = \frac{1}{1 + jx} \quad \text{where } x = 2\delta Q_e \text{ for single tuned amplifiers}$$

$$\text{Bandwidth } \Delta = \frac{f_0}{Q_e} \quad \delta = \frac{1}{2Q_e}$$

δ fractional deviation from resonant frequency. $BW = 2\delta f_0$
In stagger tuned amplifier one stage tuned to f_0 below f_0
and second stage tuned to f_0 above f_0 .

w.

so the corresponding selectivity function of circuits

$$\left[\frac{A}{A_{res}} \right]_1 = \frac{1}{1 + j(x-1)} \quad \left[\frac{A}{A_{res}} \right]_2 = \frac{1}{1 + j(x+1)}$$

$$x = 2\delta Q_e.$$

$$\left[\frac{A}{A_{res}} \right]_{pair} = \left[\frac{A}{A_{res}} \right]_1 \left[\frac{A}{A_{res}} \right]_2$$

$$= \frac{1}{1 + j(x-1)} \cdot \frac{1}{1 + j(x+1)} = \frac{1}{2 - x^2 + 2jx}$$

$$\left| \frac{A}{A_{res}} \right|_{pair} = \frac{1}{\sqrt{(2-x^2)^2 + (2x)^2}} = \frac{1}{\sqrt{4 + 4x^2 - 4x^2 + x^4}}$$

$$= \frac{1}{\sqrt{4 + x^4}} = \frac{1}{\sqrt{4 + (2\delta Q_e)^4}} = \frac{1}{2\sqrt{1 + 4\delta_0^4 Q_0^4}}$$

for stagger
tuned

for single stage tuned amplifiers

$$\frac{A_v}{A_{res}} = \frac{1}{\sqrt{1 + (2\delta Q_0)^2}}$$

In stagger tuned amplifier the overall voltage gain where δ_0 is the value of δ referred to new frequency and Q_0 is the value of Q_e for each circuit referred to ω_0

In stagger tuned amplifier gain decreases.