


## UNIT-II - GATE LEVEL MINIMIZATION

### K-Map :-

- The K-map or Karnaugh map is a chart or a graph composed of an arrangement of adjacent cells, each representing a particular combination of variable in SOP form.
- Any boolean expression can be expressed in standard & canonical SOP & POS form.
- A standard SOP form is one in which a number of product terms, each one of which contains all variables of the function either in complemented form & normal form.
- Similarly for POS form also.
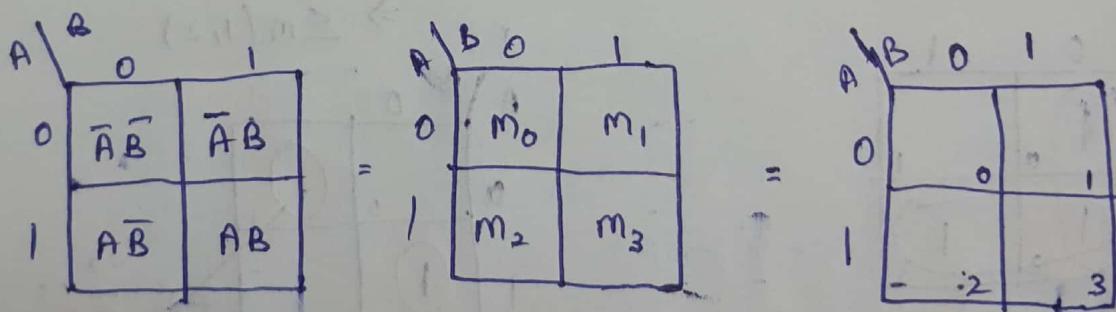
### Two Variable K-map :-

- A Two Variable K-map has  $2^2 = 4$  Squares.
- These squares are called cells. Each square & cell on the K-map represents the minterm.




- To minimize the boolean expression we look for adjacent cells & squares having i.e. minterms adjacent to each other & we combine them to form larger squares to eliminate some variables.
- Two squares are said to be adjacent if they differ in only one variable.


②

→ A minterm can be combined with any numbers of minterms adjacent to it to form larger squares.

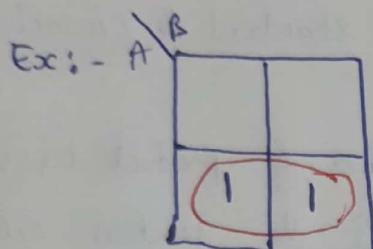
→ Two minterm which are adjacent to each other can be combined to form a larger & bigger square called a Q square & a pair.




✓  
we can group

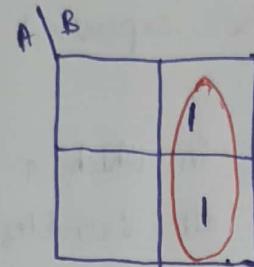

✓  
we can group

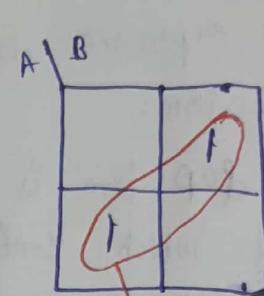

X  
grouping not possible

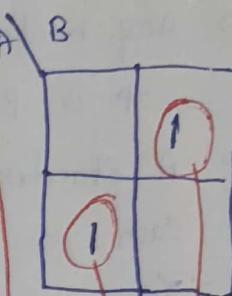


✓  
we can group single

### Problems:-


⑤ Evaluate the following using 2-Variable K-map :-

①  $F = \sum m(0, 2, 3)$

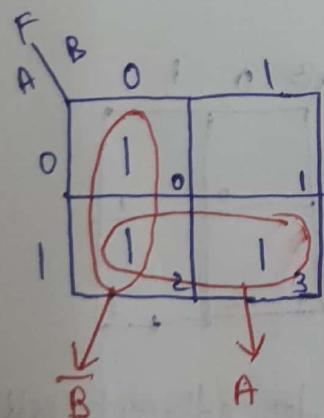

$F = \bar{B} + A$


②  $F = A\bar{B} + \bar{A}B$

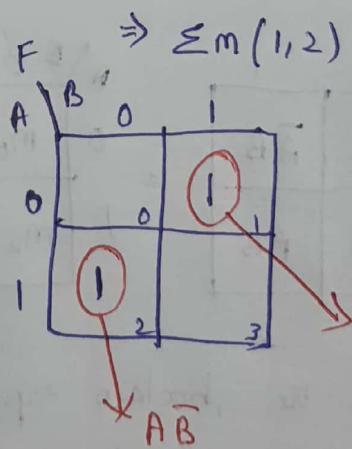

$F = A\bar{B} + \bar{A}B$

$F = A \oplus B$
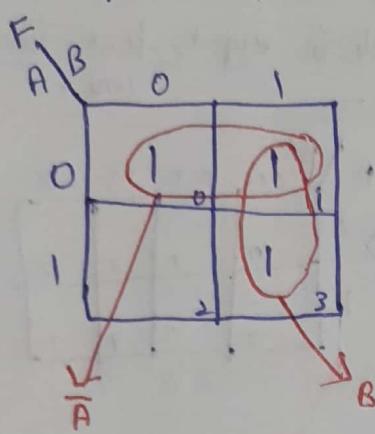
$$\textcircled{3} \quad F = \bar{A}\bar{B} + \bar{A}B + AB$$




$$\begin{aligned} F &= \bar{A}\bar{B} + \bar{A}B + AB \\ &\Rightarrow m_0 + m_1 + m_3 \\ &\Rightarrow \sum m(0, 1, 3) \end{aligned}$$

$$\therefore F = \bar{A} + B.$$

$$\textcircled{4} \quad F = (A+B)(\bar{A}+B)(\bar{A}+\bar{B})$$

$\equiv$  The given expression is in POS form. Hence write the minterms of the expression.
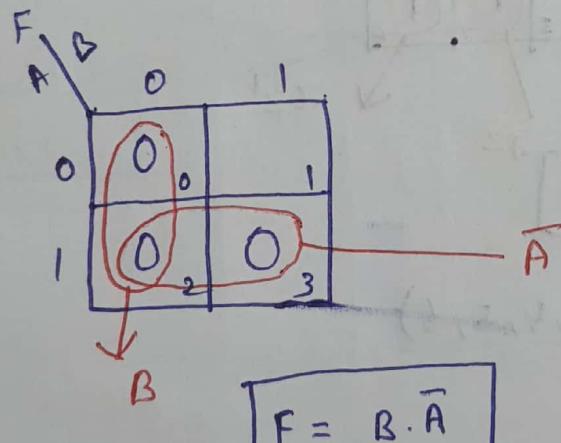
$$\begin{aligned} F &\Rightarrow (A+B)(\bar{A}+B)(\bar{A}+\bar{B}) \\ &\Rightarrow \prod M(0, 2, 3) \end{aligned}$$



$$F = B \cdot \bar{A}$$

$$\textcircled{5} \quad F = \prod M(0, 1, 3) \quad \underline{\text{H.W}}$$

(4)

3- Variable K-map :- It has  $2^3 = 8$  square cells.  
Maximum grouping possible is eight, four, two, one.

	BC	00	01	11	10
A	0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}C$	$\bar{A}BC$	$\bar{A}B\bar{C}$
	1	$A\bar{B}\bar{C}$	$A\bar{B}C$	$ABC$	$A\bar{B}\bar{C}$


	BC	00	01	11	10
A	0	$m_0$	$m_1$	$m_3$	$m_2$
	1	$m_4$	$m_5$	$m_7$	$m_6$

	BC	00	01	11	10
A	0	0	1	3	2
	1	4	5	7	6


① Evaluate the following using 3 Variable K-map :-

①  $F(x,y,z) = \sum m(3,4,6,7)$

Ans  $\sum m(3,4,6,7)$

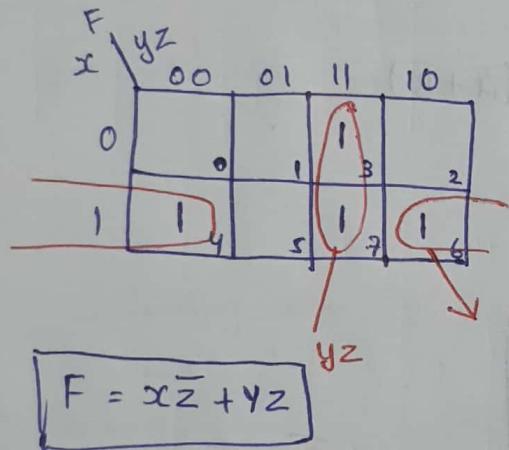

②  $F(x,y,z) = \sum m(0,2,4,5,6)$

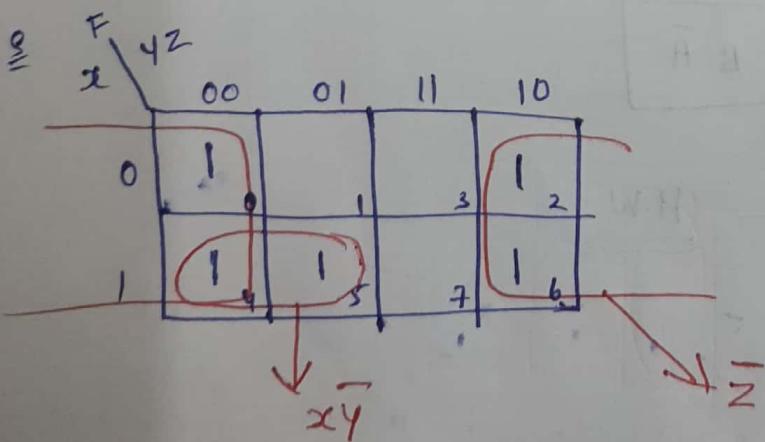

$F = x\bar{y} + \bar{z}$

$$③ F = A'c + A'B + AB'C + BC$$

$\Leftrightarrow$  Solve the given expression  $F$  as it minterms doesn't have all the variables.

$$F = A'(B+B')C + A'B(C+C') + AB'C + (A+A')BC$$

$$\Rightarrow A'(BC+BC') + A'BC + A'BC' + AB'C + ABC + A'BC$$


$$\Rightarrow \underline{A'BC} + \underline{A'BC'} + \underline{A'BC} + \underline{AB'C} + \underline{ABC} + \underline{A'BC}$$

$\Rightarrow$  eliminate the repeated terms

$$\Rightarrow A'BC + A'BC' + A'BC' + AB'C + ABC$$


$$\Rightarrow m_3 + m_1 + m_2 + m_5 + m_7$$

$$\sum m (1, 2, 3, 5, 7)$$

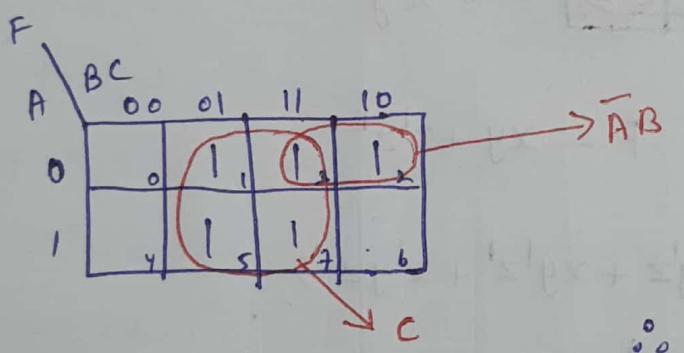

$$\therefore F = \bar{A}B + C$$
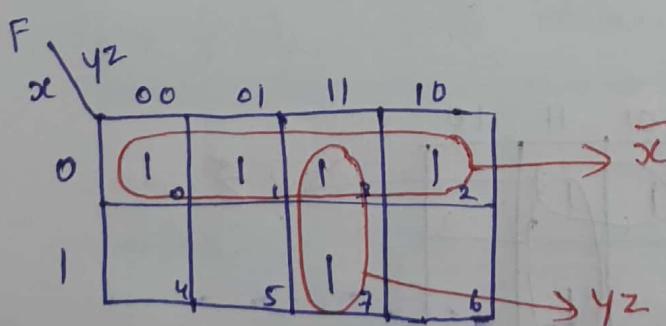
$$④ F(x, y, z) = \sum m (0, 1, 2, 3, 7)$$



$$F = \bar{x} + yz$$

(6)

$$\textcircled{5} \quad F(x, y, z) = xy + x'y'z' + x'y'z$$


$\Leftrightarrow$  Solve for variables in minterms

$$\Rightarrow xy(z+z') + x'y'z' + x'y'z$$

$$\Rightarrow xyz + x'yz' + x'y'z' + x'y'z$$

$$\Rightarrow m_7 + m_6 + m_0 + m_2$$

$$\Rightarrow \sum m(0, 2, 6, 7)$$

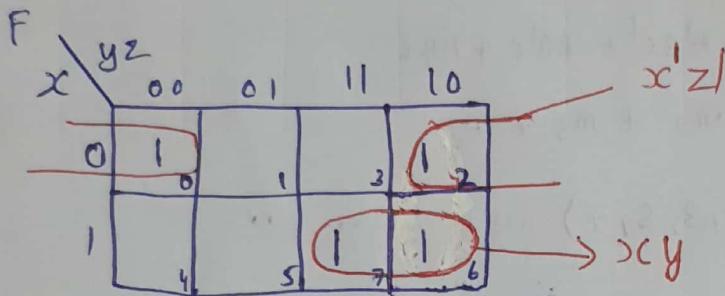


$$F = xy + x'y'z'$$

$$\textcircled{6} \quad F(x, y, z) = xyz + x'y'z + xy'z' + x'y'z ?$$

$$\Leftrightarrow F = \sum m(1, 3, 4, 7)$$

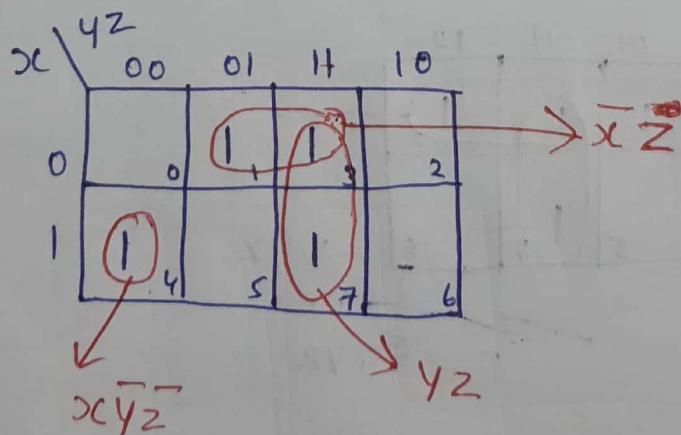(1, 3, 4, 7) minterms from above expression.



$$F = x\bar{y}\bar{z} + \bar{x}z + yz$$

## Practice problems on 3-Variable K-map :-

- ①  $F(x,y,z) = \sum m(3,4,6,7)$
- ②  $F(x,y,z) = \sum m(1,2,4,7)$
- ③  $F(x,y,z) = \sum m(0,2,3,6,7)$
- ④  $F(x,y,z) = \sum m(0,2,3,4,6)$
- ⑤  $F(x,y,z) = \sum m(3,5,6,7)$
- ⑥  $F(x,y,z) = \sum m(0,1,2,5,7)$
- ⑦  $F(x,y,z) = \sum m(1,2,3,6,7)$
- ⑧  $F(x,y,z) = \sum m(0,1,6,7)$
- ⑨  $F(x,y,z) = \sum m(0,1,3,4,5)$
- ⑩  $F(x,y,z) = \sum m(1,3,5,7)$
- ⑪  $F(x,y,z) = \sum m(1,4,5,6,7)$
- ⑫  $F(x,y,z) = x'y' + yz + x'y'z'$
- ⑬  $F(x,y,z) = x'y + yz' + y'z'$

### DEFINITIONS:-

- ① Pair :- Group of two adjacent minterms. A pair eliminates one variable in output expression.
- ② Quad :- Group of four adjacent minterms. A Quad eliminates two variables in output expression.
- ③ Octet :- Group of eight adjacent minterms. An octet eliminates three variables in output expression.
- ④ Redundant group :- A redundant group is a group in which all the elements in this group are covered by some other group.

⑤

4- Variable K-map :- It has  $2^4 = 16$  Squares & Cells.


	Yz	Wx	00	01	11	10
00	W'x'y'z	W'x'y'z	W'x'y'z	W'x'y'z		
01	W'x'y'z	W'x'y'z	W'x'yz	W'x'yz		
11	Wx'y'z	Wx'y'z	Wx'yz	Wx'yz		
10	Wx'y'z	Wx'y'z	Wx'yz	Wx'yz		

	Yz	Wx	00	01	11	10
00			m <sub>0</sub>	m <sub>1</sub>	m <sub>3</sub>	m <sub>2</sub>
01			m <sub>4</sub>	m <sub>5</sub>	m <sub>7</sub>	m <sub>6</sub>
11			m <sub>12</sub>	m <sub>13</sub>	m <sub>15</sub>	m <sub>14</sub>
10			m <sub>8</sub>	m <sub>9</sub>	m <sub>11</sub>	m <sub>10</sub>


	Yz	Wx	00	01	11	10
00			0	1	3	2
01			4	5	7	6
11			12	13	15	14
10			8	9	11	10

⑥ Evaluate the following using 4 Variable K-map:-

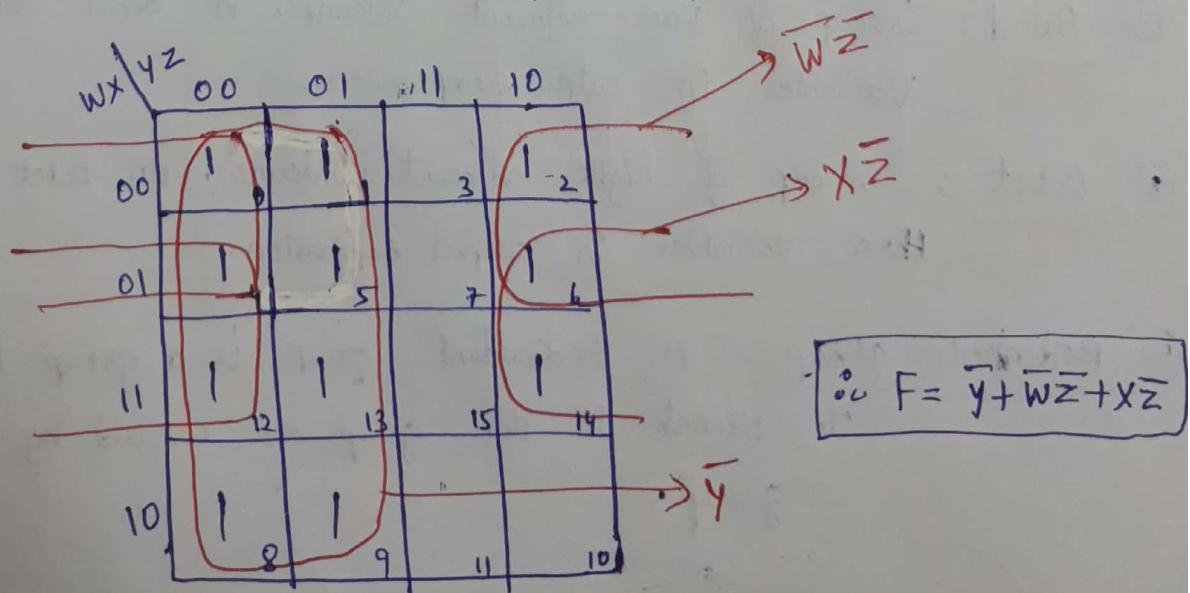①  $F(w, x, y, z) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$



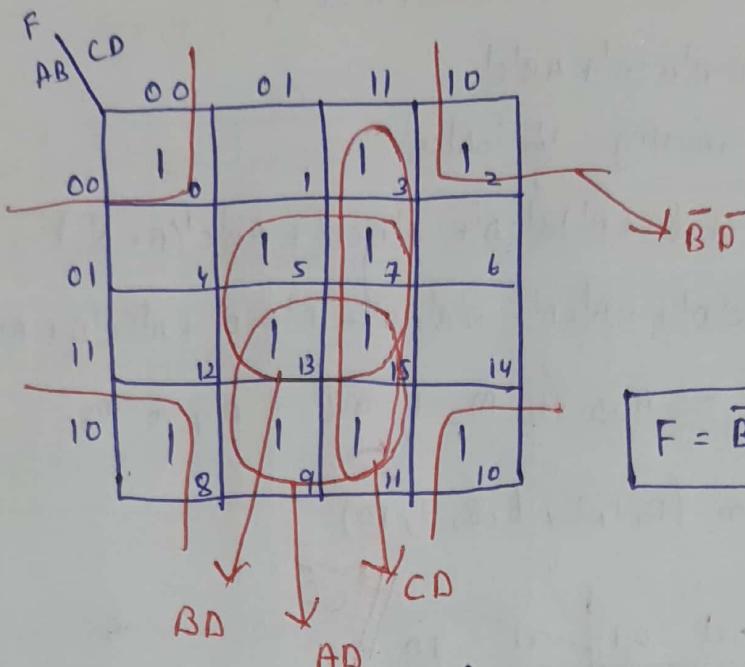
$$\textcircled{8} \quad F(A, B, C, D) = \sum (0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$$




$$F = \bar{B}\bar{D} + BD + AD + CD$$
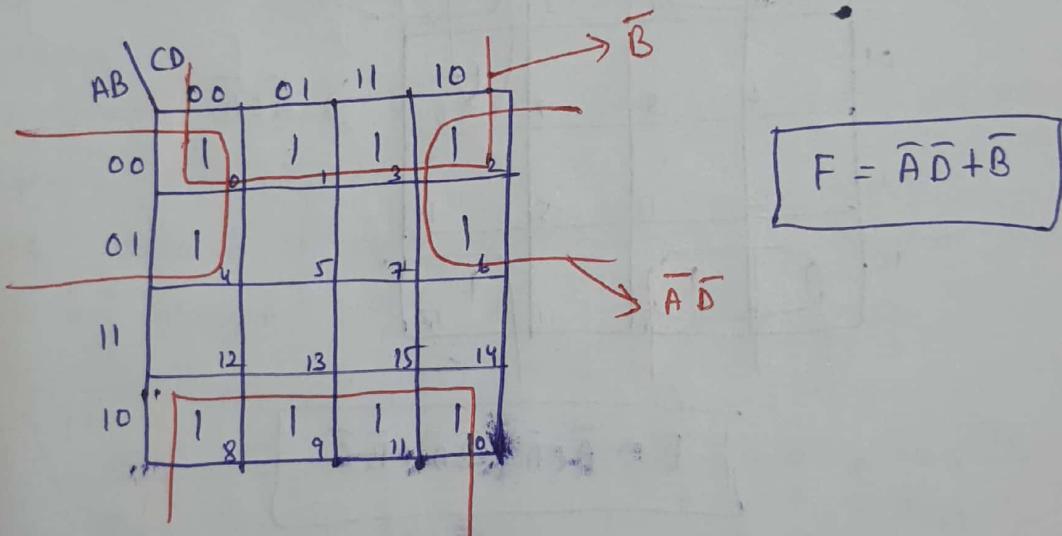
$$\textcircled{3} \quad F = \sum m(0, 1, 2, 3, 4, 6, 8, 9, 10, 11)$$



$$F = \bar{A}\bar{D} + \bar{B}$$
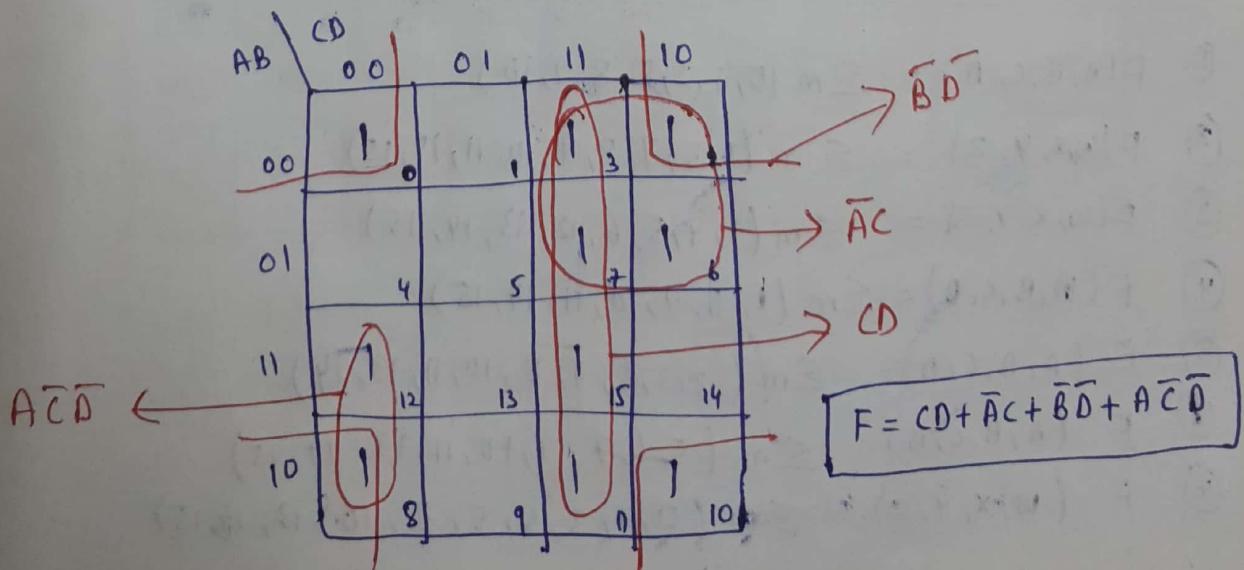
$$\textcircled{4} \quad F(A, B, C, D) = \sum m(0, 2, 3, 6, 7, 8, 10, 11, 12, 15)$$



$$F = CD + \bar{A}C + \bar{B}\bar{D} + A\bar{C}\bar{D}$$

(10)

$$⑤ F(A, B, C, D) = A'B'C'D + B'C'D' + A'B'C'D' + A'B'C'D' ?$$

$$\stackrel{?}{=} F = A'B'C'D + B'C'D' + A'B'C'D' + A'B'C'D'$$


add the missing variables.

$$F = A'B'C'D(D+D') + (A+A')B'C'D + A'B'C'D' + A'B'C'D'(D+D')$$

$$\Rightarrow A'B'C'D + A'B'C'D + A'B'C'D + A'B'C'D + A'B'C'D + A'B'C'D + A'B'C'D$$

$$\Rightarrow m_1 + m_0 + m_{10} + m_2 + m_6 + m_9 + m_8$$
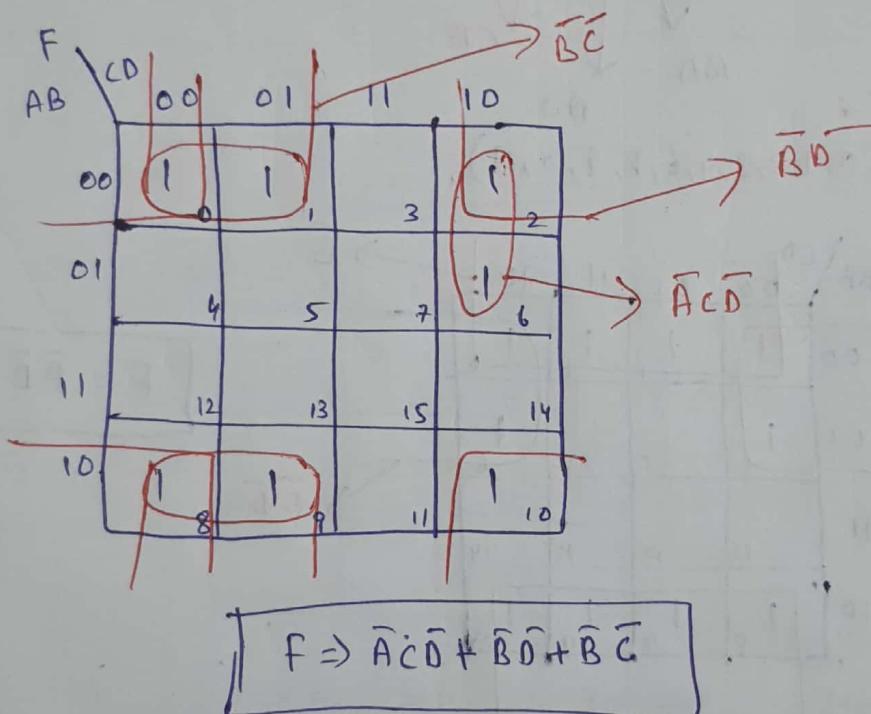
$$\Rightarrow \sum m (0, 1, 2, 6, 8, 9, 10)$$



Practice problems on 4-Variable K-maps:-

$$① F(A, B, C, D) = \sum m (0, 1, 2, 5, 8, 9, 10)$$

$$② F(w, x, y, z) = \sum m (0, 5, 7, 8, 9, 10, 11, 14, 15)$$

$$③ F(w, x, y, z) = \sum m (1, 4, 5, 6, 12, 13, 14, 15)$$

$$④ F(A, B, C, D) = \sum m (1, 5, 9, 10, 11, 14, 15)$$

$$⑤ F(A, B, C, D) = \sum m (2, 3, 6, 7, 8, 10, 11, 13, 14)$$

$$⑥ F(A, B, C, D) = \sum m (5, 6, 7, 9, 10, 11, 13, 14, 15)$$

$$⑦ F(w, x, y, z) = \sum m (0, 1, 3, 4, 5, 7, 10, 13, 14, 15)$$

5-Variable K-Map :- It consists of  $2^5 = 32$  cells.

		A = 0				
		DE	00	01	11	10
BC	00		A $\bar{B}\bar{C}\bar{D}\bar{E}$	A $\bar{B}\bar{C}D\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$
			A $\bar{B}\bar{C}\bar{D}\bar{E}$	A $\bar{B}\bar{C}D\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$
BC	01		A $\bar{B}\bar{C}\bar{D}\bar{E}$	A $\bar{B}\bar{C}D\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$
			A $\bar{B}\bar{C}\bar{D}\bar{E}$	A $\bar{B}\bar{C}D\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$
BC	11		A $\bar{B}\bar{C}\bar{D}\bar{E}$	A $\bar{B}\bar{C}D\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$
			A $\bar{B}\bar{C}\bar{D}\bar{E}$	A $\bar{B}\bar{C}D\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$
BC	10		A $\bar{B}\bar{C}\bar{D}\bar{E}$	A $\bar{B}\bar{C}D\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$
			A $\bar{B}\bar{C}\bar{D}\bar{E}$	A $\bar{B}\bar{C}D\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$

		A = 1				
		DE	00	01	11	10
BC	00		A $\bar{B}\bar{C}\bar{D}\bar{E}$	A $\bar{B}\bar{C}D\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$
			A $\bar{B}\bar{C}\bar{D}\bar{E}$	A $\bar{B}\bar{C}D\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$
BC	01		A $\bar{B}\bar{C}\bar{D}\bar{E}$	A $\bar{B}\bar{C}D\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$
			A $\bar{B}\bar{C}\bar{D}\bar{E}$	A $\bar{B}\bar{C}D\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$
BC	11		A $\bar{B}\bar{C}\bar{D}\bar{E}$	A $\bar{B}\bar{C}D\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$
			A $\bar{B}\bar{C}\bar{D}\bar{E}$	A $\bar{B}\bar{C}D\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$
BC	10		A $\bar{B}\bar{C}\bar{D}\bar{E}$	A $\bar{B}\bar{C}D\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$
			A $\bar{B}\bar{C}\bar{D}\bar{E}$	A $\bar{B}\bar{C}D\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$	A $\bar{B}C\bar{D}\bar{E}$

- It maps for more than 4 Variables are not simple as to use.
- A 5 Variable K-map needs  $2^n = 2^5 = 32$  squares.
- When number of Variables increases, number of squares also increases.
- It consists of Two - 4 Variable K-maps. It has 5 variables namely A, B, C, D and E.
- Here Variable A distinguishes blur two 4 Variable K-maps.
- It is arranged in 4 rows & 8 columns.


		A = 0				
		DE	00	01	11	10
BC	00		$m_0$	$m_1$	$m_3$	$m_2$
			$m_4$	$m_5$	$m_7$	$m_6$
BC	01		$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
			$m_8$	$m_9$	$-m_{11}$	$m_{10}$
BC	11					
BC	10					

		A = 1				
		DE	00	01	11	10
BC	00		$m_{16}$	$m_{17}$	$m_{19}$	$m_{18}$
			$m_{20}$	$m_{21}$	$m_{23}$	$m_{22}$
BC	01		$m_{28}$	$m_{29}$	$m_{31}$	$m_{30}$
			$m_{24}$	$m_{25}$	$m_{27}$	$m_{26}$
BC	11					
BC	10					

- minterms 0 to 15 belong to  $A=0$
- minterms 16 to 31 belong to  $A=1$ .

②

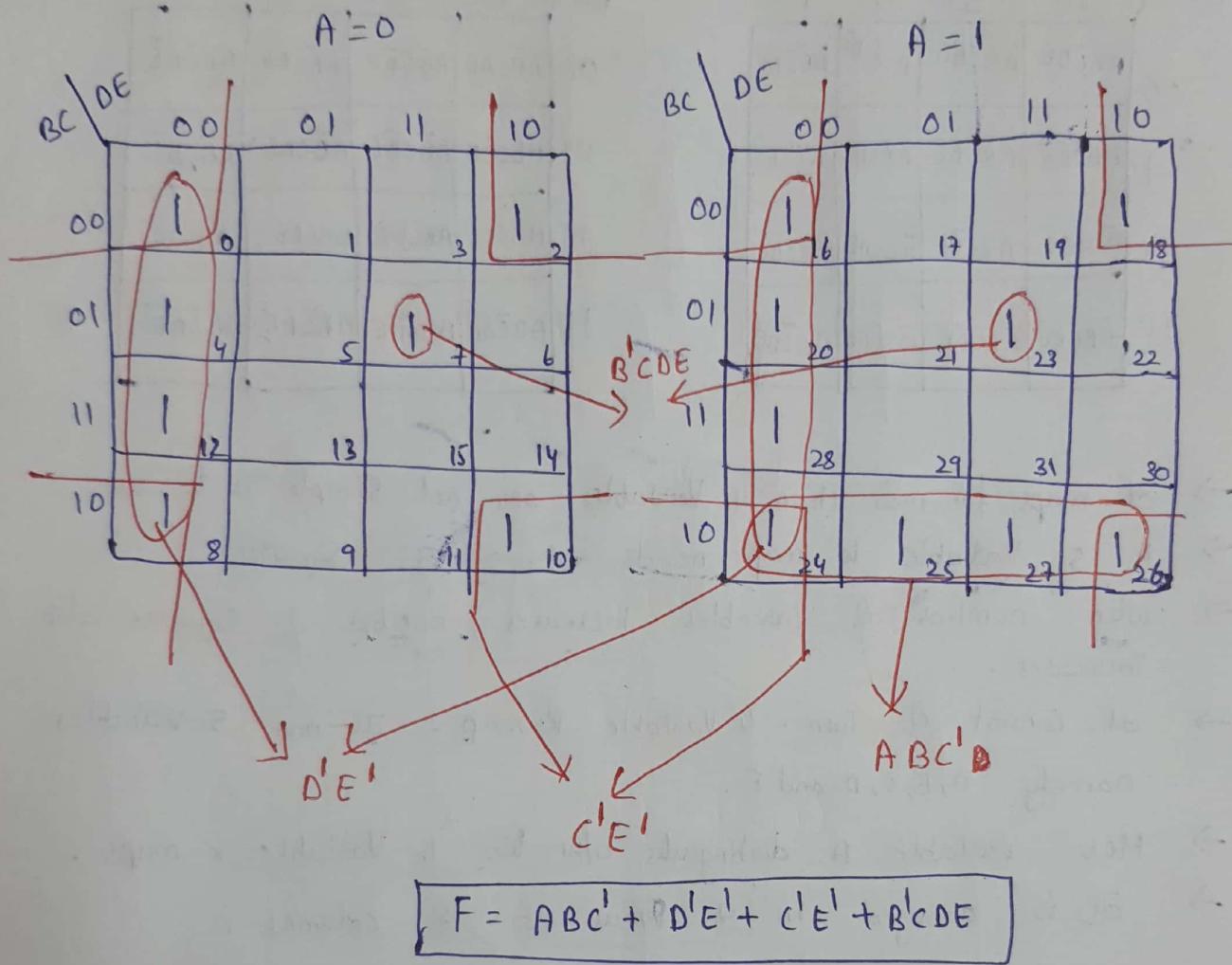③ Solve  $F(A, B, C, D, E) = \sum m(0, 2, 4, 7, 8, 10, 12, 16, 18, 20, 23, 24, 25, 26, 27, 28)$ .



H.W ①  $F(A, B, C, D, E) = \sum m(0, 2, 3, 4, 5, 6, 7, 11, 15, 16, 18, 19, 23, 27, 31)$ .


## K-Maps using POS form :-

① 3 Variable K-map

$$\textcircled{2} \quad F(A, B, C) = (A+B+C)(A+B+\bar{C})(A+\bar{B}+\bar{C})(\bar{A}+B+C)(\bar{A}+\bar{B}+C)(\bar{A}+\bar{B}+\bar{C})$$

≡ write the minterms of given literals

$$\Rightarrow \pi M(0, 1, 3, 4, 6, 7)$$

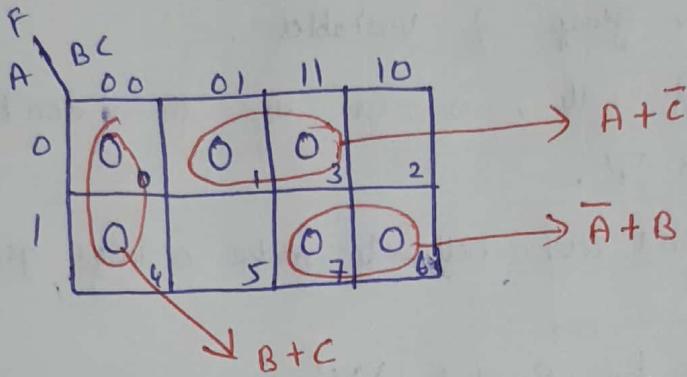

$$F(A, B, C) = (B+C)(\bar{A}+B)(A+\bar{C})$$


$$\textcircled{3} \quad F(A, B, C) = (A+B+\bar{C})(\bar{A}+\bar{B}+C)(A+B+C)(A+\bar{B}+C)(A+\bar{B}+\bar{C}).$$

② 4 Variable K-map

$$\textcircled{4} \quad F(A, B, C, D) = (A+B+C+D)(A+B+C+\bar{D})(A+B+\bar{C}+D)(A+\bar{B}+C+D) \\ (A+\bar{B}+C+\bar{D})(A+\bar{B}+\bar{C}+\bar{D})(\bar{A}+\bar{B}+\bar{C}+\bar{D})(\bar{A}+B+\bar{C}+D)$$

≡ write the minterms from the expression

$$F = \pi M(0, 1, 2, 4, 5, 7, 15, 10)$$

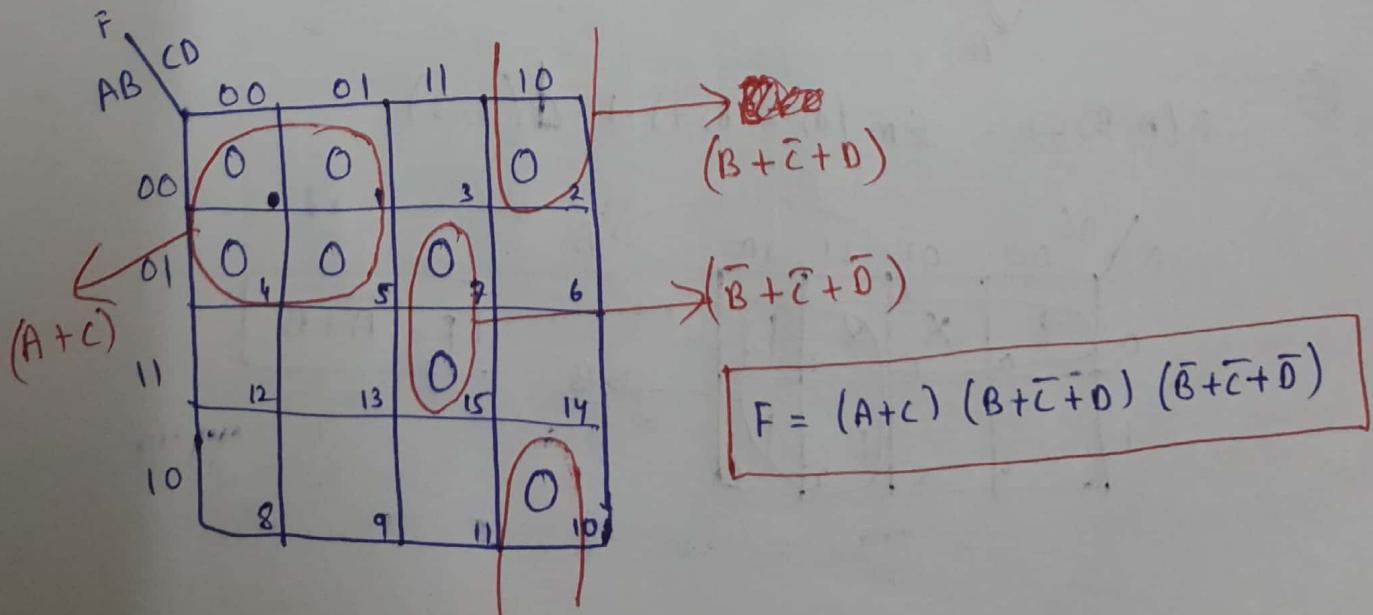

(14)

Practice :- ①  $F(A, B, C, D) = \pi M \{0, 2, 6, 7, 8, 10, 12, 13\}$


②  $F(A, B, C, D) = \pi M \{2, 3, 4, 5, 6, 7, 12, 13\}$

Don't Cares in K-Map :-


- Don't Care Condition says that we can use the blank cells of K-map to make a group of variables.
- To make a group of cells, we can use the "don't care" cell as either '0' or '1'.
- We mainly use don't care cell to make a large group of cells.
- It is represented by symbol 'X'.

⑥ Solve the given expressions :-

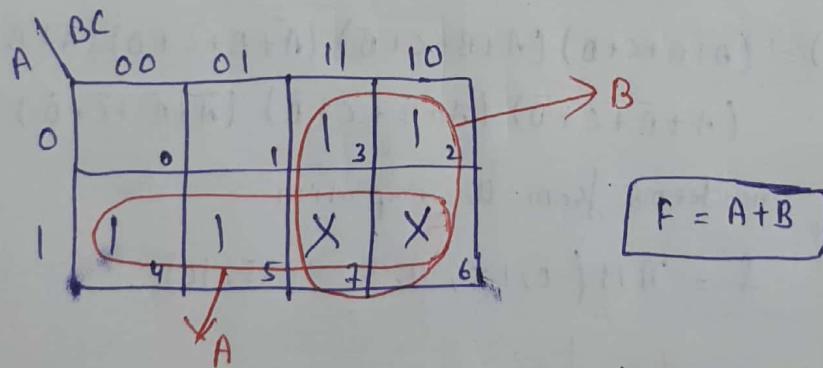①  $F(A, B, C) = \sum m(2, 3, 4, 5) + d(6, 7)$



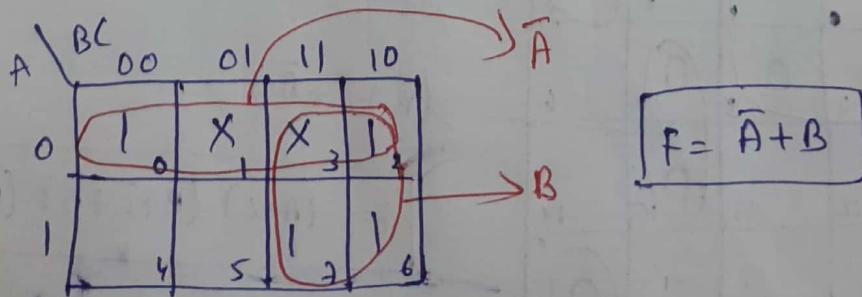②  $F(A, B, C) = \sum m(0, 2, 6, 7) + d(1, 3)$



$$\textcircled{8} \quad F(A, B, C, D) = \sum m(1, 2, 6, 7, 8, 13, 14, 15) + d(3, 5, 12).$$

AB\CD	00	01	11	10
00	0	1, 1	X, 3	1, 2
01	4	X, 5	1, 7	1, 6
11	X, 10	1, 13	1, 15	1, 14
10	1, 8	9	11	10

$$F = A\bar{C}\bar{D} + AB + \bar{A}D + \bar{A}C$$

\textcircled{8} Minimize the given expression  $F(A, B, C, D) = m(0, 1, 2, 3, 4, 5) + d(10, 11, 12, 13, 14, 15)$  in POS form.

Given The POS form of the given function is given by other terms of the given expression

$$F(A, B, C, D) = \prod M(6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15)$$

AB\CD	00	01	11	10
00	0	1	3	2
01	4	5	0, 7	0, 6
11	X, 12	X, 13	X, 15	X, 14
10	0, 8	0, 9	X, 11	X, 10

$$F = \bar{A}(\bar{B} + \bar{C})$$

(16)

H.W


$$\textcircled{1} \quad F(A, B, C, D) = \sum m(1, 3, 7, 11, 15) + d(0, 2, 5)$$

$$\textcircled{2} \quad F(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 6, 9, 10) + d(7, 11, 12, 13, 15)$$

$$\textcircled{3} \quad F(A, B, C, D) = \prod M(1, 2, 6, 7, 8, 13, 14, 15) + d(3, 5, 12)$$


NAND - Realization :-

① NOT :-

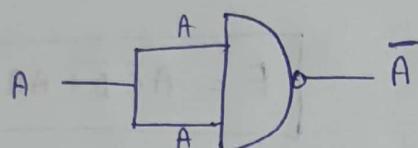


$$\{\because \overline{A \cdot A} = \bar{A}\}$$


② AND gate :-

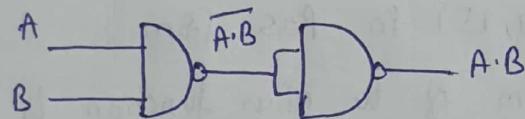

③ OR gate :-

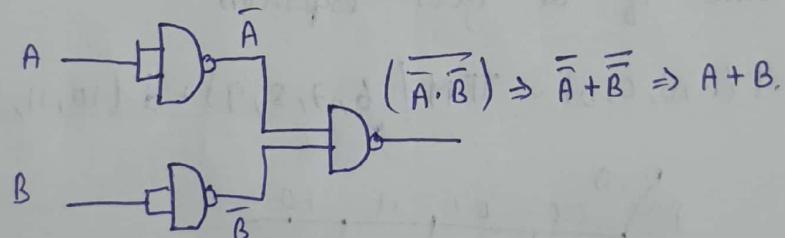


④ Ex-OR gate :-

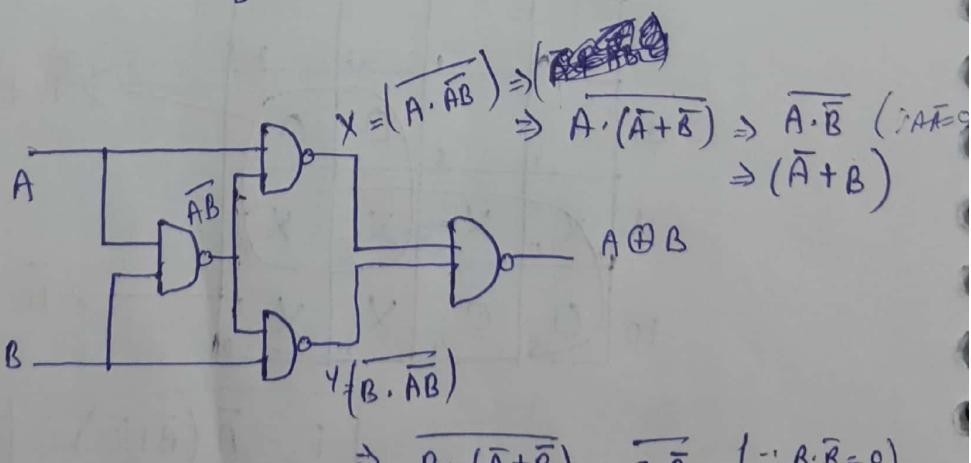

$$\Rightarrow \overline{X \cdot Y} \Rightarrow (\overline{\bar{A} + B})(\overline{\bar{B} + A}) \Rightarrow \overline{\bar{A}\bar{B} + \bar{A}A + B\bar{B} + BA} \Rightarrow \overline{\bar{A}\bar{B} + AB} = \overline{A \oplus B} = \underline{A \oplus B}$$

NOTE  
 To implement  
 Ex-OR gate using  
 NAND gate  
 it requires  
 4-Nand gates




## EX-NOR

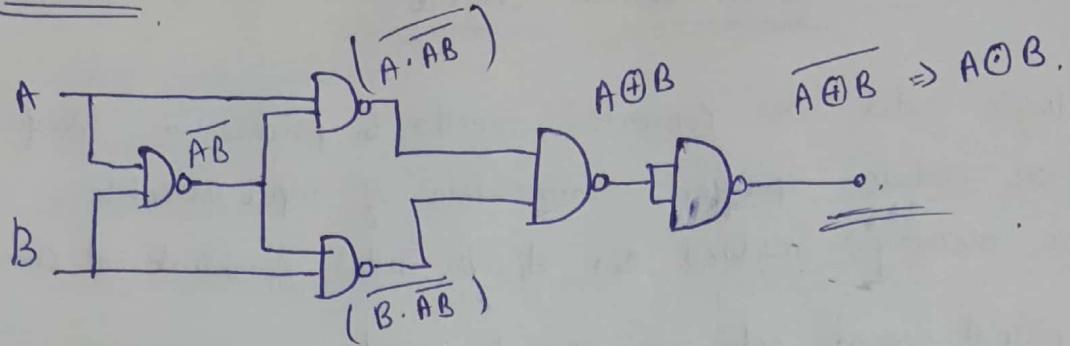

NOTE  
To implement EX-NOR gate using NAND gate it requires 5 NAND gates.

(17)

## NOR Realization :-

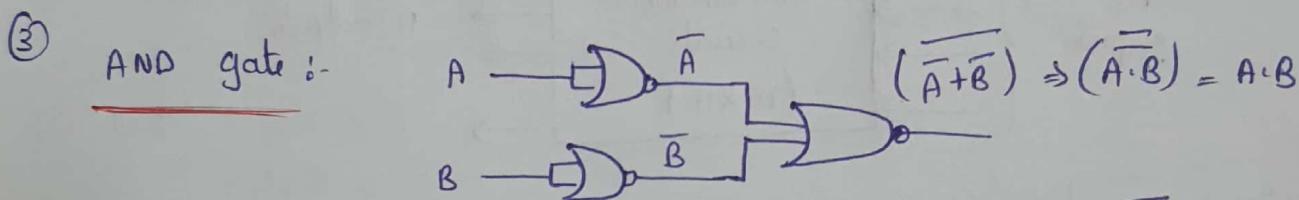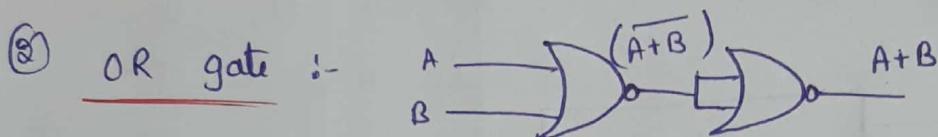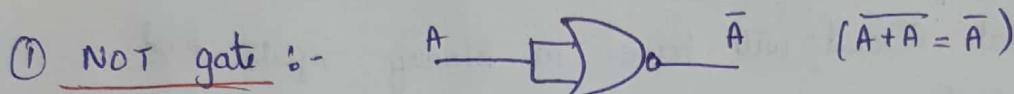

④ EX-NOR :-  $X = \overline{A + (\overline{A+B})} = \overline{A + (\overline{A} \cdot \overline{B})} = \overline{\overline{A} \cdot \overline{A \cdot \overline{B}}} = \overline{\overline{A}} (A+B) \Rightarrow \overline{AB}$

To implement EX-NOR gate using NOR gate it requires 4 NOR gates


$X = \overline{A + (\overline{A+B})} = \overline{A + (\overline{A} \cdot \overline{B})} = \overline{\overline{A} \cdot \overline{A \cdot \overline{B}}} = \overline{\overline{A}} (A+B) \Rightarrow \overline{AB}$

$Y = \overline{(B + (\overline{A+B}))} = \overline{B + (\overline{A} \cdot \overline{B})} = \overline{\overline{B} \cdot \overline{\overline{A} \cdot \overline{B}}} = \overline{\overline{B}} (A+B) \Rightarrow \overline{BA}$

$X+Y \Rightarrow \overline{AB} + \overline{BA} \Rightarrow \overline{\overline{AB}} \cdot \overline{\overline{BA}} \Rightarrow (A+\overline{B})(B+\overline{A}) \Rightarrow AB + \overline{B}\overline{A} \Rightarrow A \odot B$
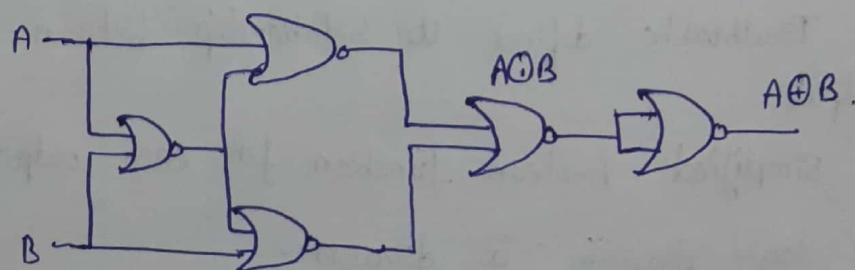
## Ex-OR :-

To implement Ex-OR gate by using NOR gates it requires 5 NOR gates




## Combinational Circuits:-

- When logic gates are connected together to produce a specified output on certain specified combination of input variable with no memory involved then it is called Combinational Circuit
- Here output depends only on present input.

$$\text{output} = F(\text{Input})$$

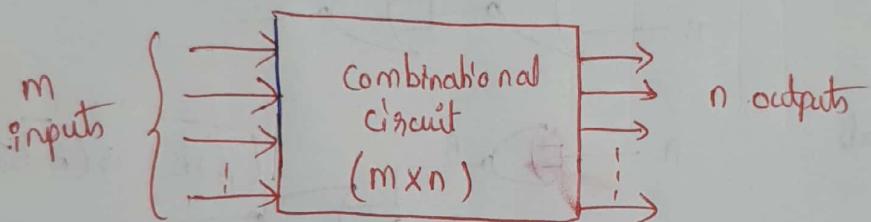- A Combinational Circuit will have m-binary inputs and n binary outputs.



### Design procedure :-

- The design of combinational circuit starts from the verbal description of the problem and ends in a logic circuit diagram.

### Steps to design :-

- ① The problem is stated. The number of available input variables and required output variables is determined.
- ② The input and output variables are assigned letters / symbols
- ③ The TruthTable defines the relationship between inputs and outputs.
- ④ The simplified boolean function for each output is obtained.
- ⑤ The logic diagram is drawn.

## Examples of Combinational Circuit


- ① Adder and Subtractors
- ② Decoder
- ③ Multiplexer
- ④ Code - Converters
- ⑤ Comparator
- ⑥ ROM

### Problems

① Design a combinational circuit with two inputs that produce logic "0" when any one input is one?

Given :- Two inputs  
one output

③ Simplify by K-map

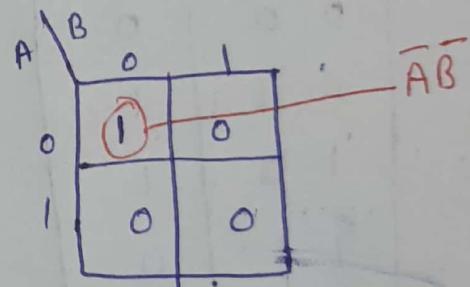


① Let inputs A, B  
output C

② Truth Table

input		output
A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

④ Draw the logic circuit

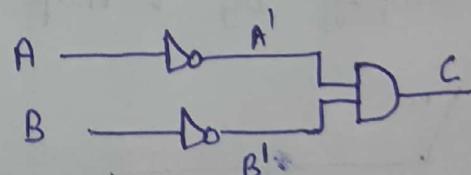



Since any one input is ~~zero~~ one  
o/p will be zero.

② Design a Combinational Circuit with two inputs that produces high output when there are odd numbers of 1's in the input?

Given :- Input - 2  
output - 1

③ logic circuit


① Combinational Circuit

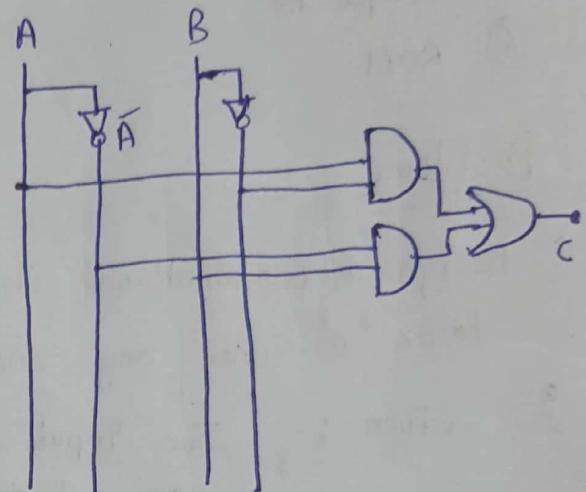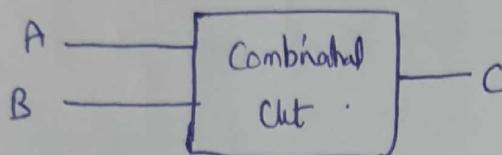

② Truth Table

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0


③ Simplify by K-map

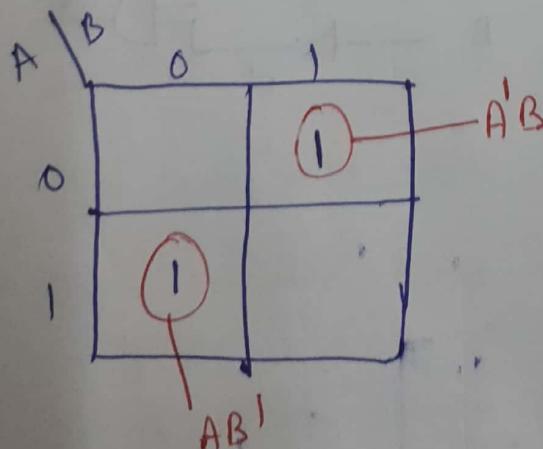

④  $C = AB' + A'B$
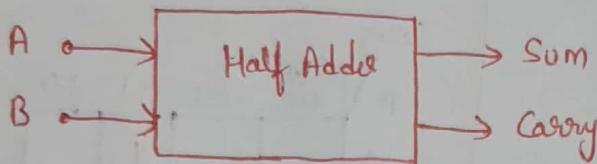
## ADDERS

- Half adder is a combinational logic circuit designed to add two single bit numbers.
- It contains two input and two outputs (sum & carry)




## Truth Table

Input		Output	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


		Carry
		A
		B
0	0	0
0	1	0
1	0	0
1	1	1

$$\text{Carry} = AB$$

## Logic Circuit

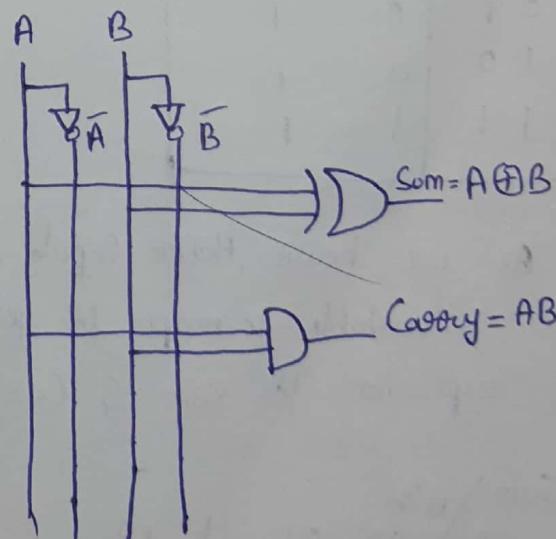

## Simplify by K-map :-

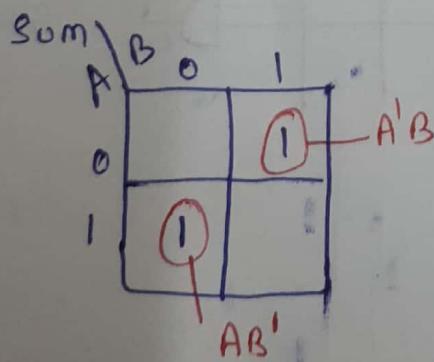

$$\text{Sum} = AB' + A'B$$

$$\Rightarrow A \oplus B$$

### Full Adder :-


- It is a arithmetic logic circuit designed to add two single bit numbers with a carry.
- It has three inputs and two outputs.



Truth Table.

Input	Output			
A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

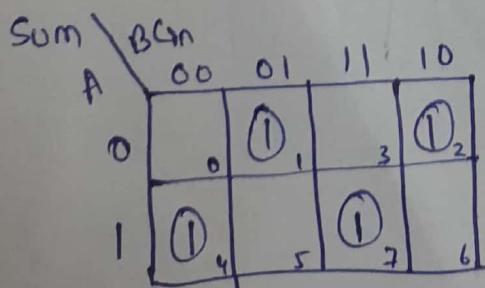
→ As we have three inputs, we use 3-Variable K-map for getting the expression for sum & carry.



$$S = A \oplus B \oplus C_{in}$$


As all are diagonal take EX-OR of all inputs.

Carry :-

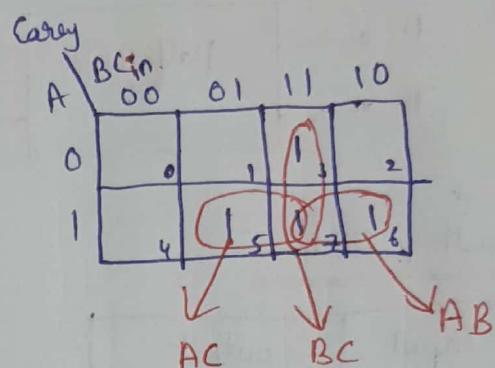

$$Carry = AB + BC_{in} + AC_{in}$$

Logic Circuit

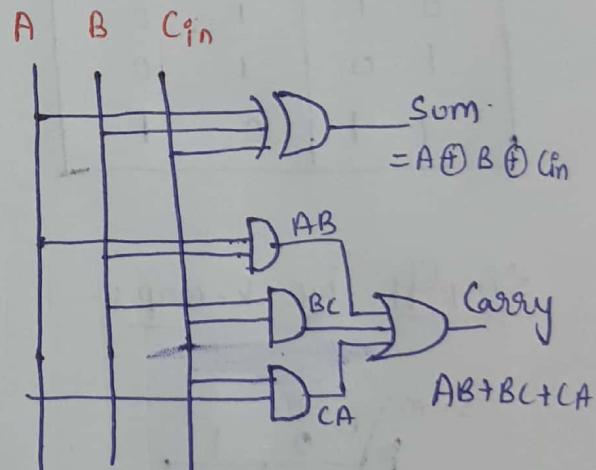


## 4-Bit Binary Adder :-

- Binary adder is a digital circuit that performs arithmetic sum of two binary numbers of any length.
- It is constructed by using full adder connected in series with output as carry connected to the next full adder and another output as sum.
- Let the inputs be A, B

As the length is given as 4 bit

$$A \rightarrow A_3 A_2 A_1 A_0$$

$$B \rightarrow B_3 B_2 B_1 B_0$$

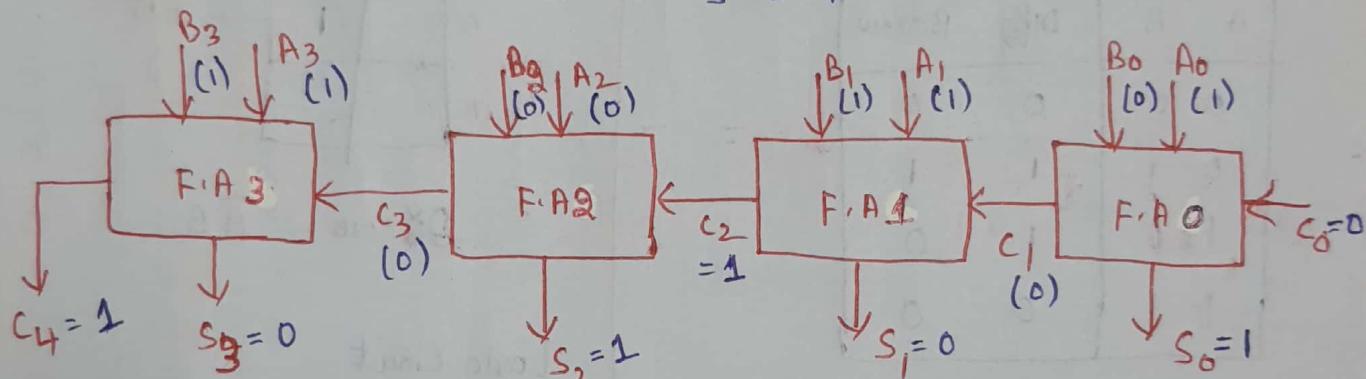

- Let's consider an example. Take 4 bits

$$A \rightarrow 1 \ 0 \ 1 \ 1$$

$$B \rightarrow 1 \ 0 \ 1 \ 0$$

$$\begin{array}{r}
 A + B \Rightarrow \\
 \begin{array}{r}
 & | & | \\
 & 1 & 0 \\
 + & 1 & 0 \\
 \hline
 & 1 & 0 \\
 \end{array} \\
 \text{Carry} \quad \underline{\text{discarded.}}
 \end{array}$$

Let's simplify it by applying A, B inputs to above diagram.

→ Initially assign  $C_0 = 0$ , as we don't have carry.


$$(S_3 S_2 S_1 S_0) = (\underline{0} \ 1 \ 0 \ 1)$$

(2)

## Subtractor :-

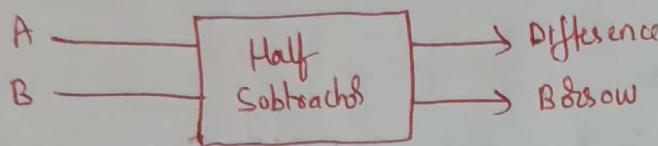
### Half Subtractor :-

- It is a combinational circuit used to get the difference between two single bit numbers.
- It has two inputs and two outputs difference and borrow.




Truth Table

Input		Output	
A	B	Diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

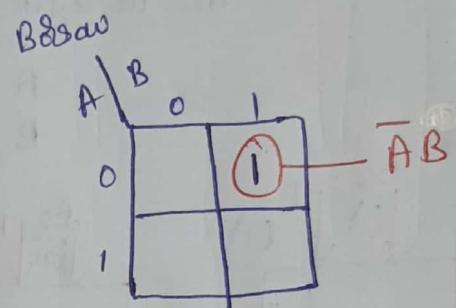


Logic Circuit

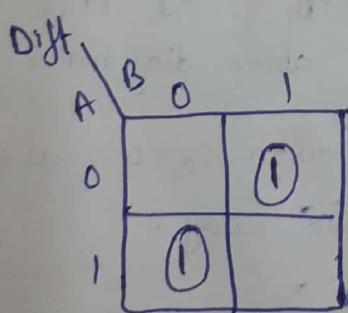Simplify Difference & borrow to obtain expressions by K-map.




$$\text{Dift} = A \oplus B$$

$$\text{Dift} = A'B + AB'$$

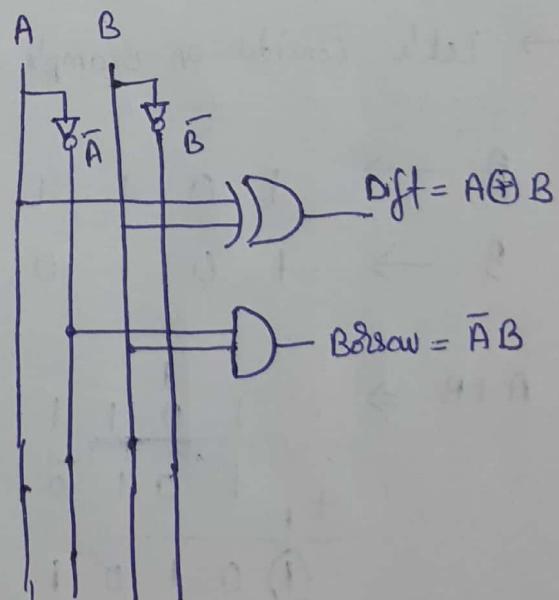

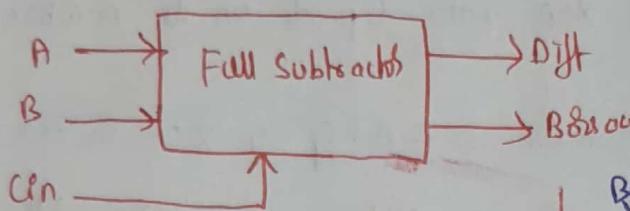
## Full Subtractor:-

- Full Subtractor is a combinational circuit used to perform subtraction among 3 bits
- It has 3 inputs and two outputs (difference & borrow)




Truth Table.

Input			Output	
A	B	Cin	Difft	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

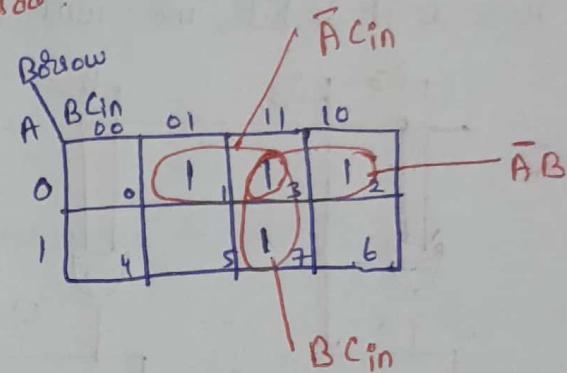


$$\text{Borrow} = \bar{A}B + BC_{in} + \bar{A}C_{in}$$

Logic Circuit

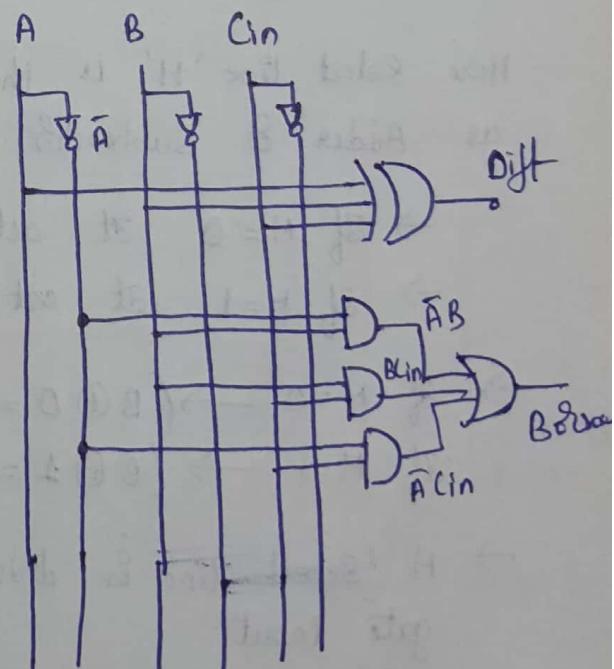

→ Simplify Difft & Borrow to get its expression.

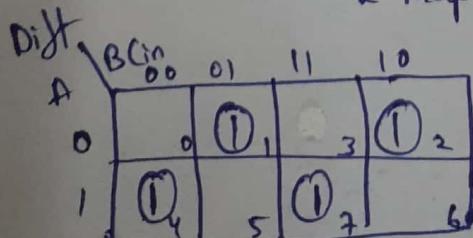
→ As we have 3 inputs Consider 3 Variable K-map.



$$\text{Difft} = A \oplus B \oplus \text{Cin}$$
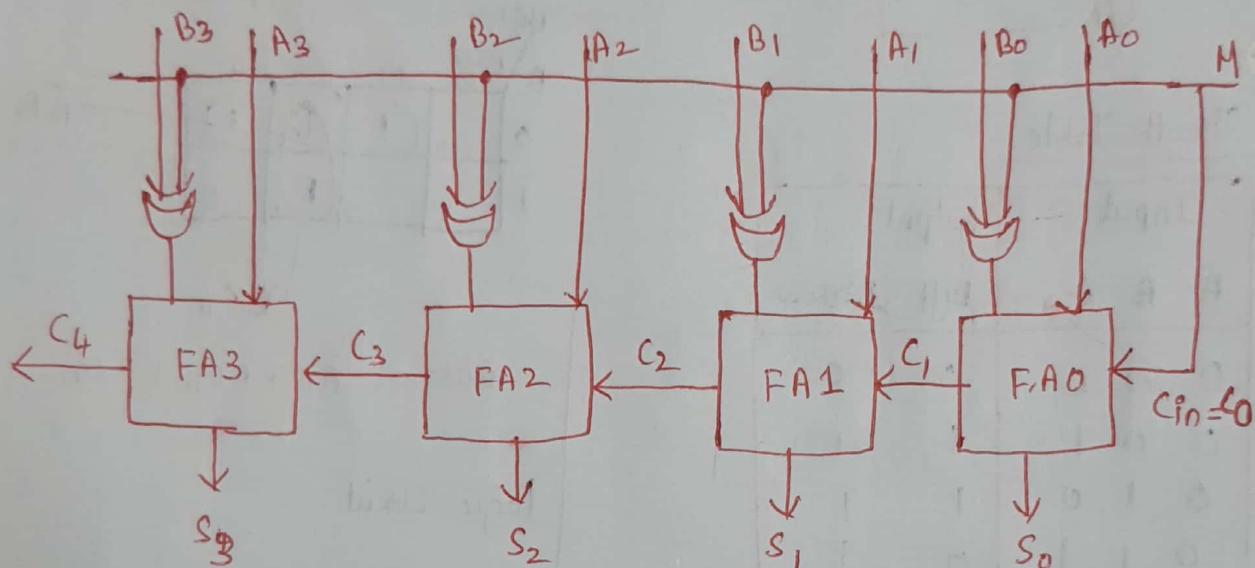
## 4-Bit Binary Adder / Subtractor :-

- It is a combinational circuit that performs both Addition & Subtraction at a single time based on the Select line "M".
- The circuit has full adders and XOR gates in it.
- Number of full adders and XOR gates depends on the number of bits.
- Here as it 4 bit, we will have 4 FA & 4 XOR in our circuit.




Here Select line 'M' is the source to make the circuit operate as Adder & Subtractor

- If  $M=0$  it act as adder
- If  $M=1$  it act as subtractor.
- If  $M=0 \rightarrow (B \oplus 0 = B)$
- If  $M=1 \rightarrow (B \oplus 1 = \bar{B})$
- M Select line is derived to all the full adder by XOR gate input

→ Let's add two numbers  $6 + 2 = 8$

$$\begin{array}{r}
 A \rightarrow \begin{array}{cccc} | & | & | & | \\ 1 & 0 & 1 & 0 \end{array} \\
 B \rightarrow \begin{array}{cccc} | & | & | & | \\ 0 & 0 & 1 & 0 \end{array} \\
 \hline
 \end{array}$$

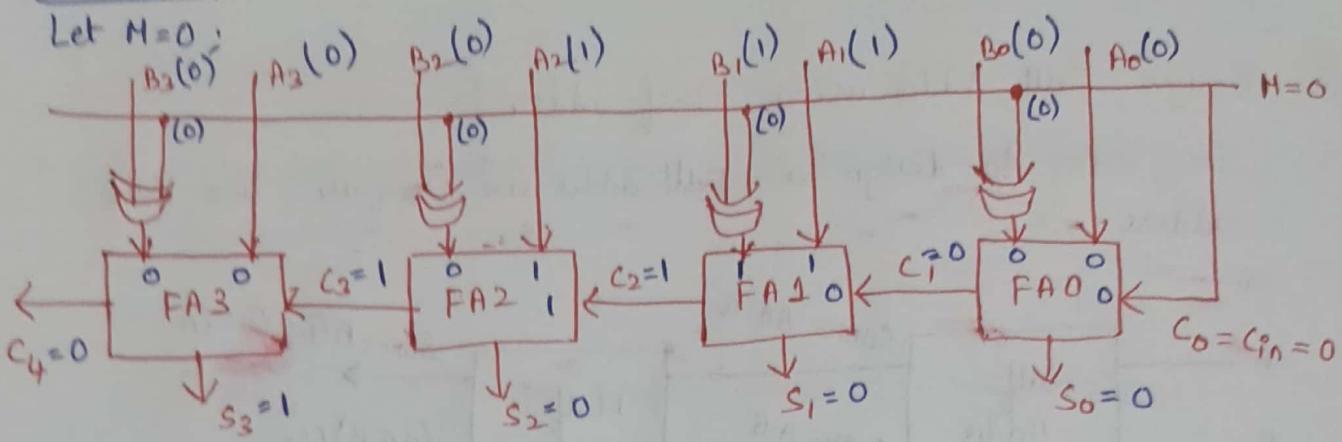CASE - I.

After solving we got  $(S_3, S_2, S_1, S_0) = (1, 0, 0, 0)$ .

Case - (ii)

Let  $M = 1$  ; now circuit behaves like subtractor.


Let take same numbers  $6 - 2 = 4$ .

$$\begin{array}{r} A = 6 \rightarrow 0110 \\ B = -2 \rightarrow 0010 \end{array}$$

$$\begin{array}{r} 0110 \rightarrow (6) \\ 1110 \rightarrow (-2) \\ \hline 0100 \rightarrow (4) \end{array}$$

Discard the carry

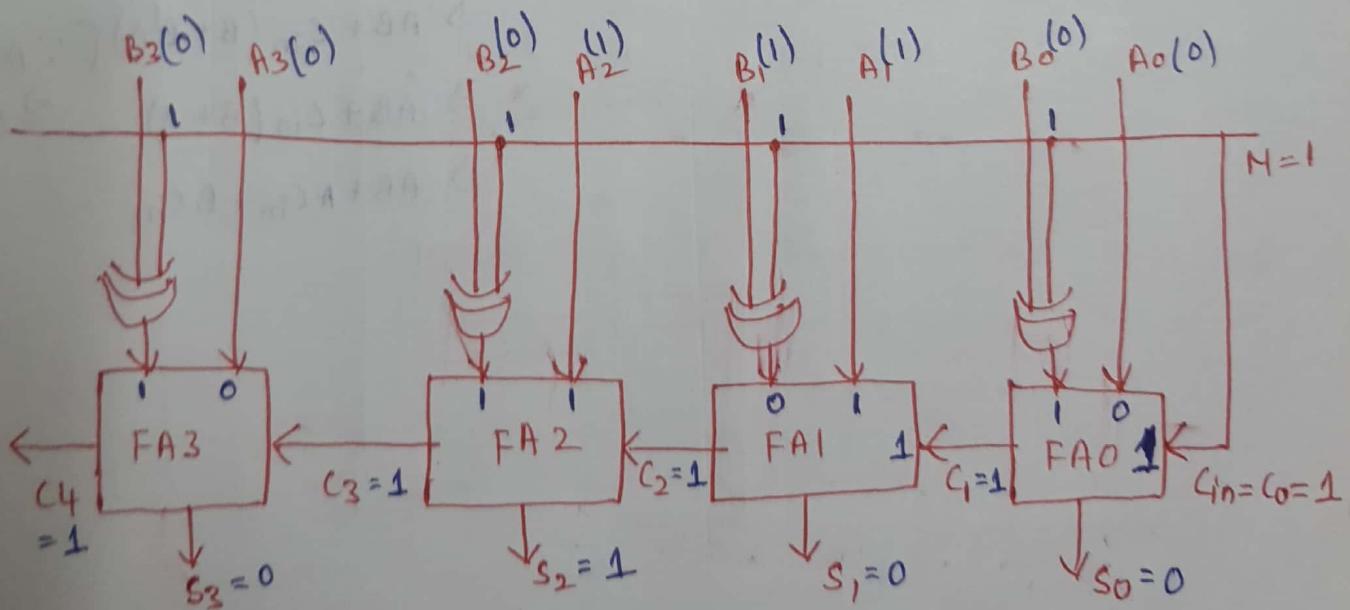
$$0010 \xrightarrow{2's} \begin{array}{r} 1101 \\ +1 \\ \hline 1110 \end{array}$$



$$(S_3, S_2, S_1, S_0) = (0100).$$

Q. Design Full Adder using Half adder?

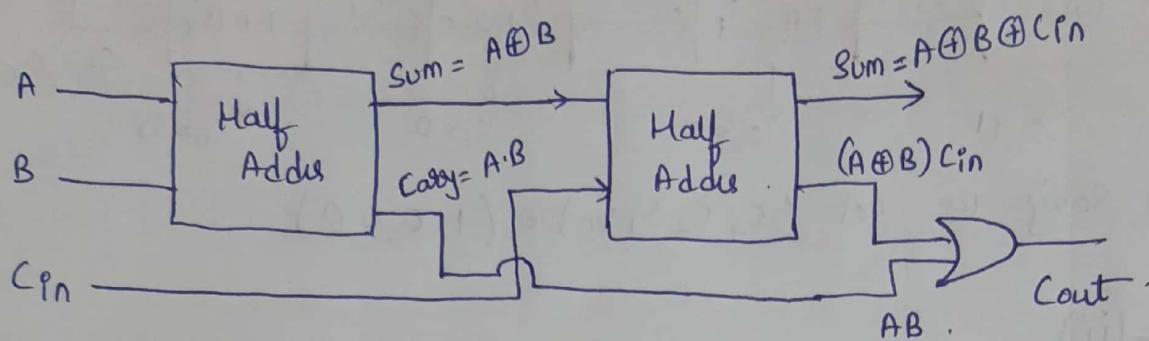In order to design a Full adder we require two Half adders.



$$C_{out} = AB + (A \oplus B) C_{in}$$

$$\Rightarrow AB + (A' B + B' A) C_{in}$$

$$\Rightarrow AB + A' B C_{in} + A B' C_{in} \quad \left\{ \begin{array}{l} \text{from } \\ A + A' B = A + B \end{array} \right\}$$

$$\Rightarrow B(A' C_{in} + A) + A B' C_{in}$$

$$\Rightarrow AB + BC_{in} + B' AC_{in}$$

$$\Rightarrow AB + C_{in}(B + B' A) \quad [ \because A + A' B = A + B ]$$

$$\Rightarrow AB + C_{in}(B + A) \quad \Rightarrow A + B$$

$$\Rightarrow AB + AC_{in} + BC_{in}$$

## BINARY MULTIPLIER

→ It is a combinational circuit that performs multiplication of Two binary numbers.

Ex:-  $A \times B$


A, B are two binary numbers used for multiplication.

A → multiplicand  
B → multiplier
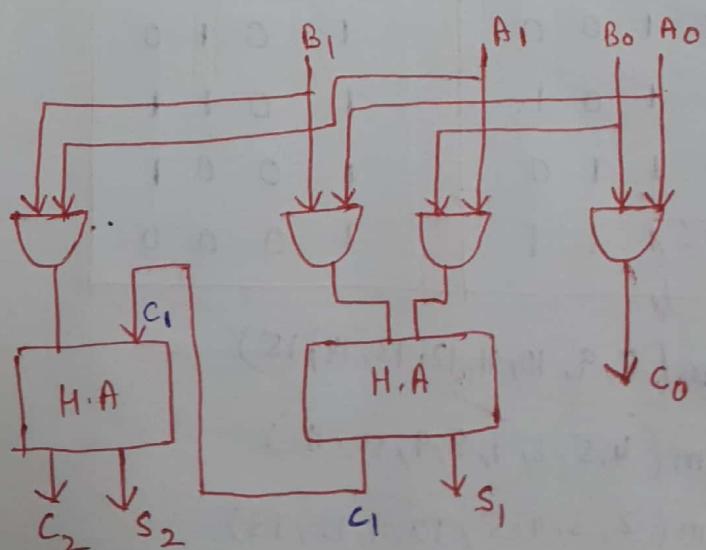
### 2x2 Multiplier

A  $\leftarrow A_1 A_0$   
B  $\leftarrow B_1 B_0$

$$\begin{array}{r}
 & A_1 \ A_0 \\
 & \times \ B_1 \ B_0 \\
 \hline
 & C_1 \quad B_0 A_1 \quad B_0 A_0 \\
 C_2 \quad B_1 \ A_1 \quad B_1 \ A_0 & \times \\
 \hline
 C_2. \ (C_1 + B_1 A_1) \ (B_0 A_1 + ) \ B_0 A_0 \\
 \downarrow \qquad \downarrow \qquad \downarrow \qquad \downarrow \\
 \text{Carry} \ (C_2) \quad \text{Sum} \ (S_2) \quad \text{Sum} \ (S_1) \quad \text{Carry} \ (C_0)
 \end{array}$$



## CODE CONVERTER:-

→ Code converters are used to convert from one code to another code.

Q) Design a 4 bit binary to Gray code converter?

Inputs = 4 ( $B_3, B_2, B_1, B_0$ ) ; Outputs = 4 ( $G_3, G_2, G_1, G_0$ )

Decimal	Binary Input				Gray code			
	$B_3$	$B_2$	$B_1$	$B_0$	$G_3$	$G_2$	$G_1$	$G_0$
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1
2	0	0	1	0	0	0	1	1
3	0	0	1	1	0	0	1	0
4	0	1	0	0	0	1	1	0
5	0	1	0	1	0	1	1	1
6	0	1	1	0	0	1	0	1
7	0	1	1	1	0	1	0	0
8	1	0	0	0	1	1	0	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	1	1	1	1
11	1	0	1	1	1	1	1	0
12	1	1	0	0	1	0	1	0
13	1	1	0	1	1	0	1	1
14	1	1	1	0	1	0	0	1
15	1	1	1	1	1	0	0	0

$$G_3 = \sum m(8, 9, 10, 11, 12, 13, 14, 15)$$

$$G_2 = \sum m(4, 5, 6, 7, 8, 9, 10, 11)$$

$$G_1 = \sum m(2, 3, 4, 5, 10, 11, 12, 13)$$

$$G_0 = \sum m(1, 2, 5, 6, 9, 10, 13, 14)$$

$C_3$	$B_1, B_0$	00	01	11	10
$B_3, B_2$	00	0	1	3	2
00	0	1	3	2	
01	4	5	7	6	
11	1 12	1 13	1 15	1 14	
10	1 8	1 9	1 11	1 10	

$$G_3 = B_3$$

$C_2$	$B_1, B_0$	00	01	11	10
$B_3, B_2$	00	0	1	3	2
00	0	1	3	2	
01	1 4	1 5	1 7	1 6	
11	12	13	15	14	
10	1 8	1 9	1 11	1 10	

$$G_2 = \bar{B}_3 \bar{B}_2 + B_2 \oplus B_3$$

$C_1$	$B_1, B_0$	00	01	11	10
$B_3, B_2$	00	0	1	3	2
00	0	1	3	2	
01	1 4	1 5	1 7	1 6	
11	1 12	1 13	1 15	1 14	
10	1 8	1 9	1 11	1 10	

$$B_2 \bar{B}_1$$


$$\bar{B}_2 B_1$$

$$G_1 = B_2 \bar{B}_1 + \bar{B}_2 B_1 \Rightarrow B_2 \oplus B_1$$

$G_0$	$B_1, B_0$	00	01	11	10
$B_3, B_2$	00	0	1	3	2
00	0	1	3	2	
01	4	5	7	6	
11	12	13	15	14	
10	1 8	1 9	1 11	1 10	

$$G_0 = \bar{B}_1 B_0 + B_1 \bar{B}_0 \Rightarrow B_1 \oplus B_0$$

Logic Circuit

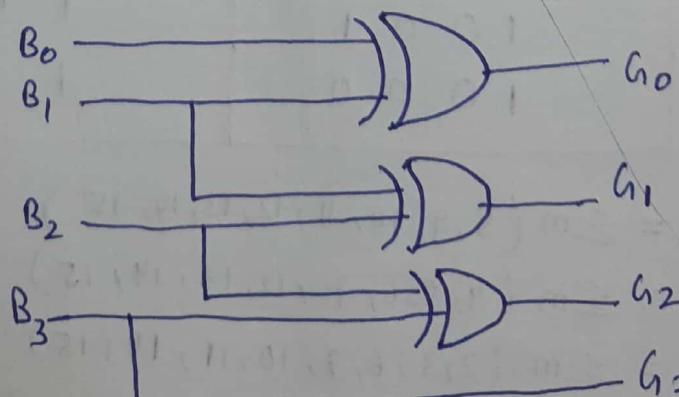

Q) Design a 4 bit Gray Code to Binary code?

S Inputs = 4 (Gray Code) ( $G_3 G_2 G_1 G_0$ )

Outputs = 4 (Binary Code) ( $B_3 B_2 B_1 B_0$ )

Gray Code				Binary Code			
$G_3$	$G_2$	$G_1$	$G_0$	$B_3$	$B_2$	$B_1$	$B_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	1	0	0	1	0
0	0	1	0	0	0	1	1
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	1
0	1	0	1	0	1	1	0
0	1	0	0	0	1	1	1
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	1
1	1	1	1	1	0	1	0
1	1	1	0	1	0	1	1
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	0	0	1	1	1	1	0
1	0	0	0	1	1	1	1

$B_3$	$G_3 G_2 G_1 G_0$	00	01	11	10
$G_3$		00	01	11	10
00					
01					
11	1 1 1 1				
10	1 1 1 1				

$B_3 = G_3$

$B_2$	$G_3 G_2 G_1 G_0$	00	01	11	10
$G_3 G_2$		00	01	11	10
00					
01	1 1 1 1				
11					
10	1 1 1 1				

$\bar{G}_3 \bar{G}_2$

$$B_2 = \bar{G}_3 G_2 + G_3 \bar{G}_2$$

$$B_2 \Rightarrow G_3 \oplus G_2$$

$B_1$	$G_3 G_2 G_1 G_0$	00	01	11	10
$G_3 G_2 G_1$		00	01	11	10
00	1 1				
01		1 1			
11			1 1		
10				1 1	

$\bar{G}_3 \bar{G}_2 \bar{G}_1$


$$B_1 = G_3 \bar{G}_2 \bar{G}_1 + G_3 G_2 \bar{G}_1 + \bar{G}_3 G_2 G_1$$

$$B_1 = G_3 \oplus G_2 \oplus G_1$$

$B_0$	$G_3 G_2 G_1 G_0$	00	01	11	10
$G_3 G_2 G_1 G_0$		00	01	11	10
00					
01		1			
11			1		
10				1	

$\bar{G}_3 \bar{G}_2 \bar{G}_1 \bar{G}_0$
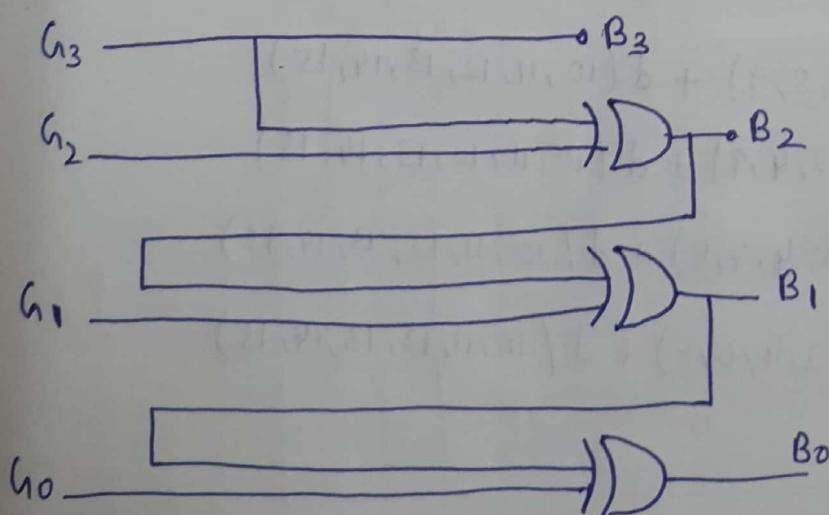
$$B_0 = G_3 \oplus G_2 \oplus G_1 \oplus G_0$$



- H.W
- ① Design 3 bit binary to Gray converter,
  - ② Design 3 bit Gray to Binary converter

(34)

Q) Convert a 4 bit BCD to Excess-3 code?

S Inputs - 4 - (A, B, C, D)    Outputs - 4 (E<sub>3</sub>, E<sub>2</sub>, E<sub>1</sub>, E<sub>0</sub>).

→ As it is BCD → 0 to 9 will be active states (10 to 15)  
will be invalid state.

Decimal	BCD				Excess-3			
	A	B	C	D	E <sub>3</sub>	E <sub>2</sub>	E <sub>1</sub>	E <sub>0</sub>
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0

$$E_3 = \sum m(5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15)$$

$$E_2 = \sum m(1, 2, 3, 4, 9) + d(10, 11, 12, 13, 14, 15)$$

$$E_1 = \sum m(0, 3, 4, 7, 8) + d(10, 11, 12, 13, 14, 15)$$

$$E_0 = \sum m(0, 2, 4, 6, 8) + d(10, 11, 12, 13, 14, 15)$$

(35)

		CD		AB		BD				
		00	01	11	10	00		01	11	10
		00	0	1	3	2				
		01	4	5	7	6				
		11	X <sub>12</sub>	X <sub>13</sub>	X <sub>15</sub>	X <sub>14</sub>				
		10	8	9	X <sub>11</sub>	X <sub>10</sub>				

$E_3 = A + BD + BC$

(35)

		CD		AB		BD				
		00	01	11	10	00		01	11	10
		00	0	1	1	1				
		01	1	4	5	7	6			
		11	X <sub>12</sub>	X <sub>13</sub>	X <sub>15</sub>	X <sub>14</sub>				
		10	8	9	X <sub>11</sub>	X <sub>10</sub>				

$E_2 = \bar{B}\bar{C}\bar{D} + \bar{B}\bar{D} + \bar{B}\bar{C}$


		CD		AB		BD				
		00	01	11	10	00		01	11	10
		00	1	0	1	3	2			
		01	1	4	5	7	6			
		11	X <sub>12</sub>	X <sub>13</sub>	X <sub>15</sub>	X <sub>14</sub>				
		10	1	8	9	X <sub>11</sub>	X <sub>10</sub>			

$E_1 = \bar{C}\bar{D}$        $\bar{C}D$

$E_1 = C \oplus D$       ( $\because \bar{C}\bar{D} + CD = C \oplus D$ )

		CD		AB		BD				
		00	01	11	10	00		01	11	10
		00	1	0	1	3	2			
		01	1	4	5	7	6			
		11	X <sub>12</sub>	X <sub>13</sub>	X <sub>15</sub>	X <sub>14</sub>				
		10	1	8	9	X <sub>11</sub>	X <sub>10</sub>			

$E_0 = \bar{D}$

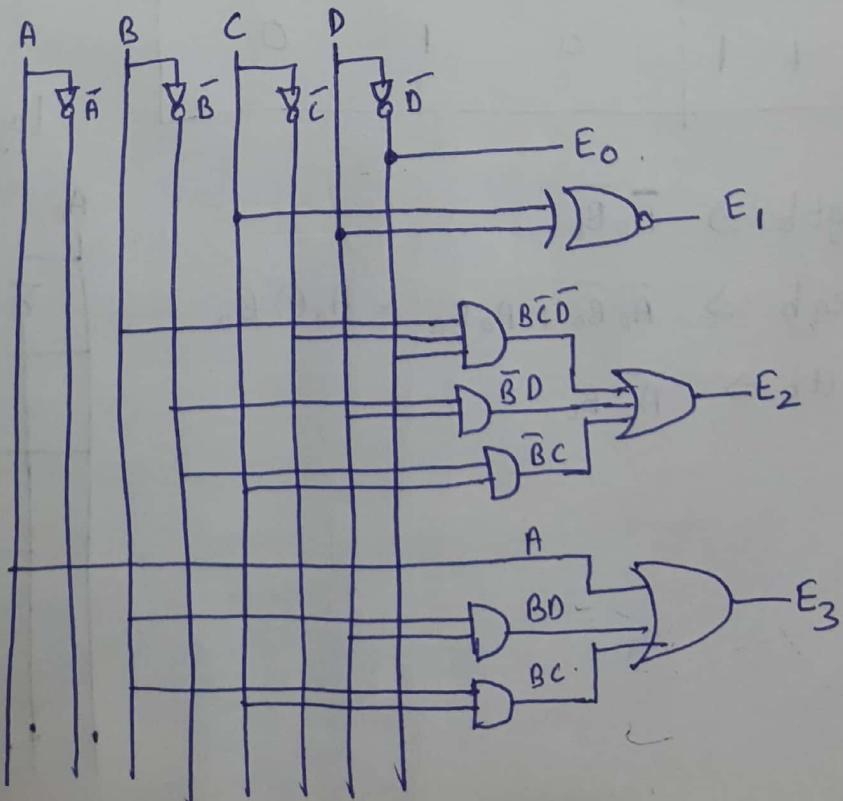
Logic Circuit

⑩ Convert Decs to Seven Segment

COMPARATOR :-

- Comparator is used to compare two N bit numbers, let say  $a$  &  $b$ .
- It is going to compare magnitude of numbers provided  $a > b$ ,  $a < b$  &  $a = b$ .

single bit & 1-bit Comparator :-

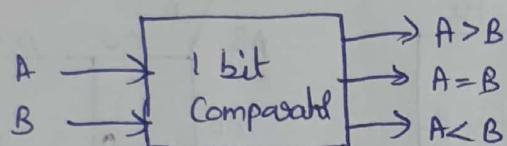

Truth Table.


Input		Output		
$A_0$	$B_0$	$a > b$	$a = b$	$a < b$
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

logic circuit

$$a > b \Rightarrow A_0 \bar{B}_0$$


$$a = b \Rightarrow \bar{A}_0 \bar{B}_0 + A_0 B_0 = A_0 \oplus B_0$$

$$a < b \Rightarrow \bar{A}_0 B_0$$

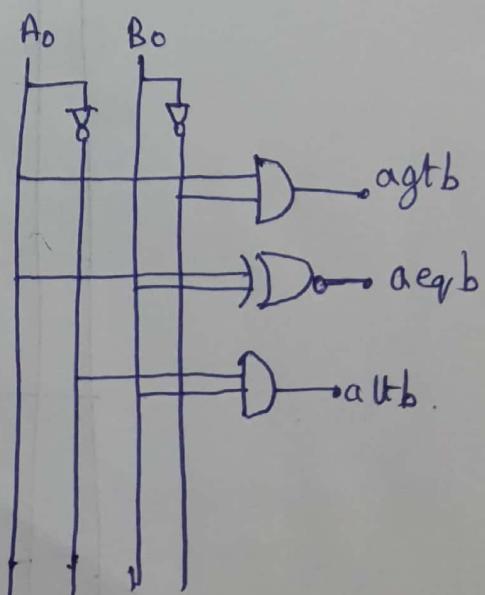

2-Bit Comparator :- Here let take two inputs A, B. Each input having length two i.e.  $A = A_1, A_0$ ;  $B = B_1, B_0$ ; where outputs are  $a_{gtb}$ ,  $a_{eqb}$ ,  $a_{ltb}$ .

Truth Table:

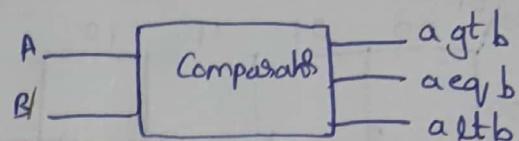




Inputs				outputs		
A		B		$a_{gtb}$	$a_{eqb}$	$a_{ltb}$
$A_1$	$A_0$	$B_1$	$B_0$			
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

$$a_{gtb} = \sum m(4, 8, 9, 12, 13, 14)$$

$$a_{eqb} = \sum m(0, 5, 10, 15)$$

$$a_{ltb} = \sum m(1, 2, 3, 6, 7, 11)$$


Simplify by K-map.

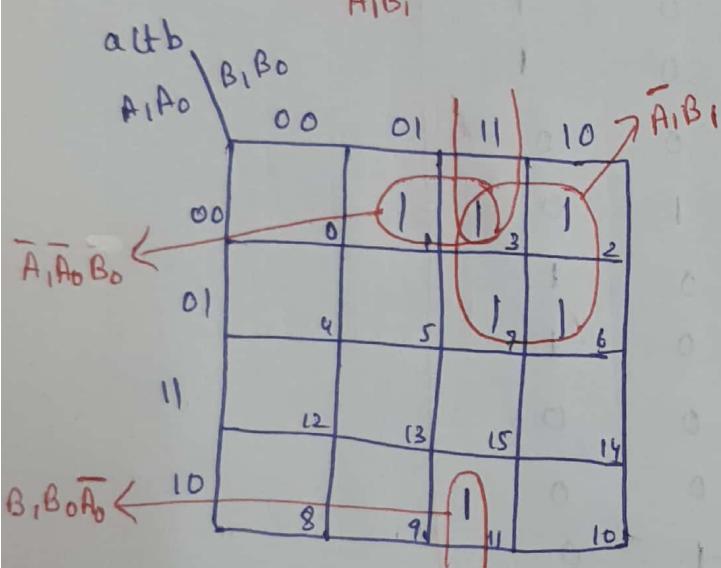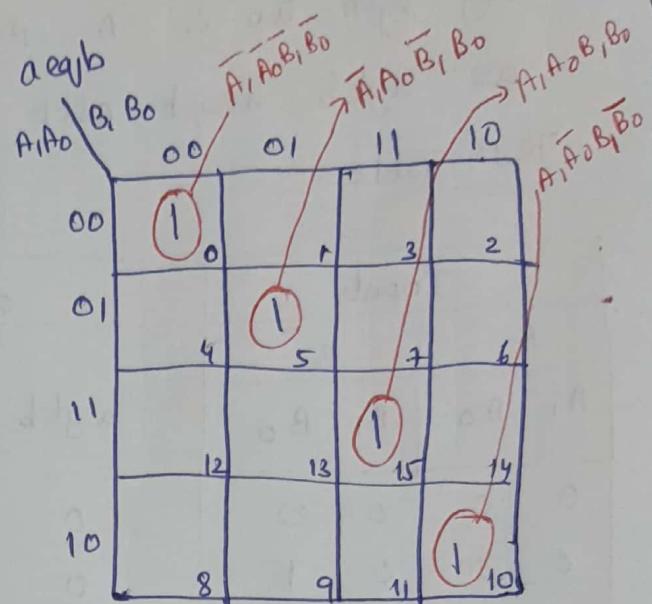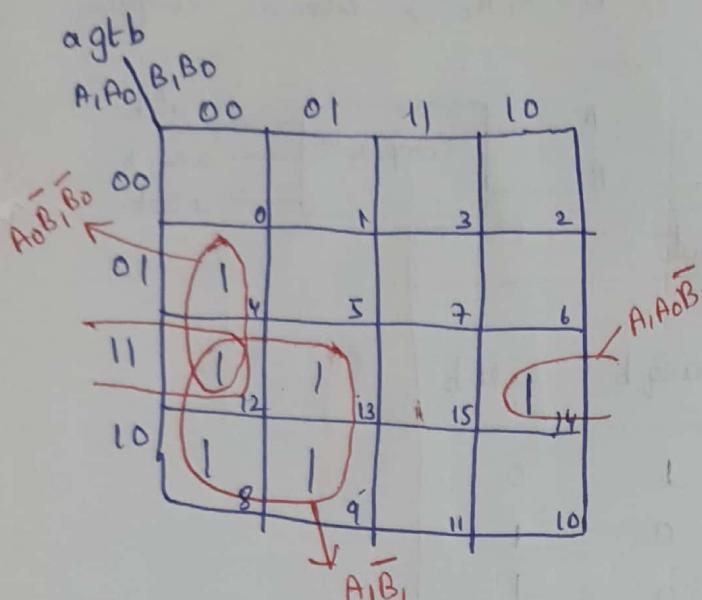

Simplified expression:-


$$\begin{aligned} agt'b &= A_0 \bar{B}_1 \bar{B}_0 + A_1 A_0 \bar{B}_0 + A_1 \bar{B}_1 \\ aeq'b &= \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 A_0 \bar{B}_1 B_0 + \\ &\quad A_1 A_0 B_1 B_0 + A_1 \bar{A}_0 B_1 \bar{B}_0 \\ \Rightarrow (A_1 \oplus B_1) (A_0 \oplus B_0) \end{aligned}$$
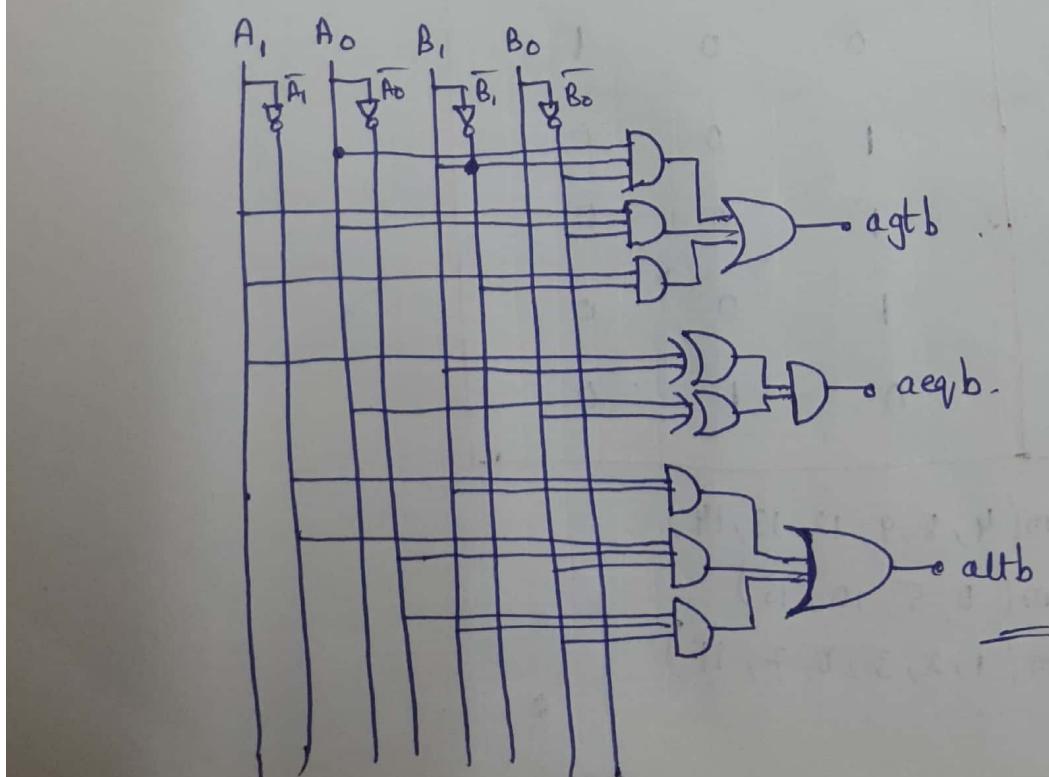
$$agt'b \Rightarrow \bar{A}_1 B_1 + \bar{A}_1 \bar{A}_0 B_0 + \bar{A}_0 B_1 B_0$$


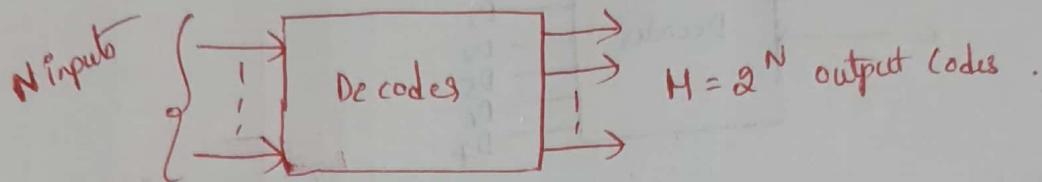
### Decodes :-

→ Decodes is a multi input multi output logic circuit that converts  $n$  bit binary input code to  $M$  output lines.



### 8 to 4 Decodes . (8) 2x4 Decodes:-

→ 8 to 4 Decodes has two inputs E & four outputs.

→ Let two inputs be A, B, outputs be  $D_0, D_1, D_2, D_3$ .

### Truth Table :

Enable	Inputs		Outputs				
	E	A	B	$D_0$	$D_1$	$D_2$	$D_3$
0	X	X		X	X	X	X
1	0	0		1	0	0	0
1	0	1		0	1	0	0
1	1	0		0	0	1	0
1	1	1		0	0	0	1


### Expressions.

$$D_0 = \bar{A} \bar{B}$$

$$D_1 = \bar{A} B$$


$$D_2 = A \bar{B}$$

$$D_3 = A B$$

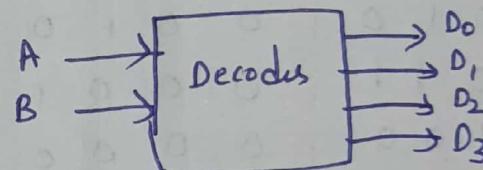


### (a) Block diagram .

### logic Circuit

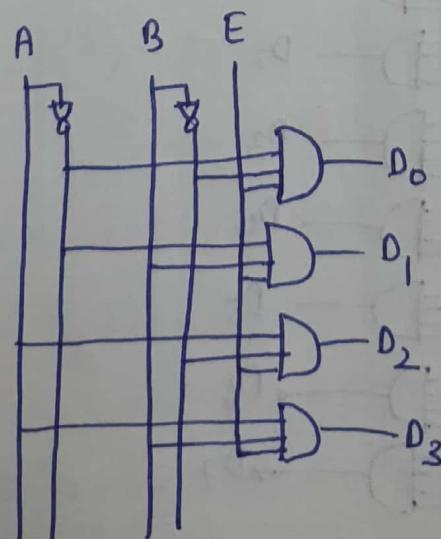

3 to 8 Decodes :- 3x8 Decodes has three inputs and eight outputs  
 Let the three inputs be A, B, C and outputs be D<sub>0</sub>, D<sub>1</sub>, D<sub>2</sub>, D<sub>3</sub>, D<sub>4</sub>, D<sub>5</sub>, D<sub>6</sub>, D<sub>7</sub>.

Block diagram

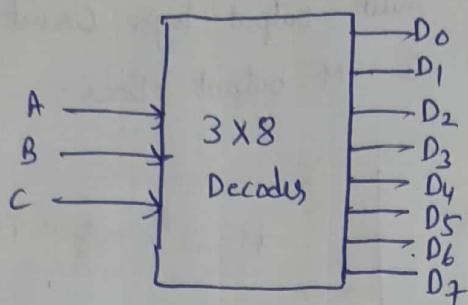

Truth Table :-

E	Inputs			outputs							
	A	B	C	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
0	X	X	X	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	0	0	0	0
1	0	1	0	0	0	1	0	0	0	0	0
1	0	1	1	0	0	0	1	0	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	0	0	1	0	0	0
1	1	1	0	0	0	0	0	0	1	0	0
1	1	1	1	0	0	0	0	0	0	0	1

expression of output

$$D_0 = \bar{A}\bar{B}\bar{C}$$

$$D_1 = \bar{A}\bar{B}C$$

$$D_2 = \bar{A}BC$$

$$D_3 = \bar{A}B\bar{C}$$


$$D_4 = A\bar{B}\bar{C}$$

$$D_5 = A\bar{B}C$$

$$D_6 = AB\bar{C}$$


$$D_7 = ABC$$

logic Circuit

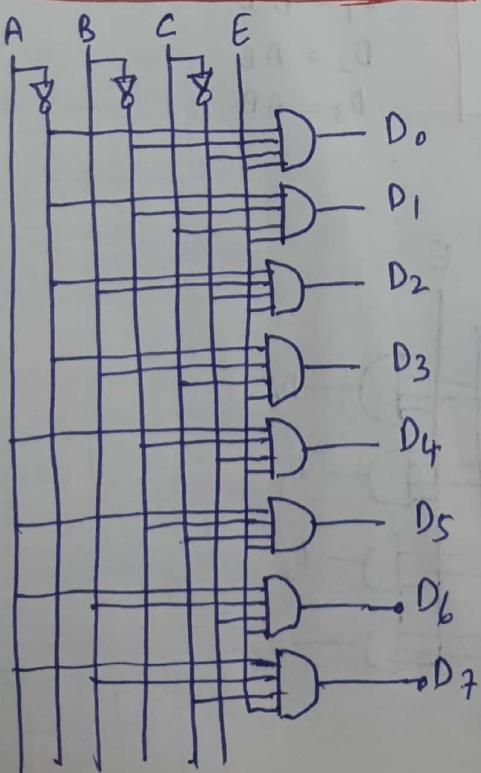


## ⑥ BCD to Seven Segment Decodes :-

Block diagram .

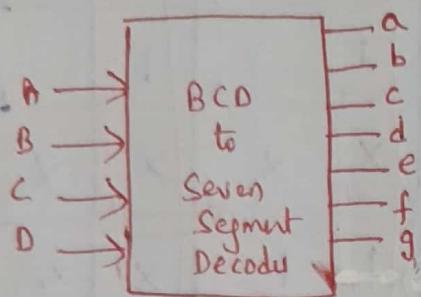

Seven Segment

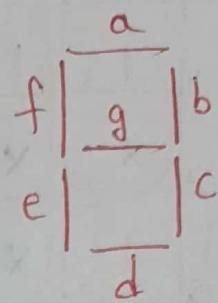

Truth Table .

Decimal value	Inputs				Outputs						
	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1

BCD will have inputs from (0 to 9)

& (10 to 15) will be Invalid states .

O/p. Expressions :-

$$a = \sum m(0, 2, 3, 5, 6, 7, 8, 9) + d(10-15)$$

$$b = \sum m(0, 1, 2, 3, 4, 7, 8, 9) + d(10-15)$$

$$c = \sum m(0, 1, 3, 4, 5, 6, 7, 8, 9) + d(10-15)$$







$$d = \sum m(0, 2, 3, 5, 6, 8, 9) + d(10-15)$$


$$e = \sum m(0, 2, 6, 8) + d(10-15)$$

$$f = \sum m(0, 4, 5, 6, 8, 9) + d(10-15)$$


$$g = \sum m(2, 3, 4, 5, 6, 8, 9) + d(10-15)$$

42

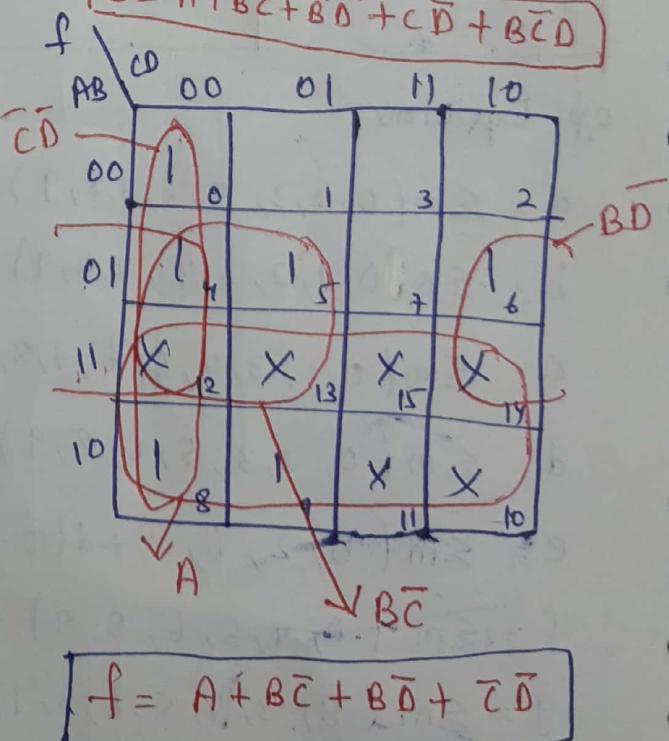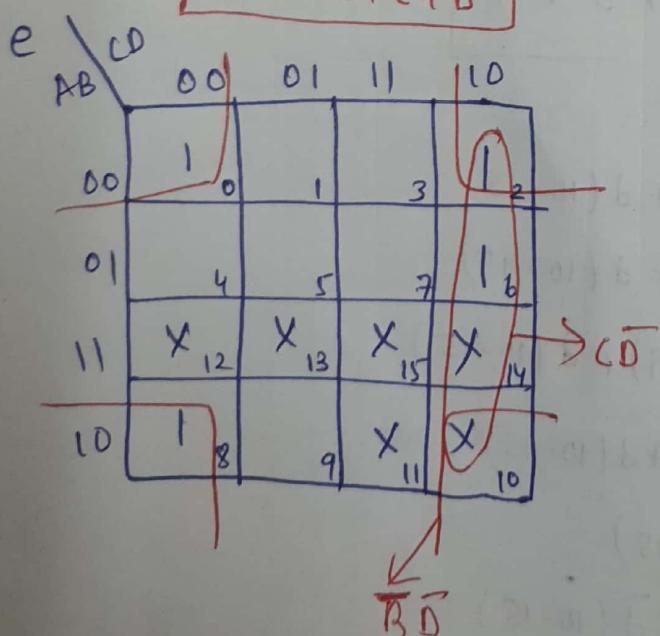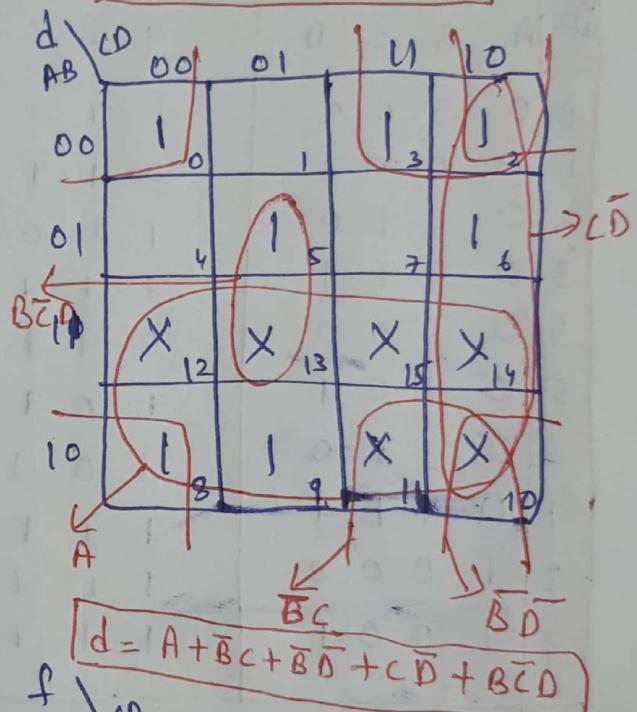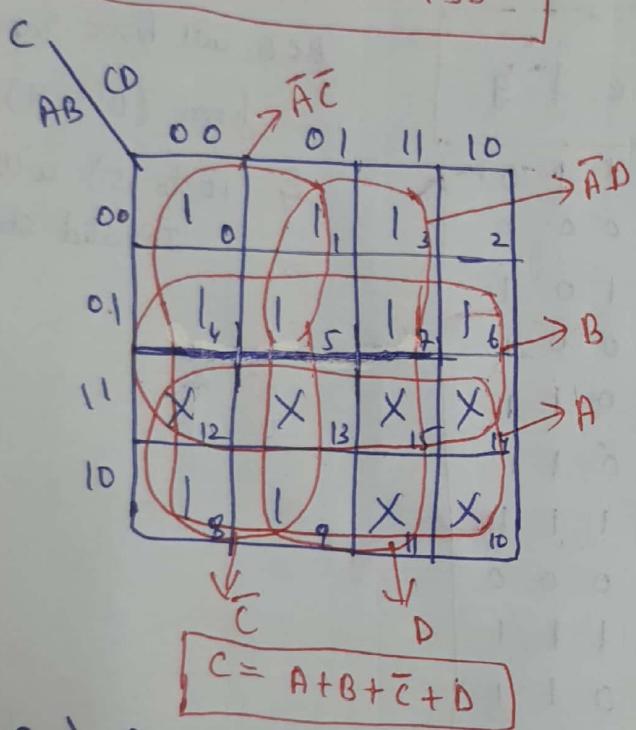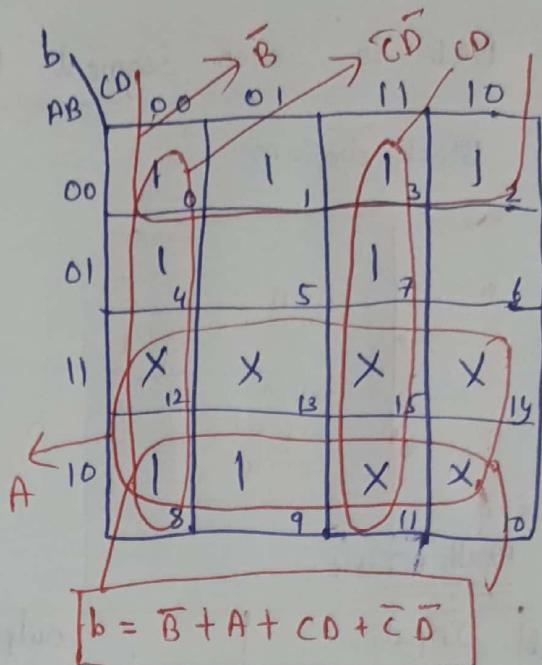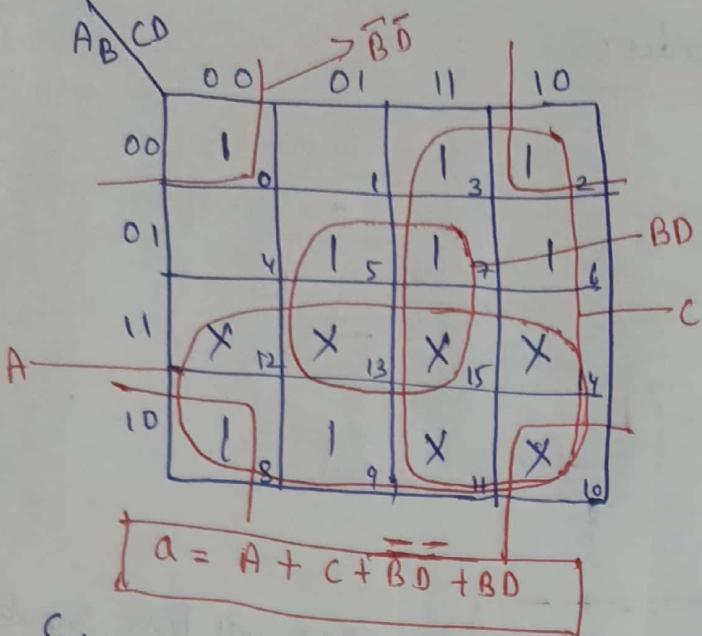

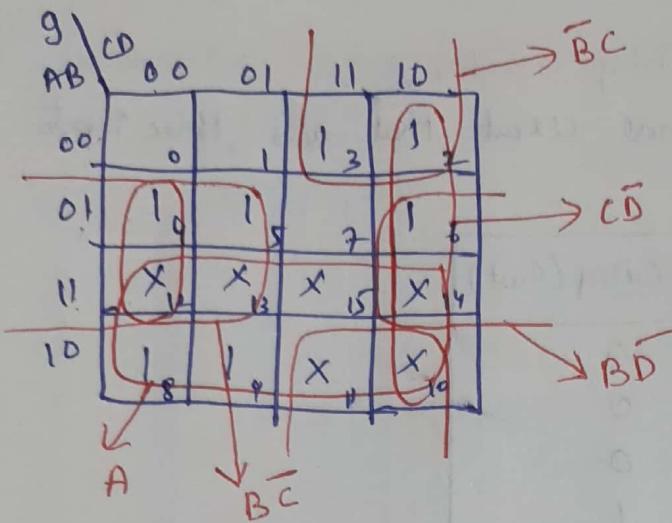
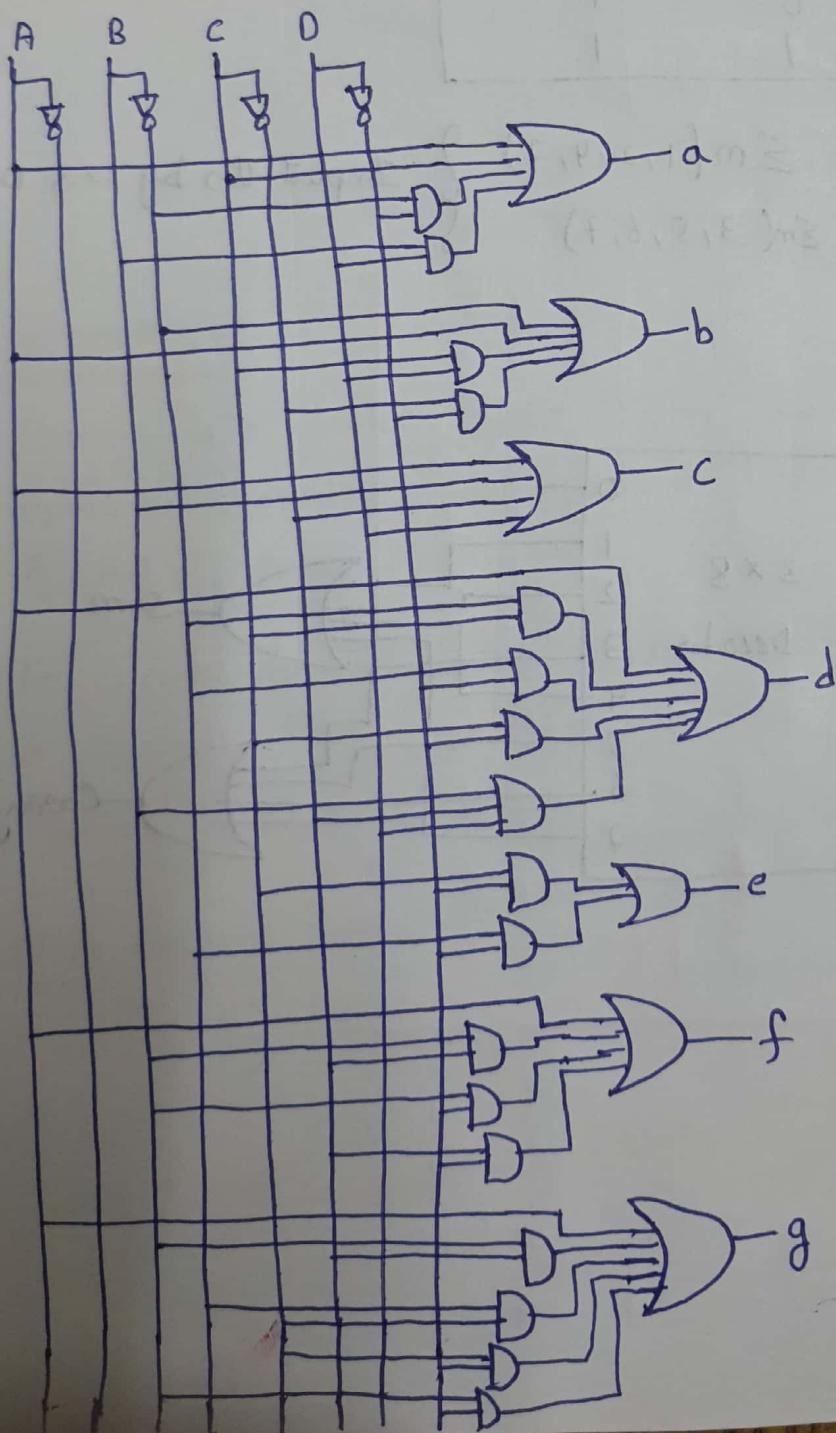
$$g = A + B\bar{C} + \bar{B}C + C\bar{D} + B\bar{D}$$



(44)

Q

Implement the full adder using Decoders?


S

Full adder is a combinational circuit that adds three inputs and have two outputs.

A	B	C	Sum(s)	Carry (Cout)
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$$\begin{aligned} \text{Sum} &= \sum m(1, 2, 4, 7) \\ \text{Carry} &= \sum m(3, 5, 6, 7) \end{aligned} \quad \left. \begin{array}{l} \text{Implement this by } 3 \times 8 \text{ Decoders} \\ \text{Implementation details: } \end{array} \right\}$$

3x8 Decodes.

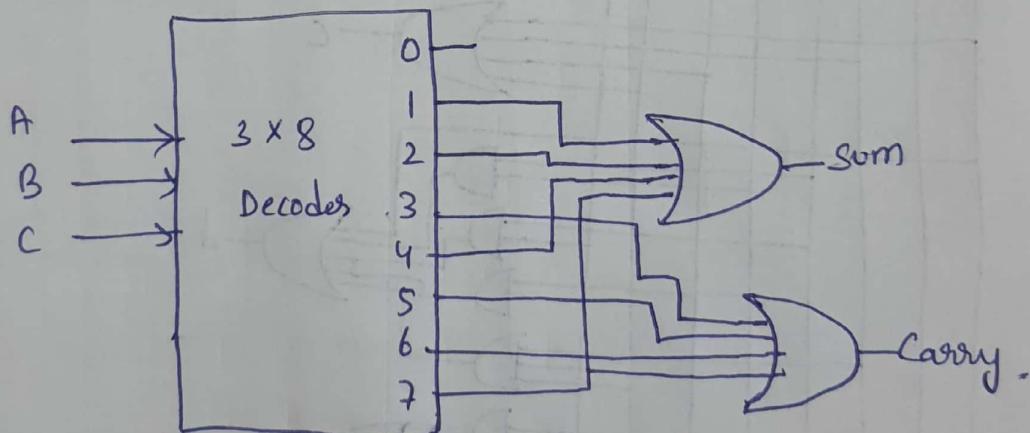

⑤ Implement  $4 \times 16$  Decodes by using two  $3 \times 8$  Decoders?


8

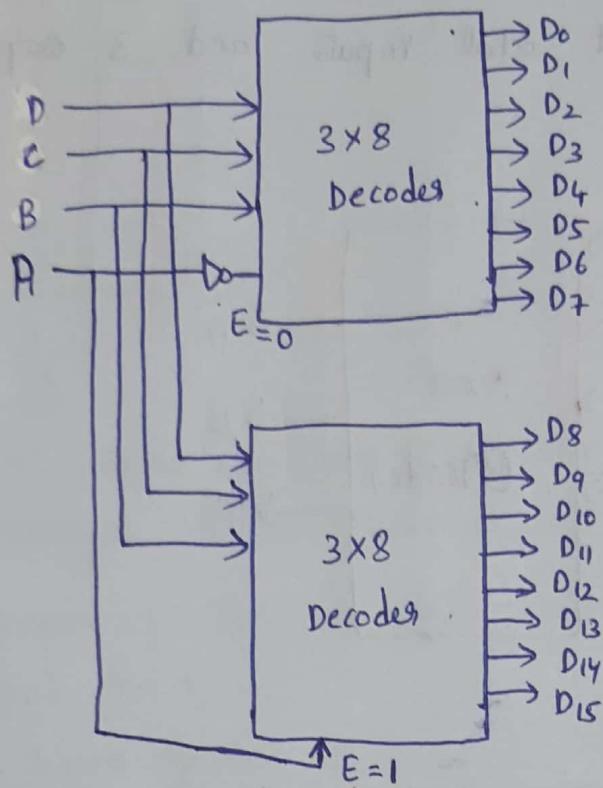

### ENCODERS.

- Encoder is a device whose inputs are decimal digits / 8 alphabetic characters and outputs are coded representation of those inputs.
- An encoder is a device which converts familiar numbers / symbols into coded format.
- It is reverse of decoders.

### Block diagram

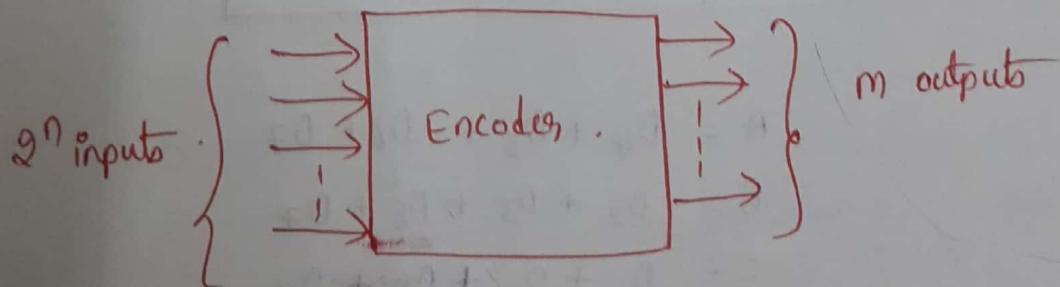


4b

## Octal to Binary Encoder :-

- It is also called as 8 to 3 line encoders.
- It has eight octal inputs and 3 outputs.

Block diagram.

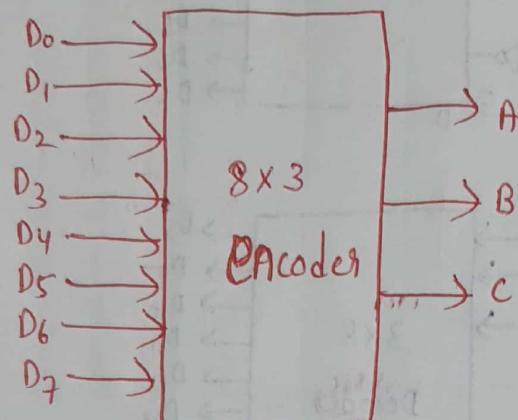


## Truth Table :-

Inputs								outputs		
D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>	A	B	C
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$A = D_4 + D_5 + D_6 + D_7$$

$$B = D_2 + D_3 + D_6 + D_7$$

$$C = D_1 + D_3 + D_5 + D_7$$

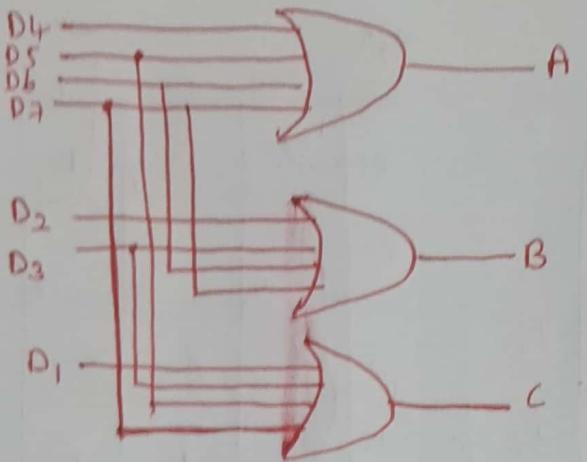


Priority Encoder :- It is one type of encoder where the input signal are prioritized to be driven at output.

→ 4 input priority encoder :- Here we have four inputs  $I_0, I_1, I_2, I_3$  and two outputs  $Y_0, Y_1$ .

→ Here  $I_0$  has lowest priority compared to remaining all, where as  $I_3$  holds highest priority.

Block diagram :-

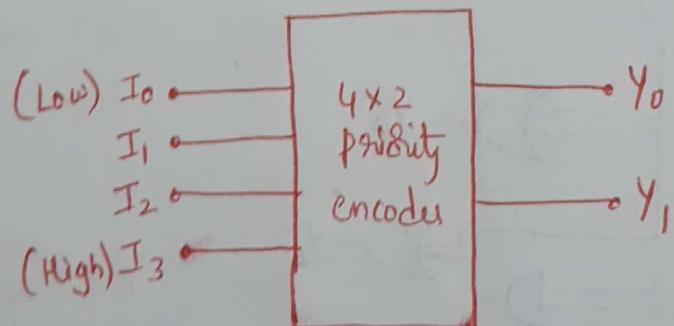

Truth Table :

Inputs				outputs	
$I_2$	$I_1$	$I_0$		$Y_0$	$Y_1$
0	0	0	0	X	X
0	0	0	1	0	0
0	0	1	X	0	1
0	1	X	X	1	0
1	X	X	X	1	1



when  $I_0$  is high

when  $I_1$  is high

when  $I_2$  is high

when  $I_3$  is high


(18)

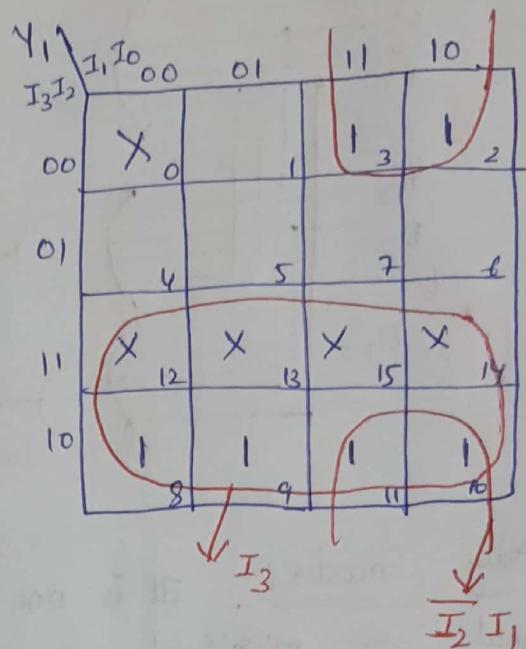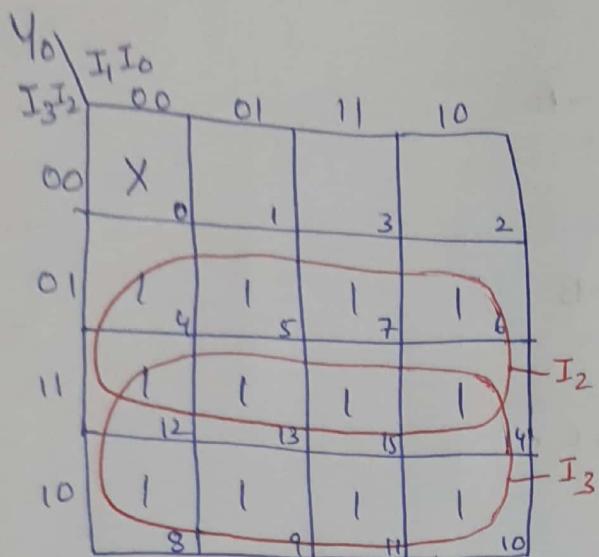

$$Y_0 = I_2 + I_3$$

$$Y_1 = I_3 + \overline{I_2} I_1$$

### Logic Circuit

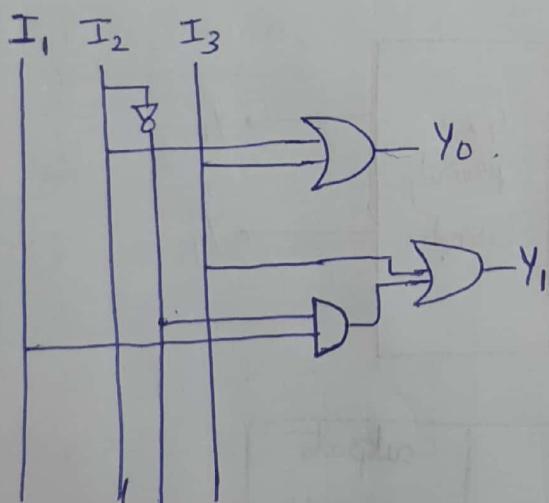
H.W

⑧ Design a Decimal to BCD Encoders?

## Multiplexers:-

- Multiplexers is also called as Data Selectors.
- It is a logic circuit that accepts several data inputs and allows only one of them to get through to the output.
- The routing of the desired data input to the output is controlled by select inputs.


## Block diagram:-

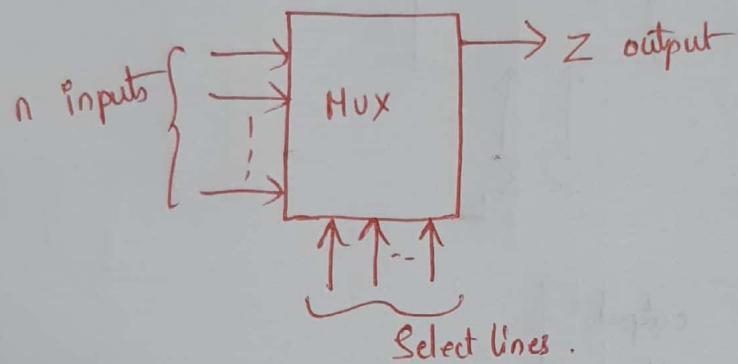


## 2x1 Mux

- It has two inputs, one select line and one output.

## Block diagram

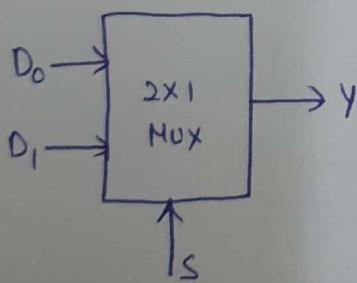

## Logic Circuit

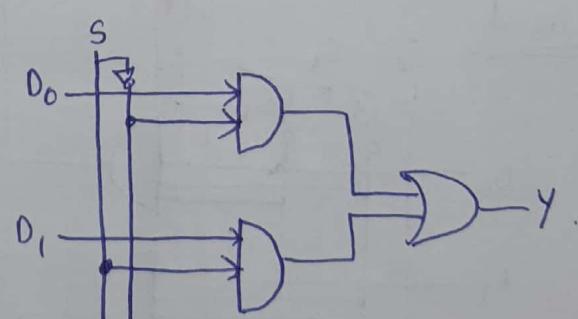

## Truth Table

S	output
0	$D_0$
1	$D_1$


50

$$4 = 2^2 \rightarrow \text{Select lines}$$

4x1 Mux :-

It has 4 inputs, 2 select lines and one output.


Block diagram :-

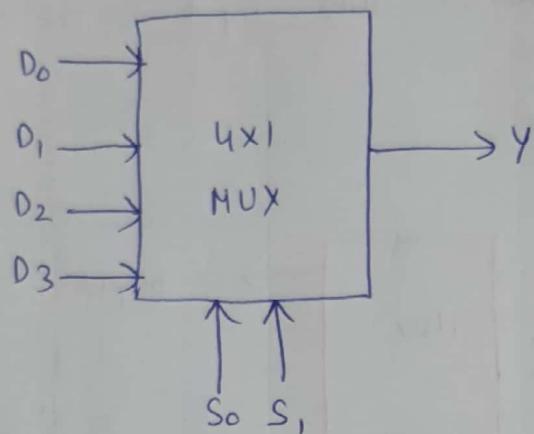

Truth Table


Inputs		outputs
S <sub>0</sub>	S <sub>1</sub>	Y
0	0	D <sub>0</sub>
0	1	D <sub>1</sub>
1	0	D <sub>2</sub>
1	1	D <sub>3</sub>

Logic Circuit

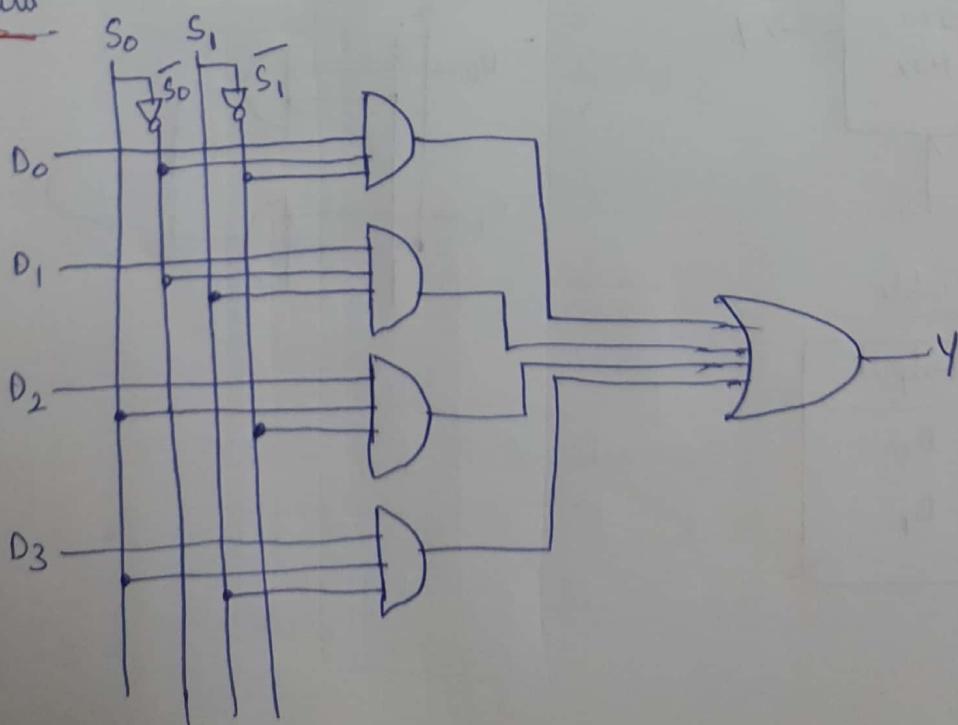

8x1 MUX :- It has 8 Inputs, 3 Select Lines and one output.


### Block Diagram

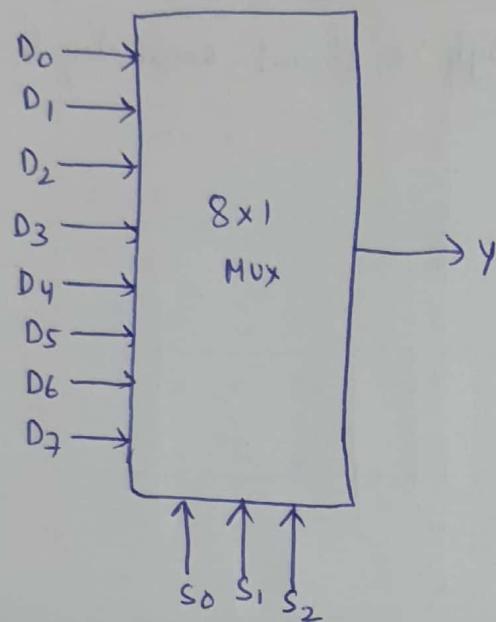


Truth Table

Inputs	Output
S <sub>0</sub> S <sub>1</sub> S <sub>2</sub>	Y
0 0 0	D <sub>0</sub>
0 0 1	D <sub>1</sub>
0 1 0	D <sub>2</sub>
0 1 1	D <sub>3</sub>
1 0 0	D <sub>4</sub>
1 0 1	D <sub>5</sub>
1 1 0	D <sub>6</sub>
1 1 1	D <sub>7</sub>

### Logic Circuit

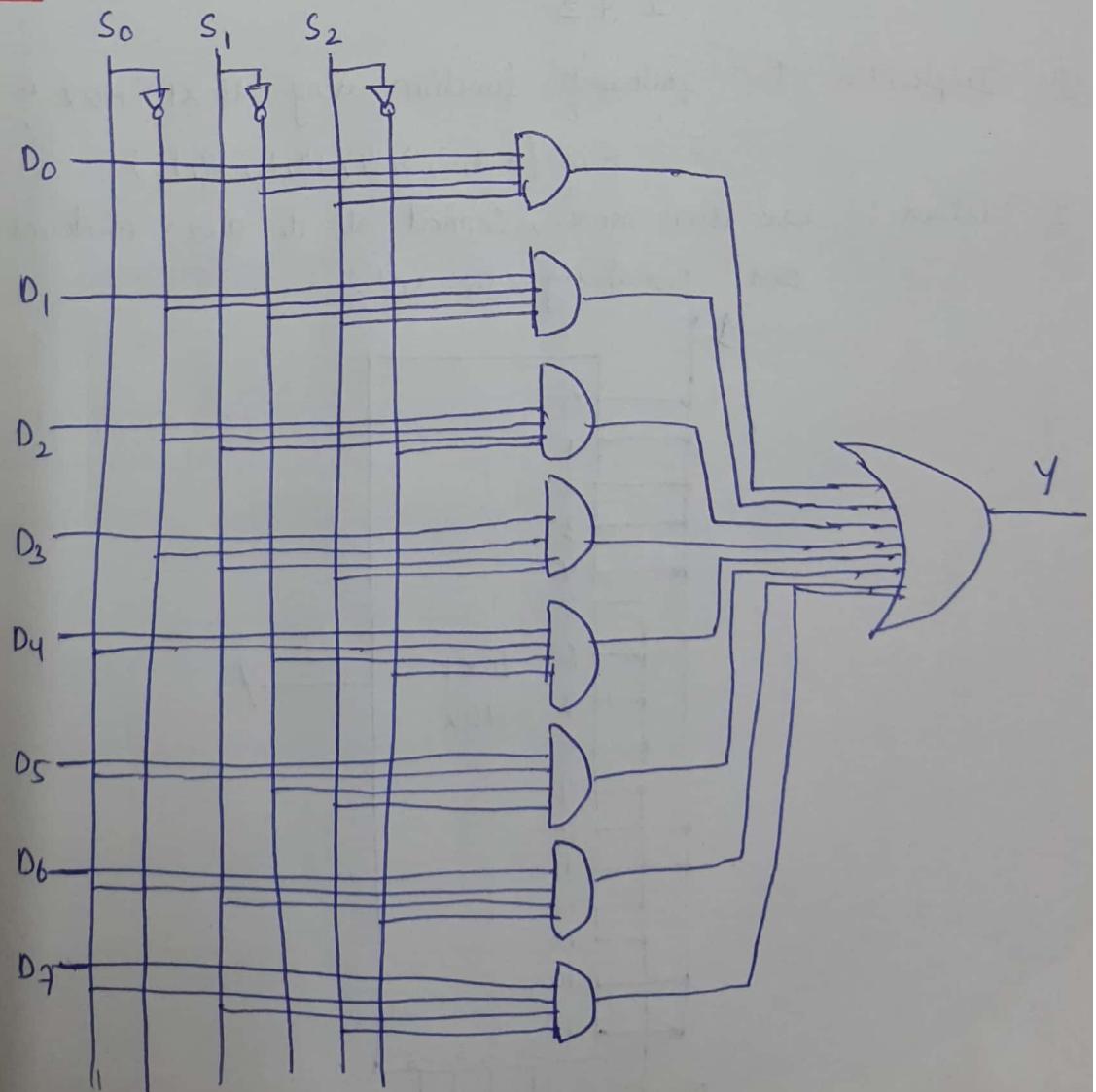

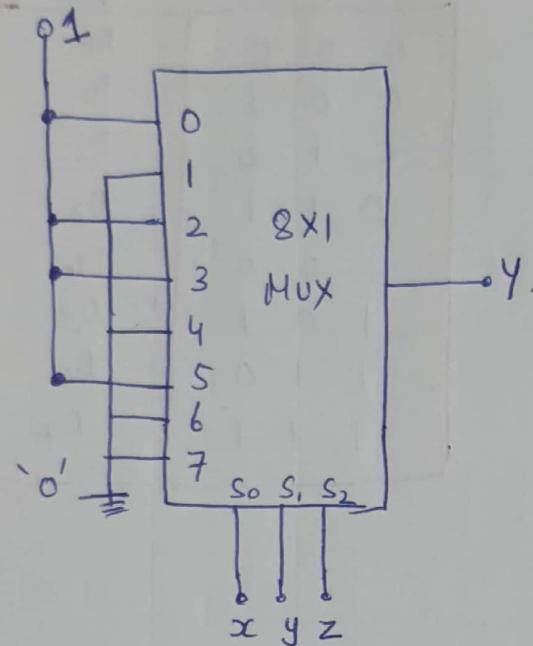
- (5)
- ④ Use the MUX to implement the logic function  
 $F(x, y, z) = \sum m(0, 2, 3, 5)$
- As the given function is 3 Variable we need to use  $8 \times 1$  mux  
 Connect all the given minterms to high i.e '1' and remaining to '0'.



- ⑤ Implement the following function using  $16 \times 1$  MUX ?

$$F = \sum m(0, 1, 2, 3, 4, 10, 11, 14, 15).$$

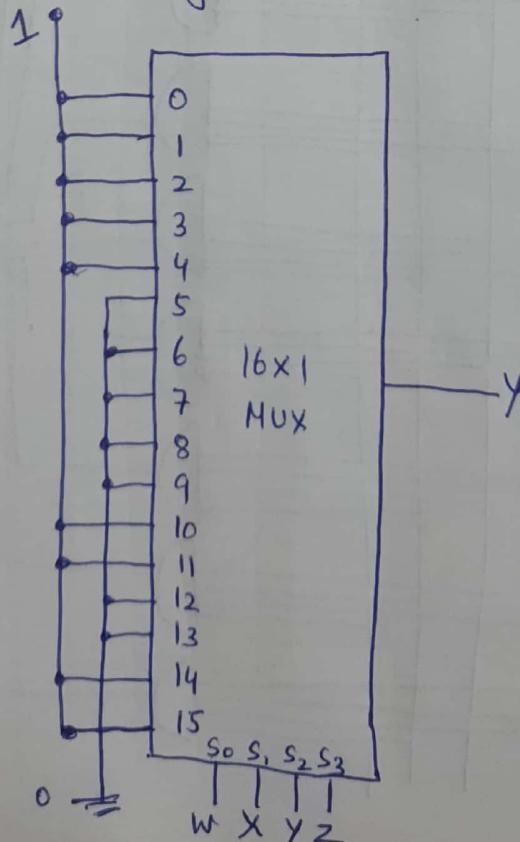- Ques :- use  $16 \times 1$  mux , Connect all the given minterms to high '1' and remaining to '0'.



Q) Use  $8 \times 1$  Mux to implement the logic function  $f(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 10, 11, 14, 15)$ ?

≡

$S_0$	$S_1$	$S_2$		$f$
$A$	$B$	$C$	$D$	
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

$$F = 1 \rightarrow (D_0)$$

$$F = 1 \rightarrow (D_1)$$

$$F = \bar{D} \rightarrow (D_2)$$


$$F = 0 \rightarrow (D_3)$$

$$F = 0 \rightarrow (D_4)$$

$$F = 1 \rightarrow (D_5)$$

$$F = 0 \rightarrow (D_6)$$

$$F = 1 \rightarrow (D_7)$$

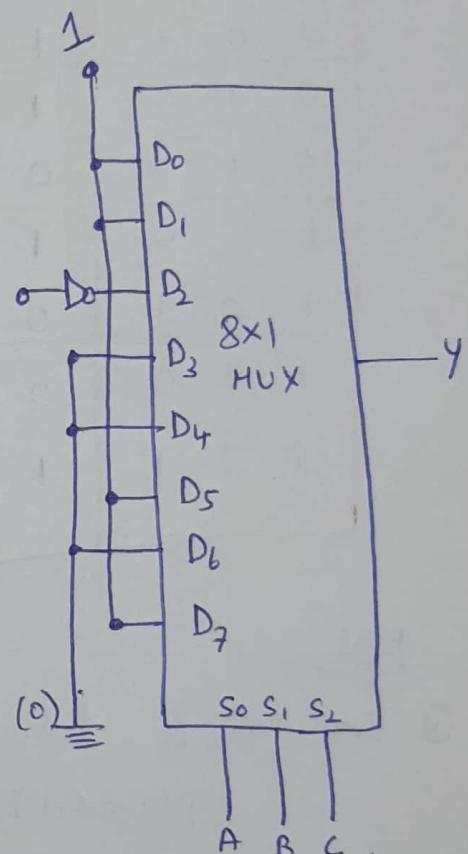

(54)

- ① Implement the logic function  $f(A, B, C) = \sum m(1, 2, 4, 7)$  by using 4x1 MUX?

S

Truth Table


A	B	C	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
<hr/>			$f = C(D_0)$
1	0	0	
1	0	1	0
<hr/>			$f = \bar{C}(D_1)$
1	1	0	
1	1	1	1

$$f = C(D_0)$$

$$f = \bar{C}(D_1)$$

$$f = \bar{C}(D_2)$$

$$f = C(D_3)$$

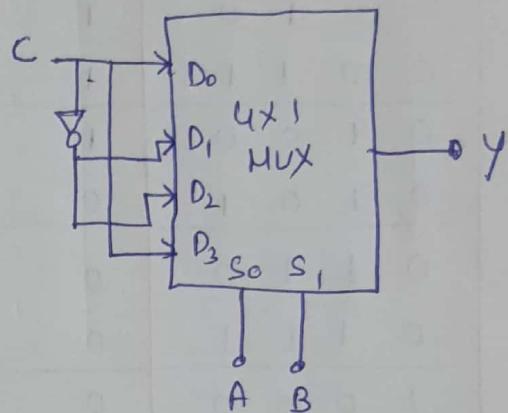H.W

- ① Implement the following function using 8x1 MUX

$$F(A, B, C, D) = \sum m(1, 3, 4, 11, 12, 13, 14, 15)$$

- ② Implement the following boolean function  $F(a, b, c) = ab + \bar{b}c$  using 4:1 MUX


- ③ Implement the boolean function

$$F(A, B, C, D) = A\bar{B} + BD + \bar{B}C\bar{D} \text{ using } 16 \times 1 \text{ mux}$$

and 8x1 MUX.
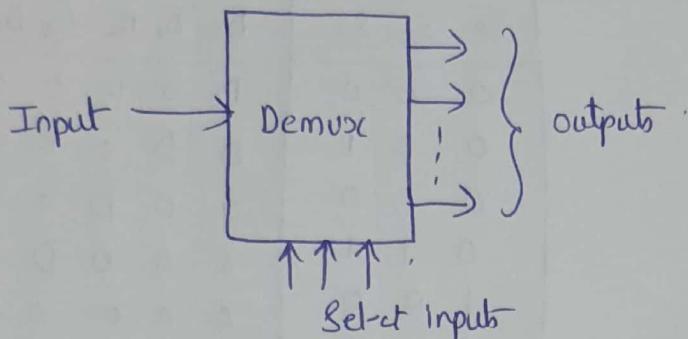
### Demultiplexers :-


- It is also called as Data Distributor.
- It performs reverse operation of Multiplexers.
- It takes single input and distribute to the several outputs.



### 1 to 4 De-mux.

- It has one input, two select line ( $S_0, S_1$ ) and 4 outputs.


### Block diagram.

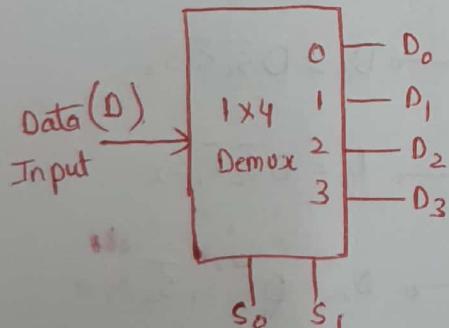

Truth Table

Inputs	Outputs					
	$S_0$	$S_1$	$D_0$	$D_1$	$D_2$	$D_3$
0 0	0 0		D	0	0	0
0 1	0 1		0	D	0	0
1 0	1 0		0	0	D	0
1 1	1 1		0	0	0	D


### Logic Circuit

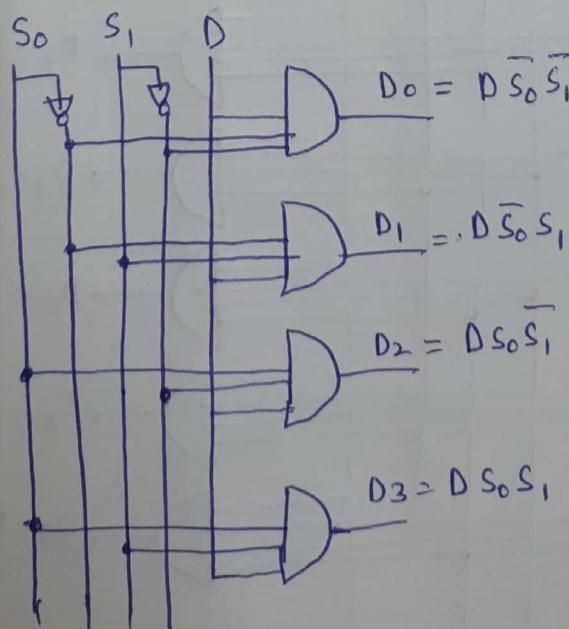

56

1x8 Demux :- It has one input 'D', eight outputs ( $D_0 - D_7$ ),  
Three select inputs ( $S_0, S_1, S_2$ )


Block diagram

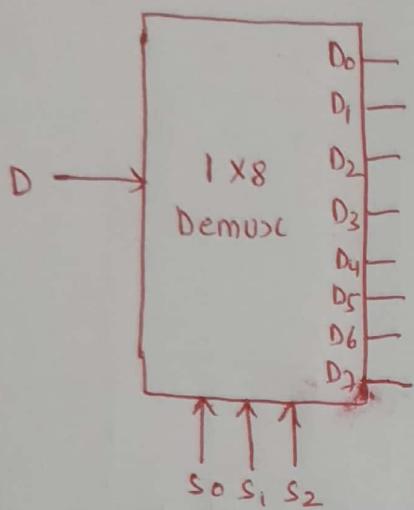

Truth Table


Inputs			Outputs							
$S_0$	$S_1$	$S_2$	$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Logic Circuit

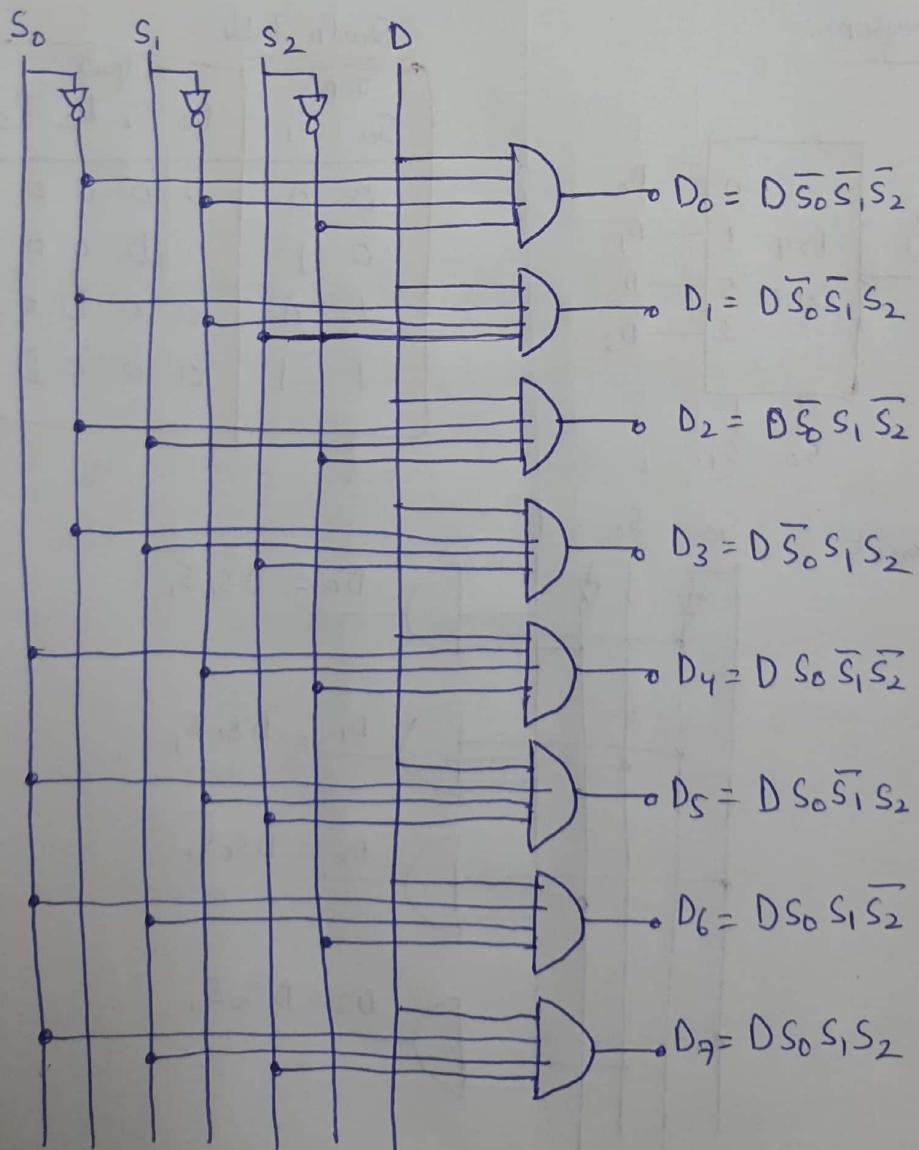

⑤ Implement 16x1 MUX using two 8x1 MUX?

Q

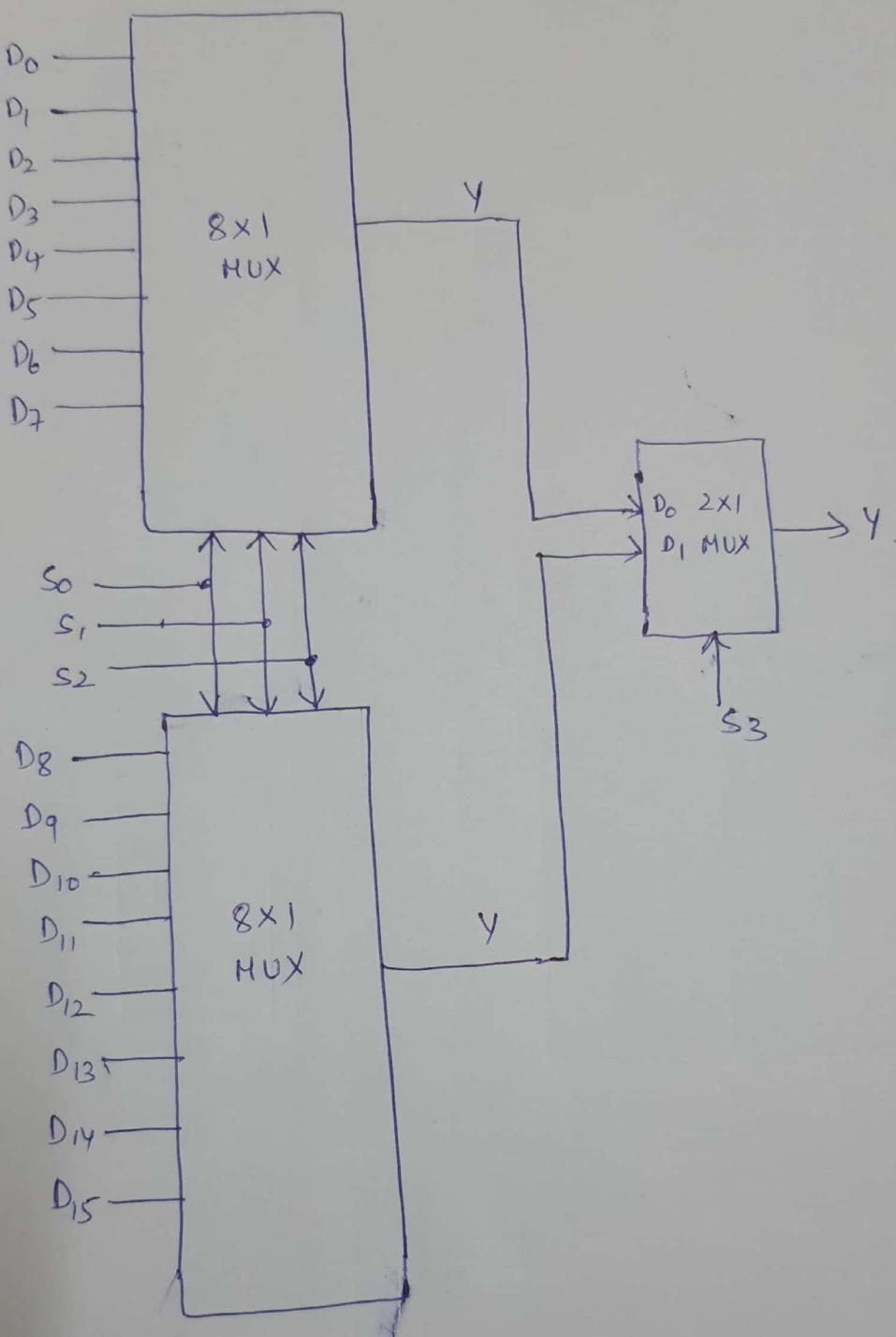

X